

# High Step-up Ratio DC-DC Converter Topologies

## Part I

Speaker: G. Spiazzi

P. Tenti, L. Rossetto, G. Spiazzi, S. Buso, P. Mattavelli,  
L. Corradini

Dept. of Information Engineering - DEI  
University of Padova

---



# Seminar Outline

---

- Why we need high step-up ratio converters?
  - Application fields
- Low power high step-up ratio topologies
  - Coupled inductors
- High power high step-up ratio topologies
  - Non isolated
  - Isolated




# High Step-up Ratio Topologies

---

## Why?

- Low-voltage high-current energy sources
  - Fuel-cells (some kW)
  - Paralleled photovoltaic modules in domestic applications (some kW)
  - Microinverter, i.e. connection of a single photovoltaic module to the grid (some hundred watts)
- Step-down inverters require an input voltage higher than the maximum line voltage peak

# Example of Microinverter

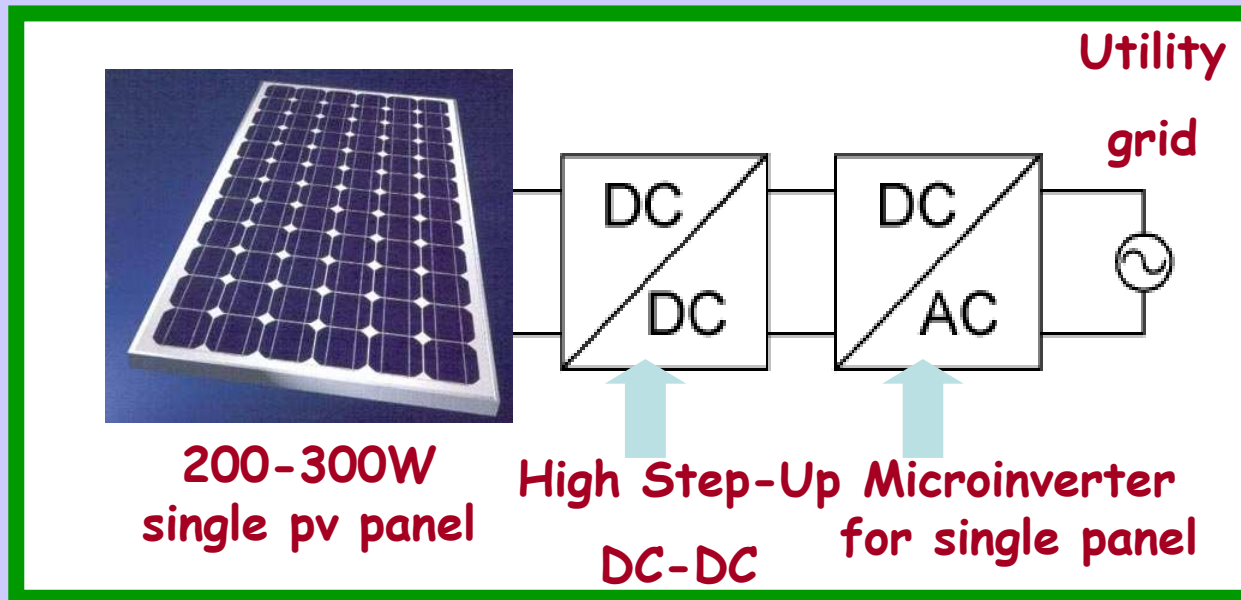


**Microinverter structure**

- Modularity
- Reduction of partial shading effects
- Dedicated Maximum Power Point Tracker (MPPT)
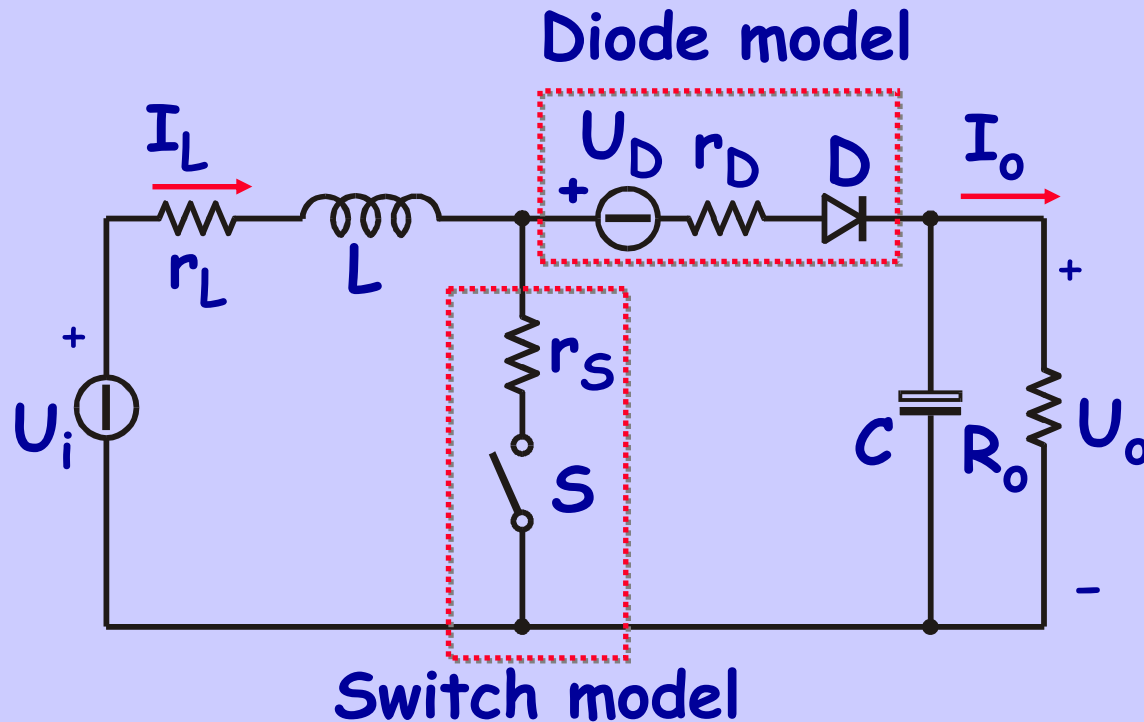
# Simple Boost Topology

Boost scheme including some parasitic elements:




Voltage conversion ratio (neglecting inductor current ripple):

$$M = \frac{1}{1-d} \frac{1}{1 + \frac{r_D(1-d) + r_S d + r_L}{R_o(1-d)^2} + \frac{U_D}{U_o}} = \frac{1}{1-d} \cdot F(d, U_o, R_o)$$
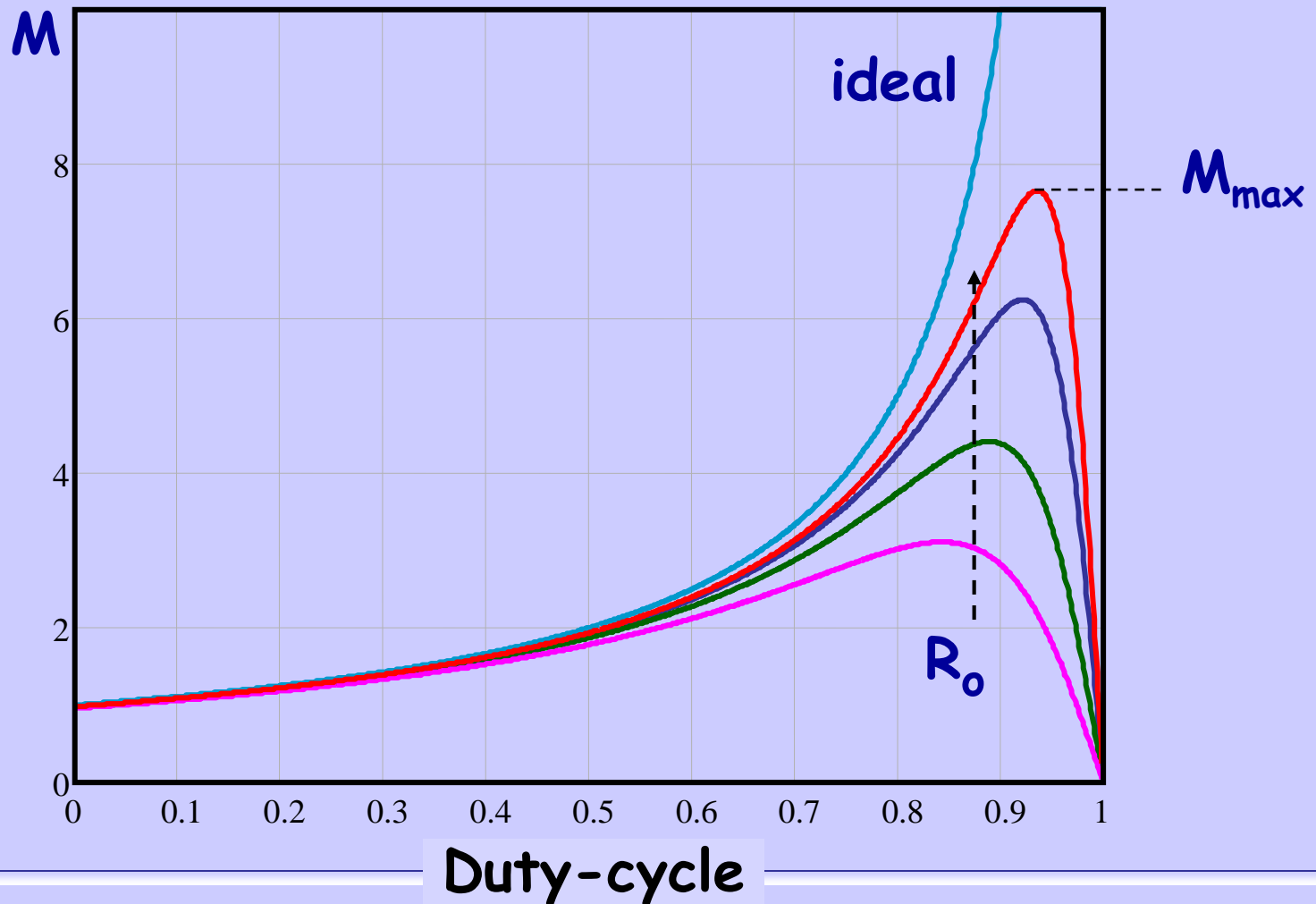
# Simple Boost Topology


Voltage conversion ratio  $M$  including conduction losses:


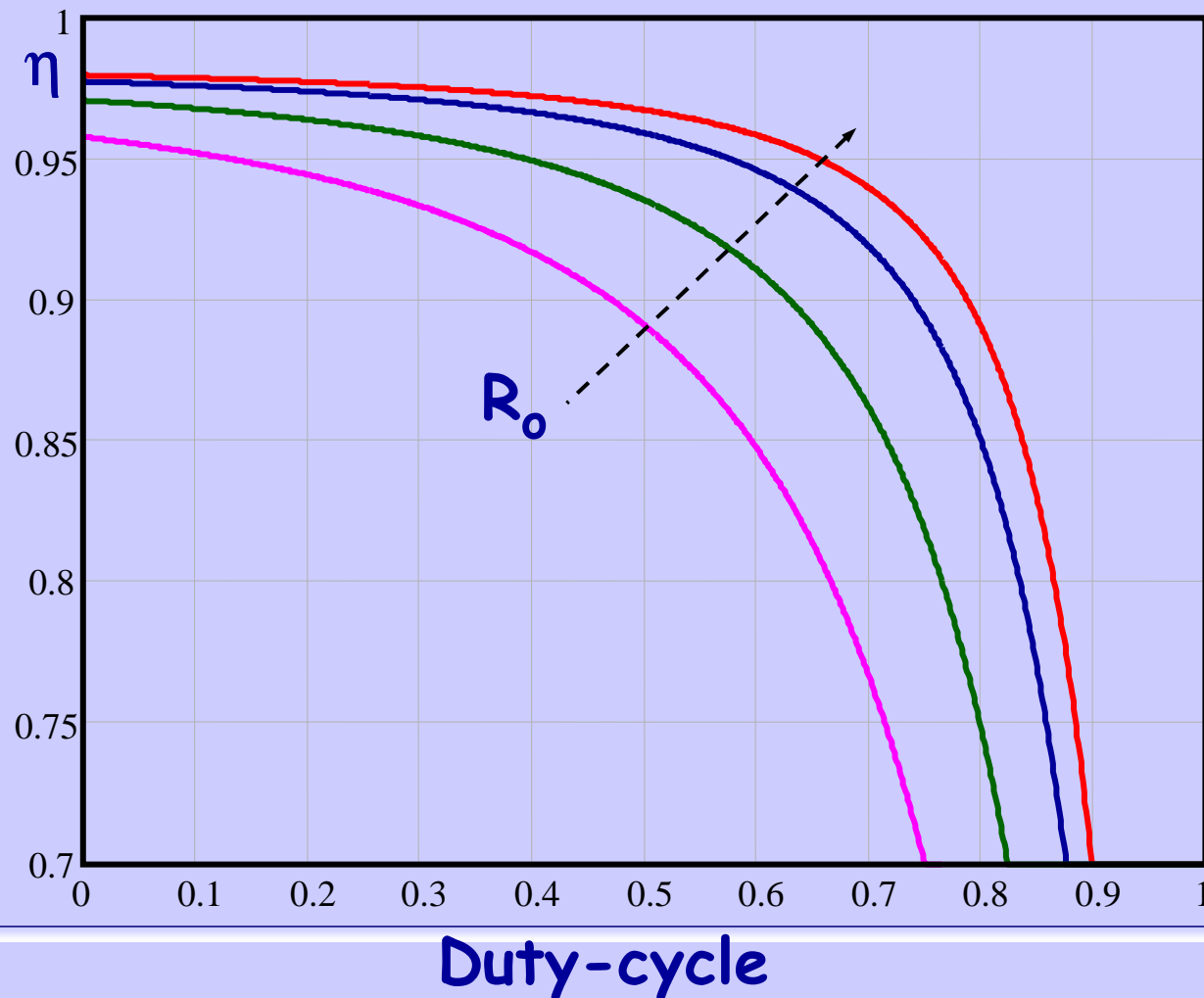
# Simple Boost Topology


Converter efficiency:

$$\eta = \frac{P_{out}}{P_{in}} = \frac{U_o I_o}{U_{iL}} = \frac{U_o I_D}{U_{iL}} = M(1-d) = F(d, U_o, R_o)$$



# Low Power Applications

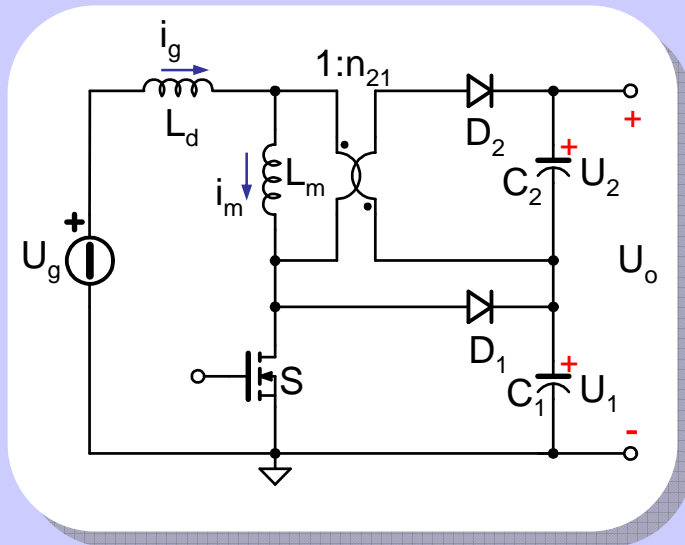- **Example:** integrated Boost-Flyback converter





It can be seen as a **flyback** converter with a non dissipative snubber:  $D_1$  and  $C_1$  deliver to the output the energy stored in the transformer leakage inductance  $L_d$



# Integrated Boost-Flyback Converter
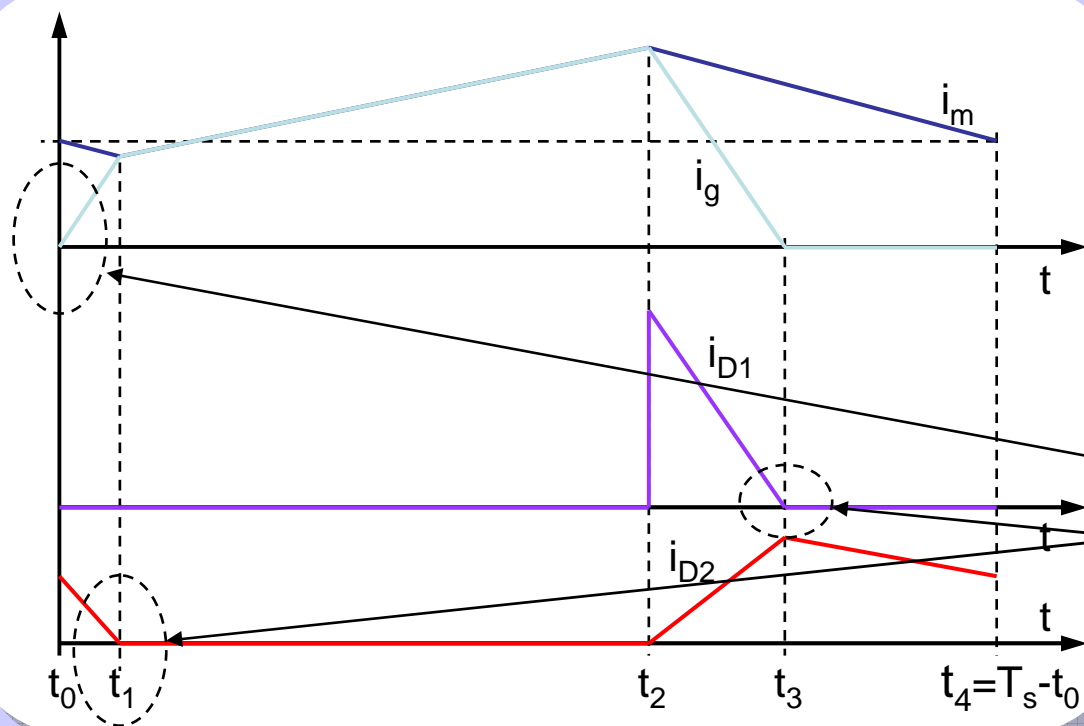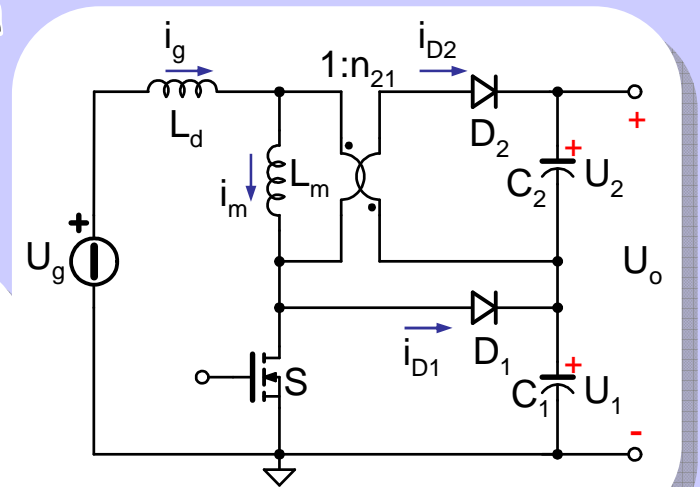
## Ideal waveforms:

- CCM operation of flyback section
- DCM operation of boost section




## Advantages:

- ZCS turn on
- Soft diode turn off
- Reduced switch voltage stress

# Integrated Boost-Flyback Converter
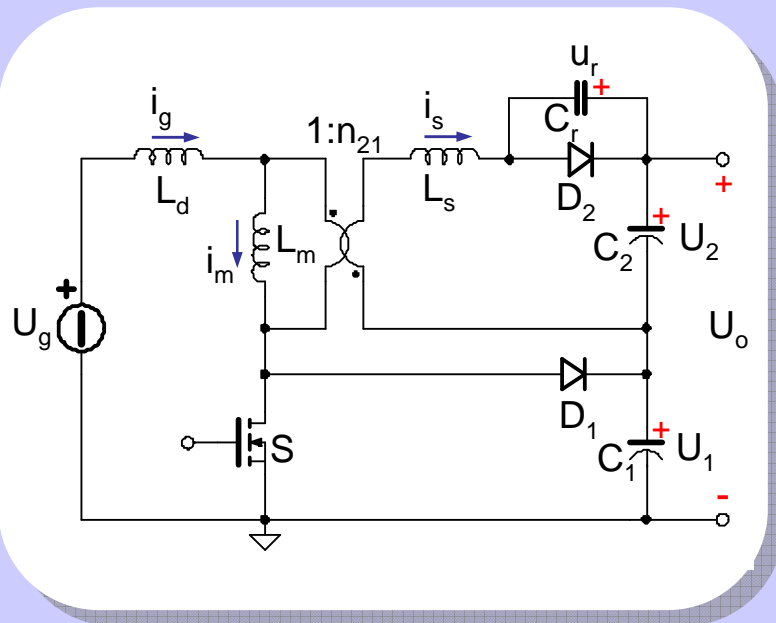
## Problems:


Parasitic oscillations at  $D_2$  turn off caused by its capacitance  $C_r$  resonating with transformer leakage inductances  $L_d$  and  $L_s$



High voltage stress  
across  $D_2$

Dissipative R-C-D snubber  
is needed

# Modified IBF Converter

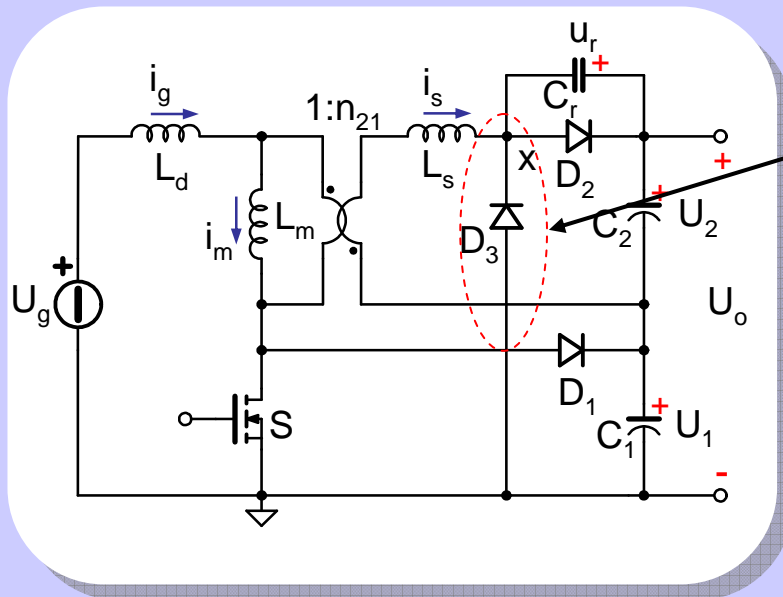


Clamping diode  $D_3$  added to the original topology


## Advantages:

- Clean diode voltage waveforms without parasitic oscillations
- Energy transfer toward the output also during switch turn on interval
- Slight voltage gain increase due to resonances between parasitic components


# Modified IBF Converter

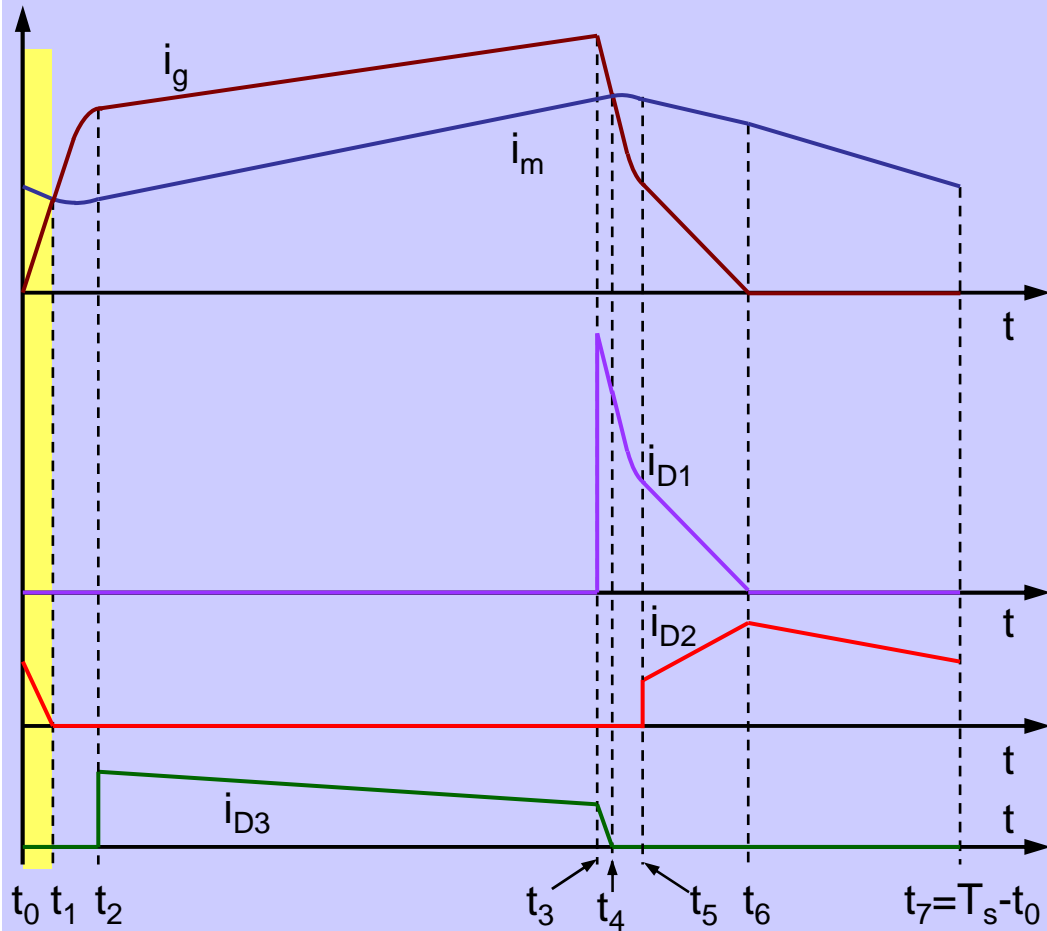


Interval  $T_{01} = t_1 - t_0$

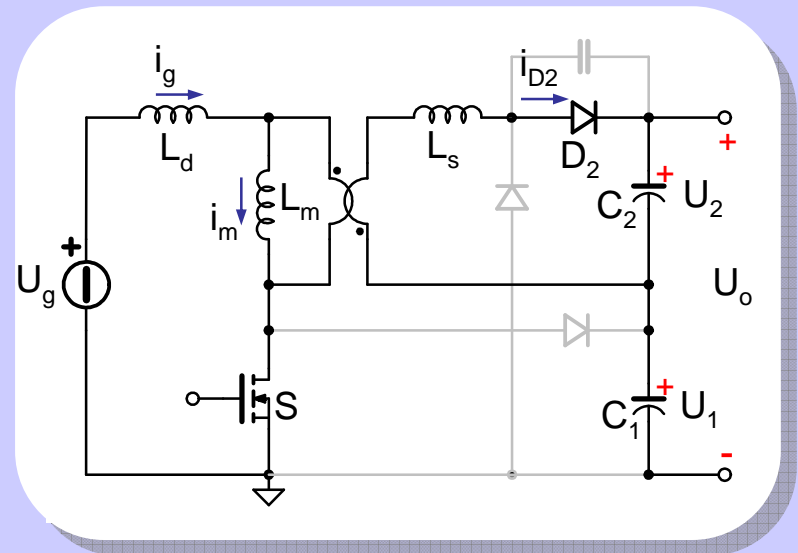


# Modified IBF Converter

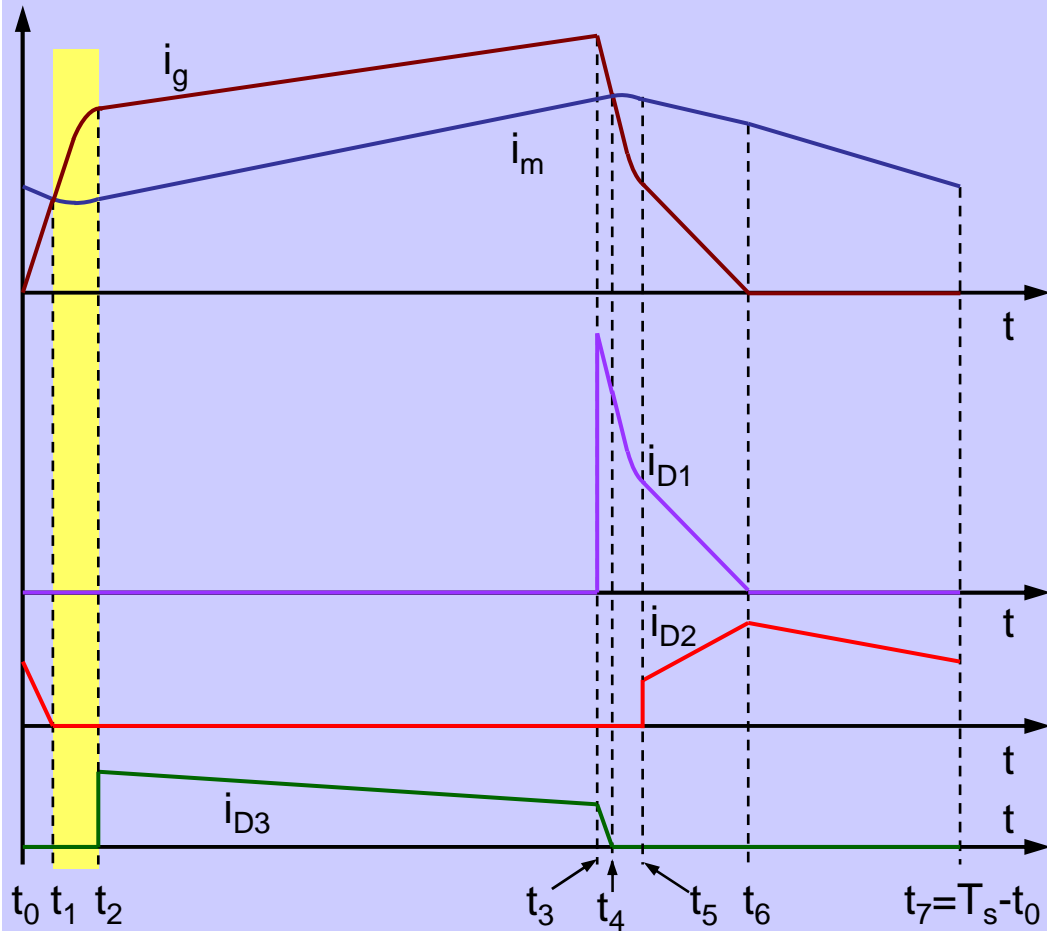


Interval  $T_{12} = t_2 - t_1$

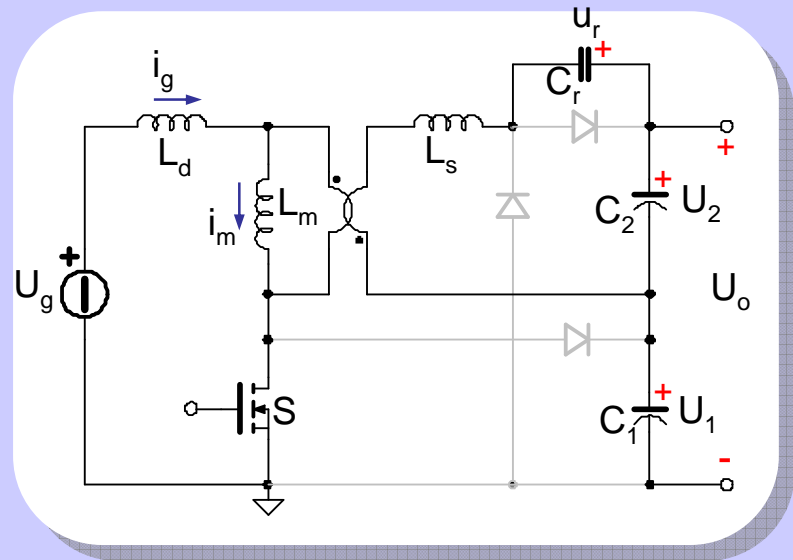

# Modified IBF Converter

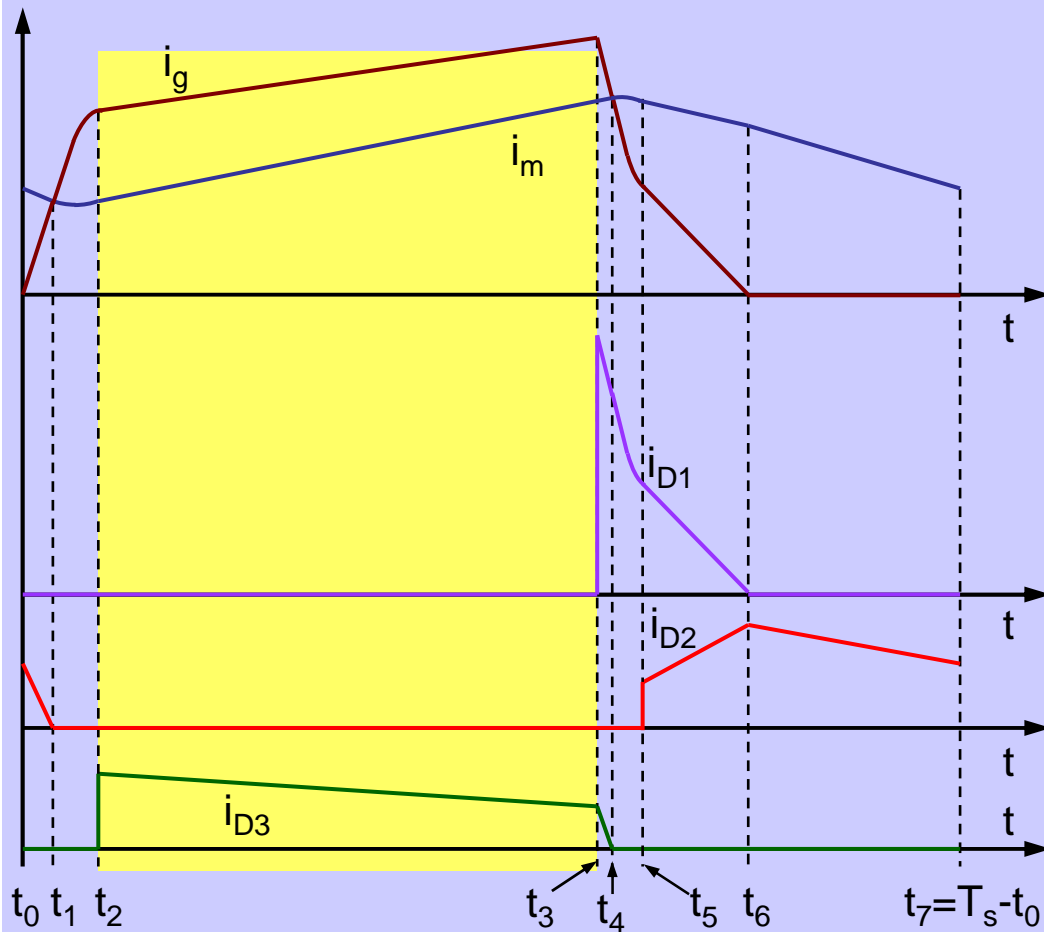


Interval  $T_{23} = t_3 - t_2$

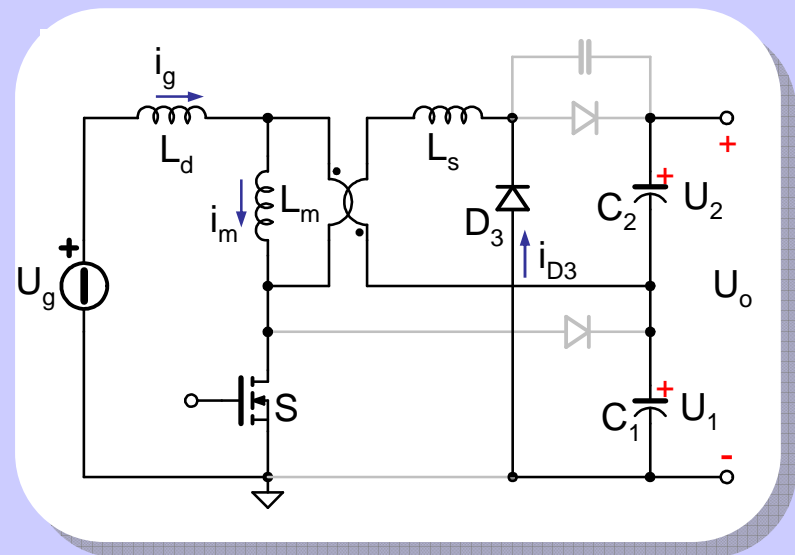


Note: actual  $i_{D3}$  slope can be either positive or negative


# Modified IBF Converter

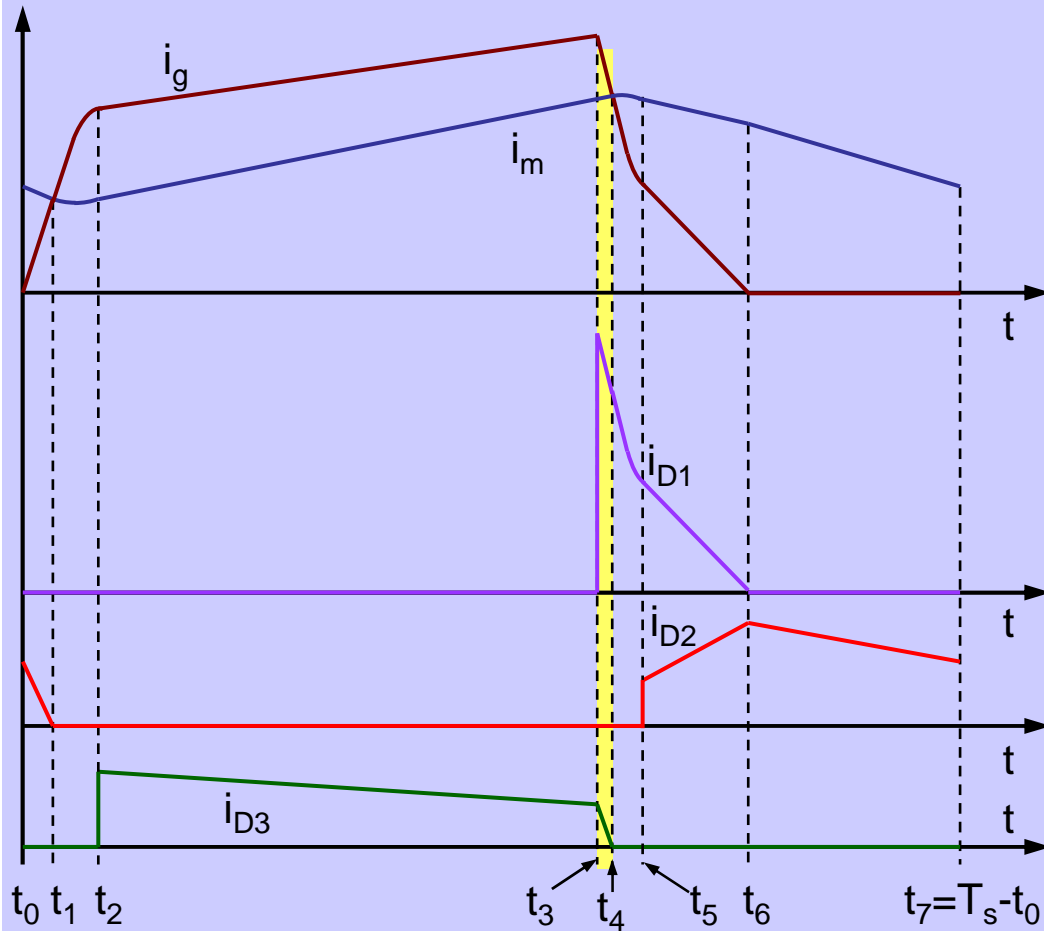


Interval  $T_{34} = t_4 - t_3$

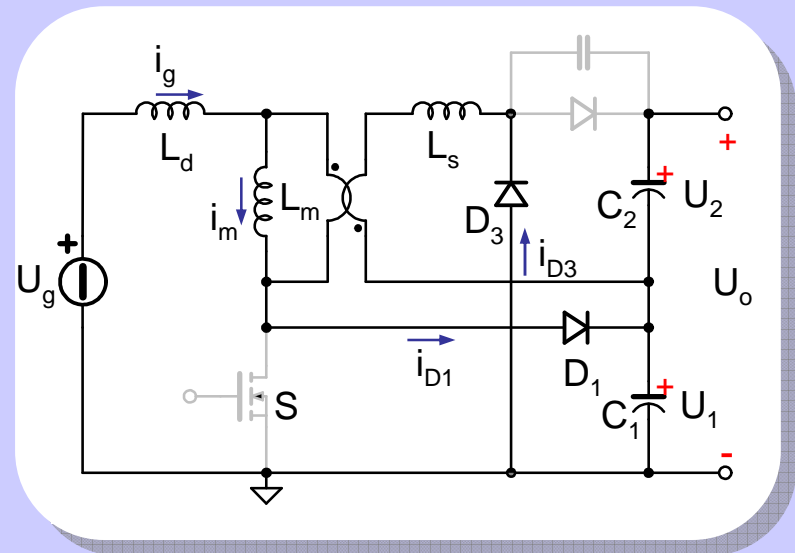

# Modified IBF Converter

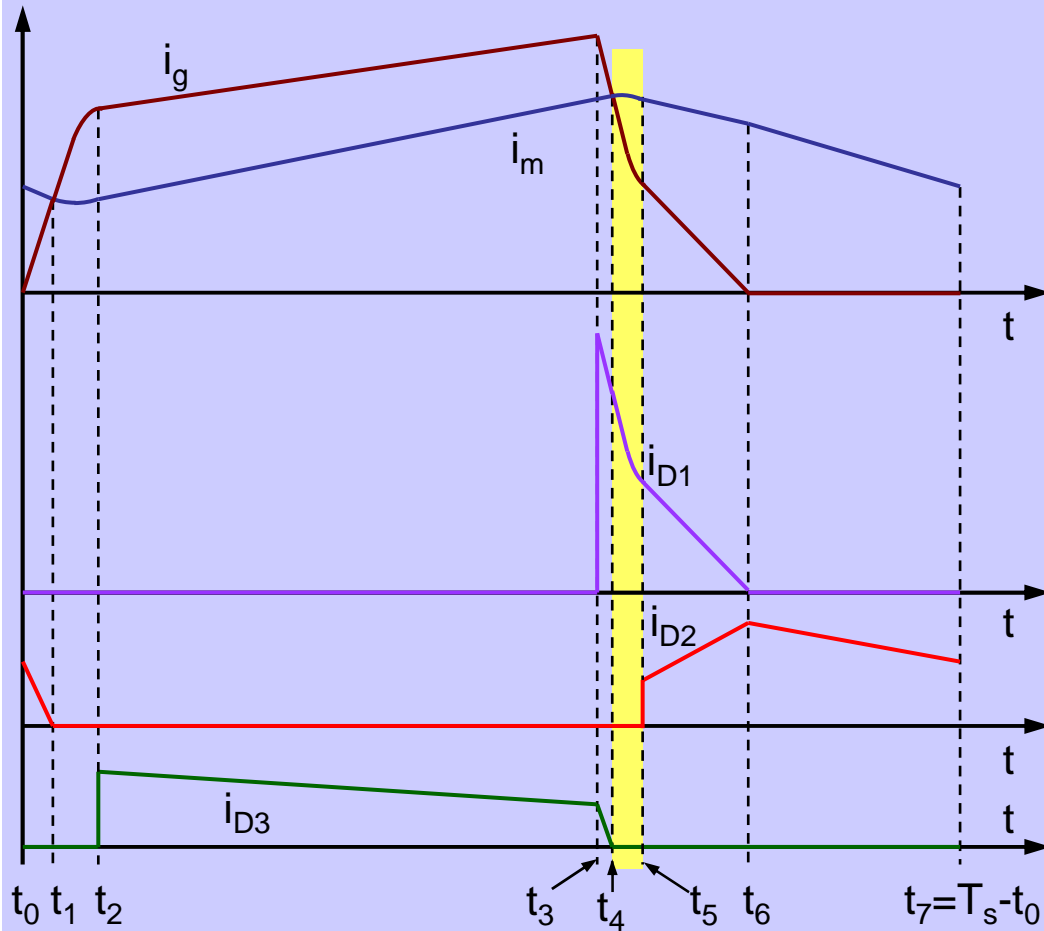


Interval  $T_{45} = t_5 - t_4$

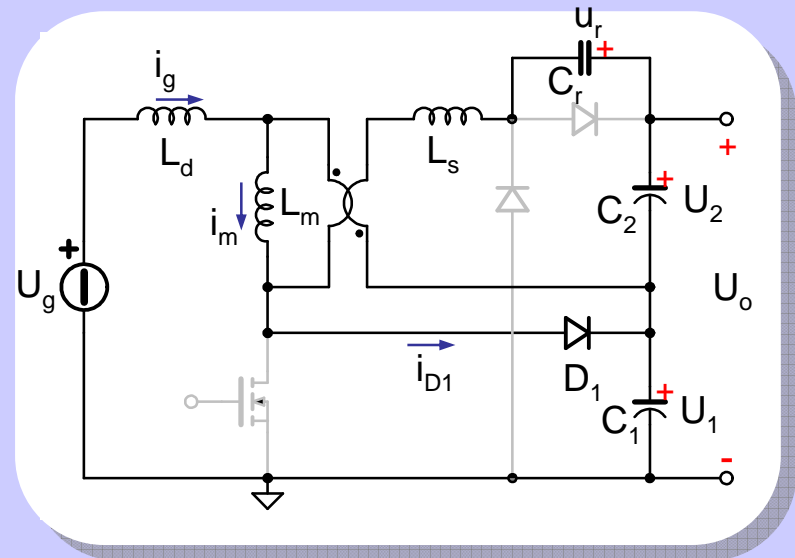





# Modified IBF Converter

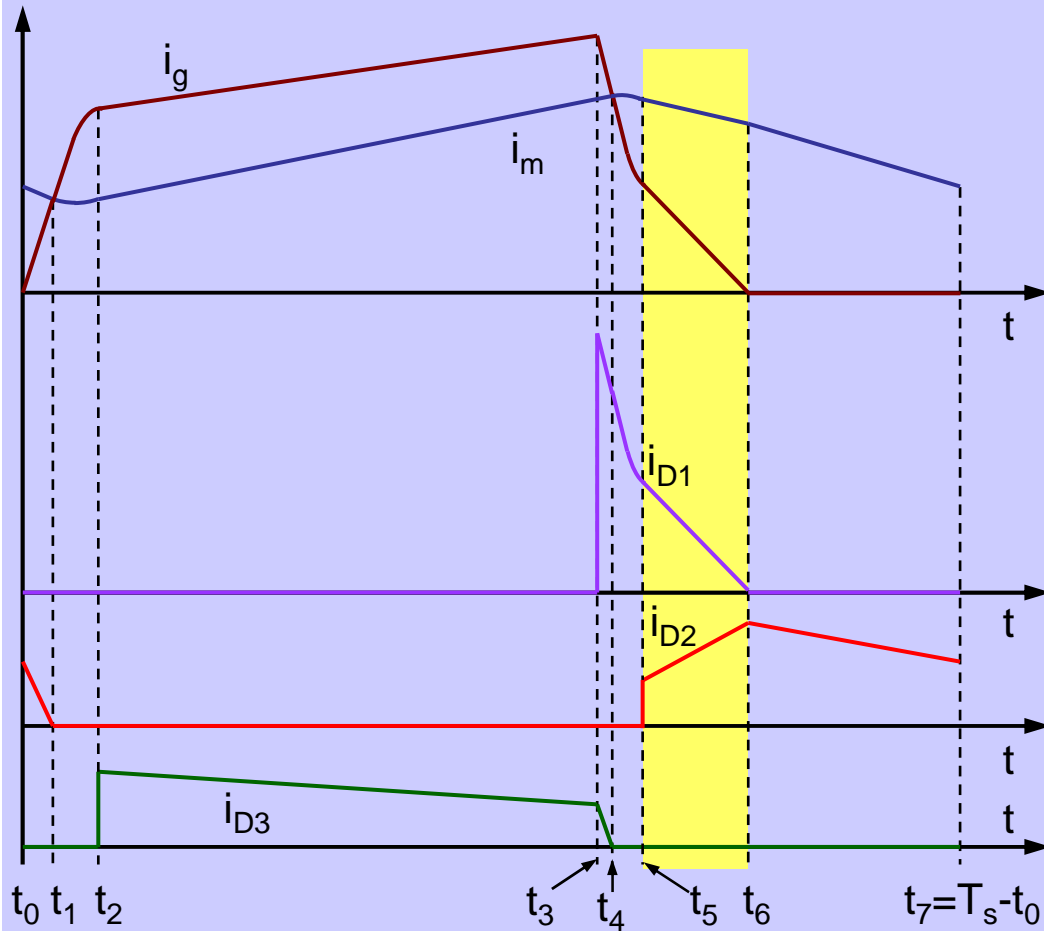


Interval  $T_{56} = t_6 - t_5$

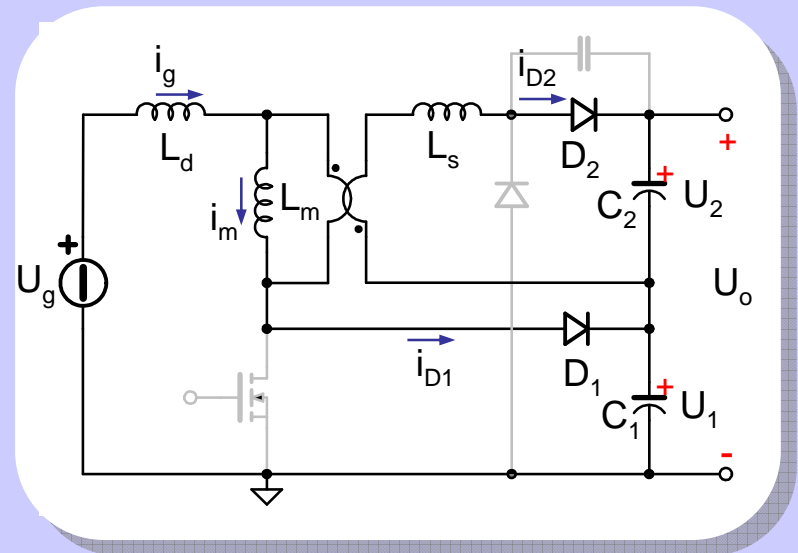

# Modified IBF Converter

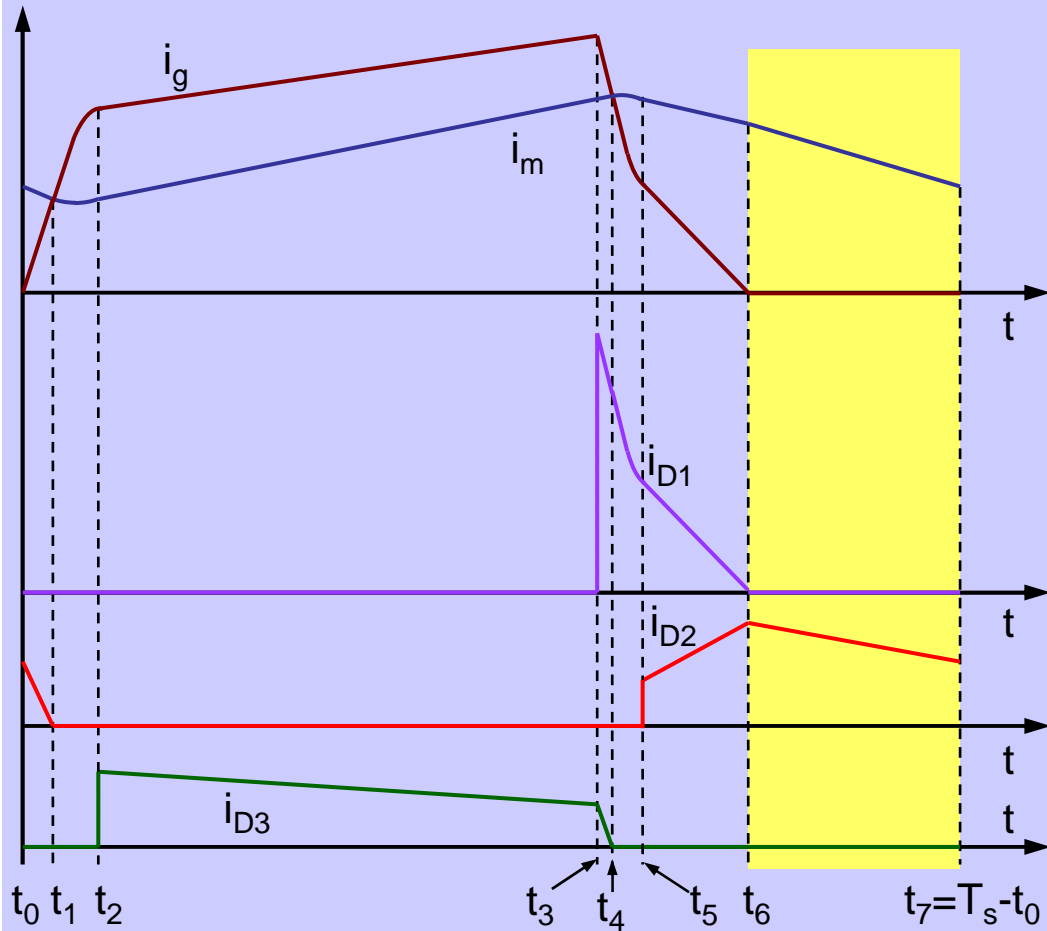

Interval  $T_{67} = t_7 - t_6$

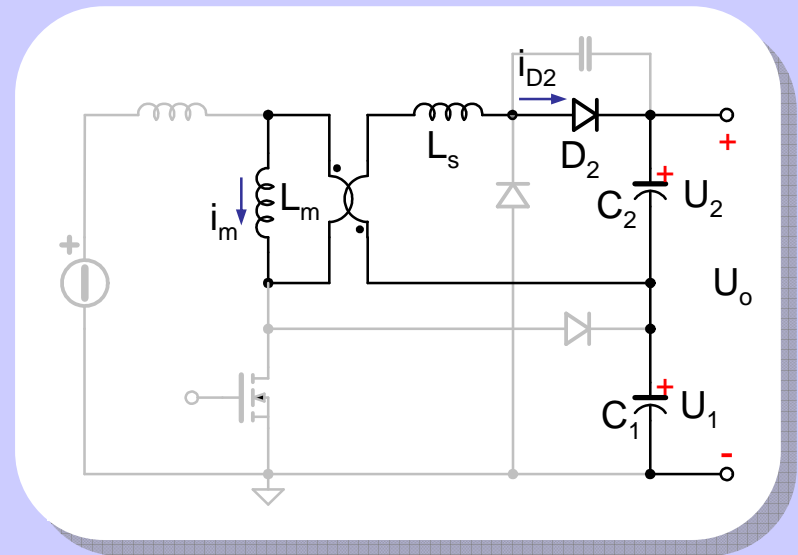



# Converter Parameters


---

- Input voltage:  $U_g = 25-35 \text{ V}$
- Output voltage:  $U_o = 400 \text{ V}$
- Nominal output power:  $P_o = 300 \text{ W}$
- Switching frequency:  $f_s = 100 \text{ kHz}$
  
- Magnetizing inductance:  $L_m = 20 \mu\text{H}$
- Primary leakage inductance:  $L_d = 0.4 \mu\text{H}$
- Secondary leakage inductance:  $L_s = 2 \mu\text{H}$
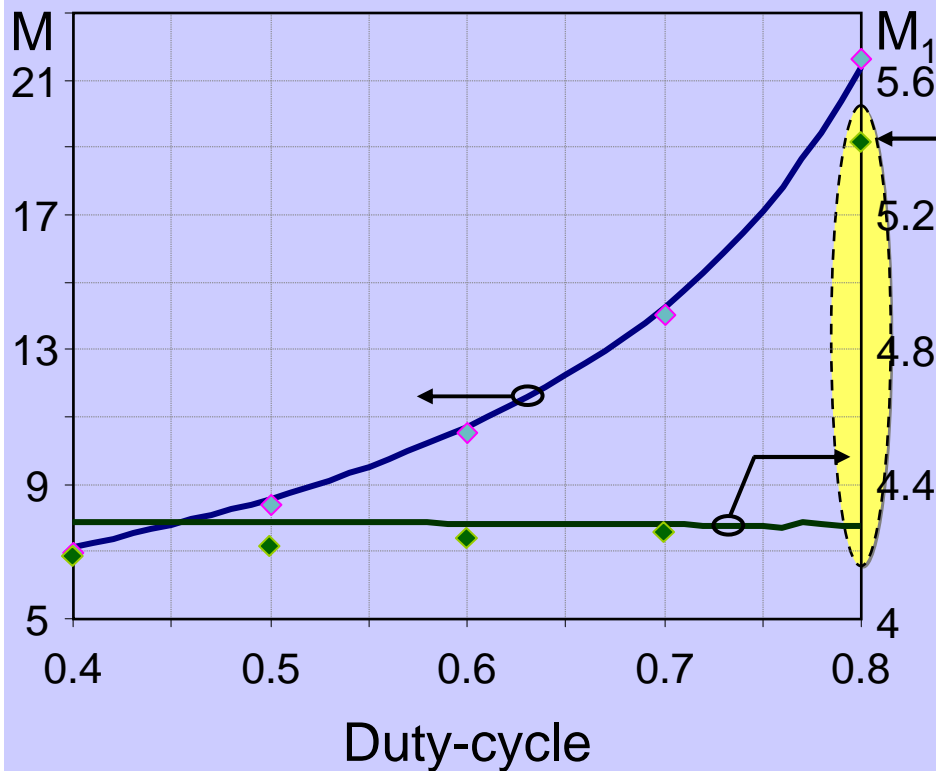
# Voltage Conversion Ratio

Comparison between calculations and spice simulations


$$M = \frac{U_o}{U_g} \quad M_1 = \frac{U_1}{U_g}$$



This unmatched point corresponds to a different topological sequence
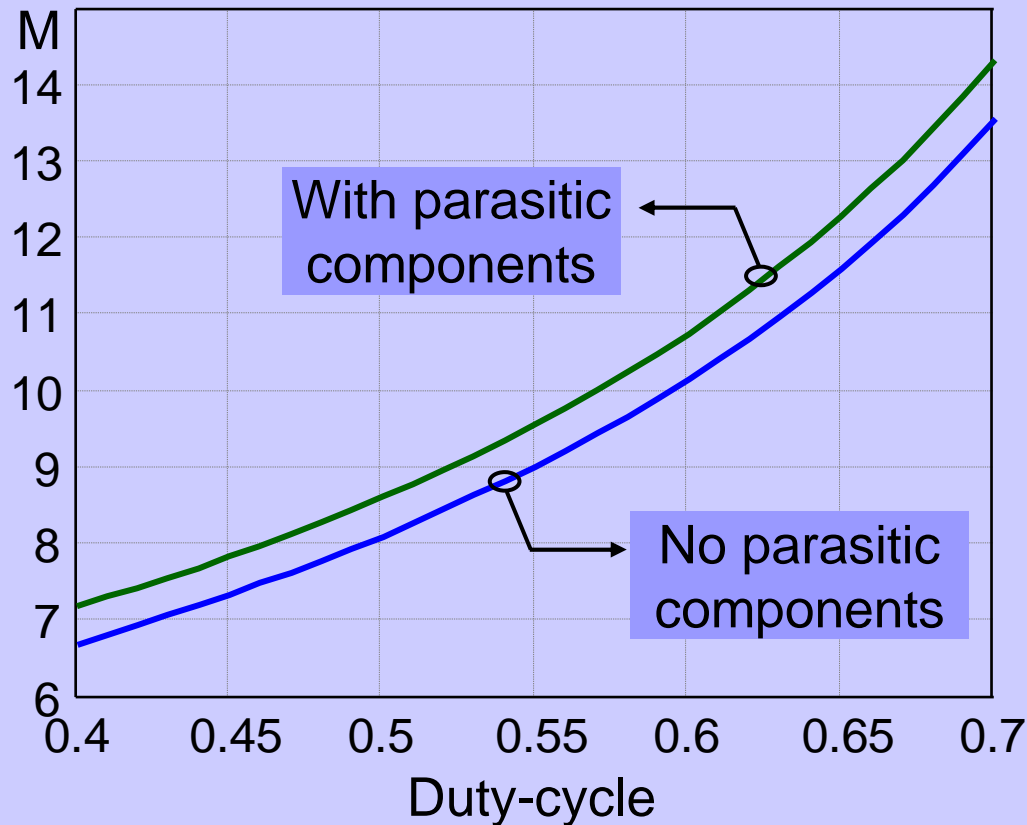
# Voltage Conversion Ratio


Effect of resonant intervals on the overall voltage gain



$$M = \frac{U_o}{U_g}$$
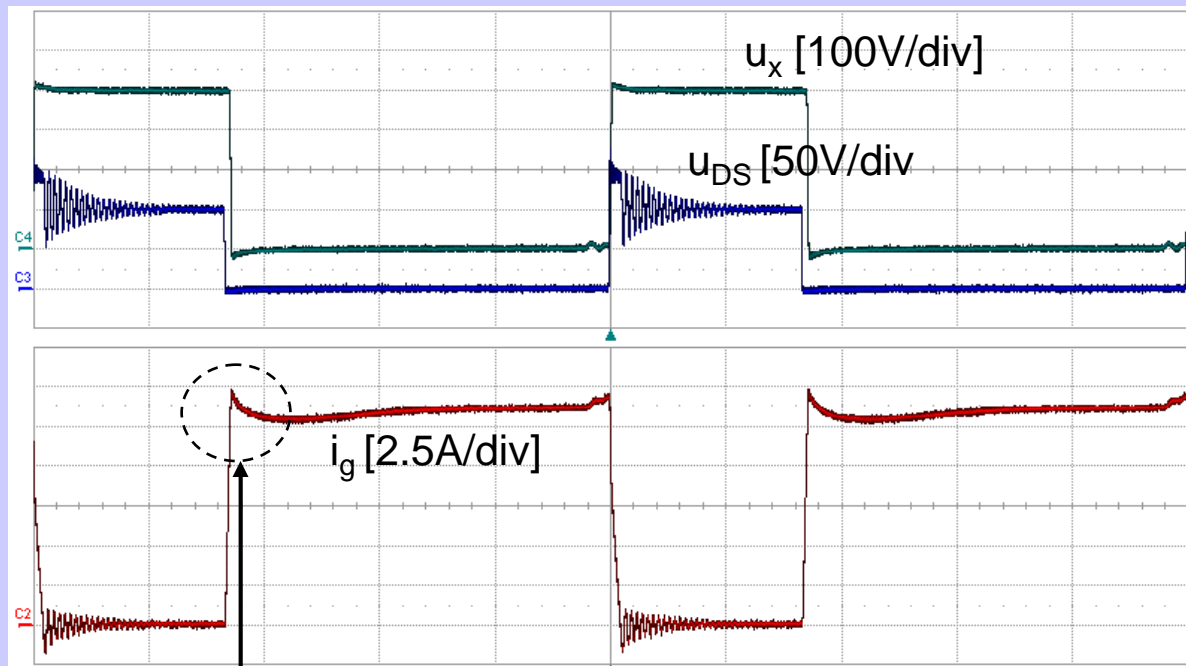
# Experimental Results



$$U_g = 35 \text{ V}, U_o = 400 \text{ V}, P_o = 300 \text{ W}$$



Peaking due to a small dip in the converter input voltage due to fast current rise time

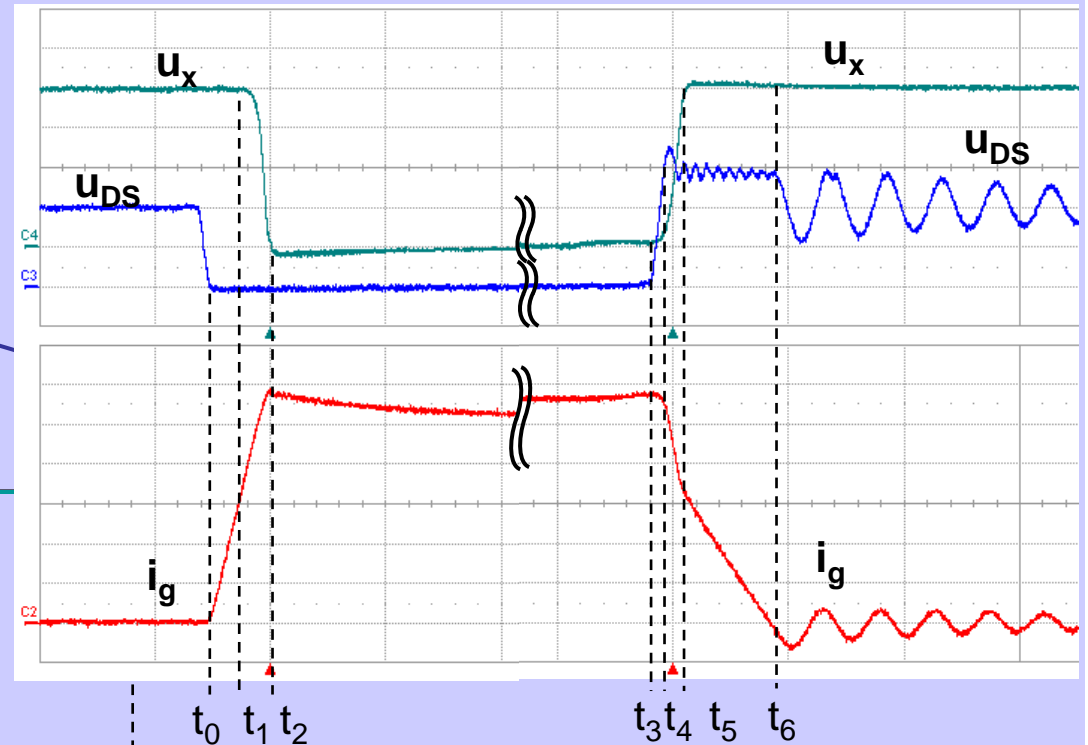
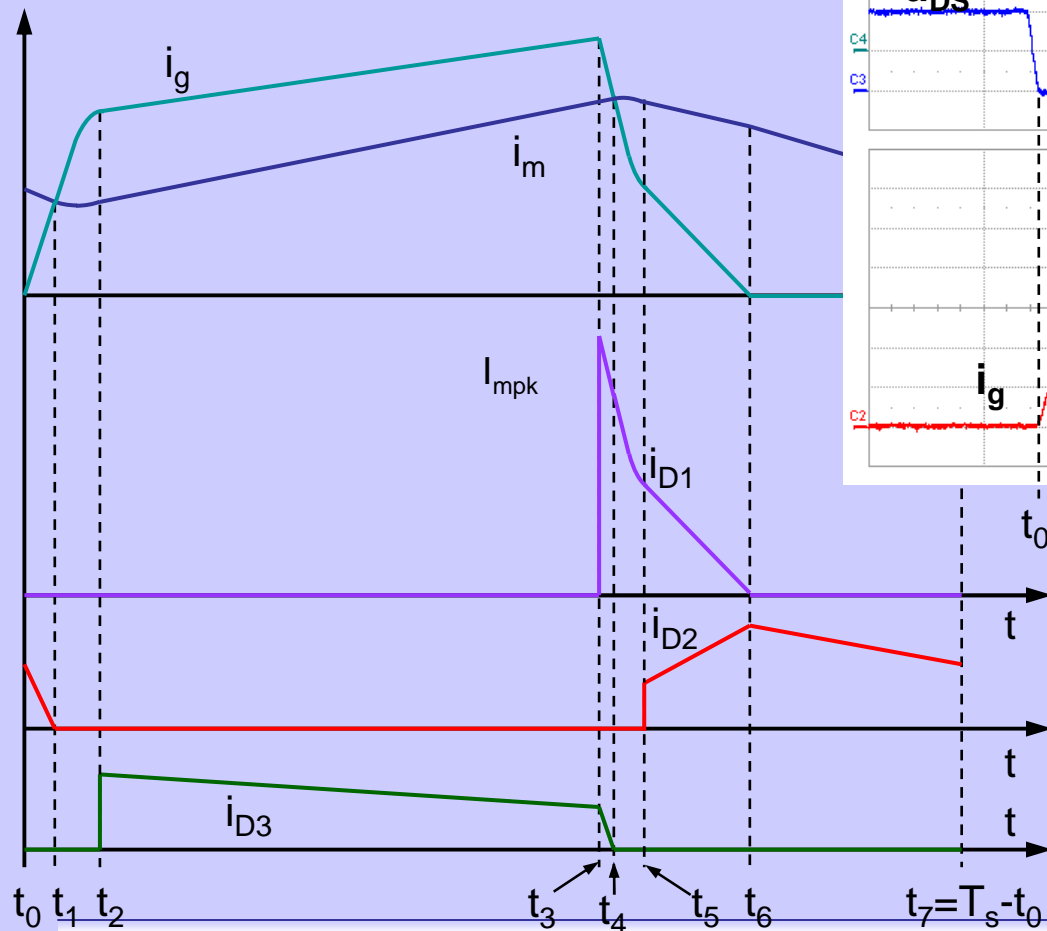
# Experimental Results

$$U_g = 35 \text{ V}, U_o = 400 \text{ V}, \\ P_o = 300 \text{ W}$$


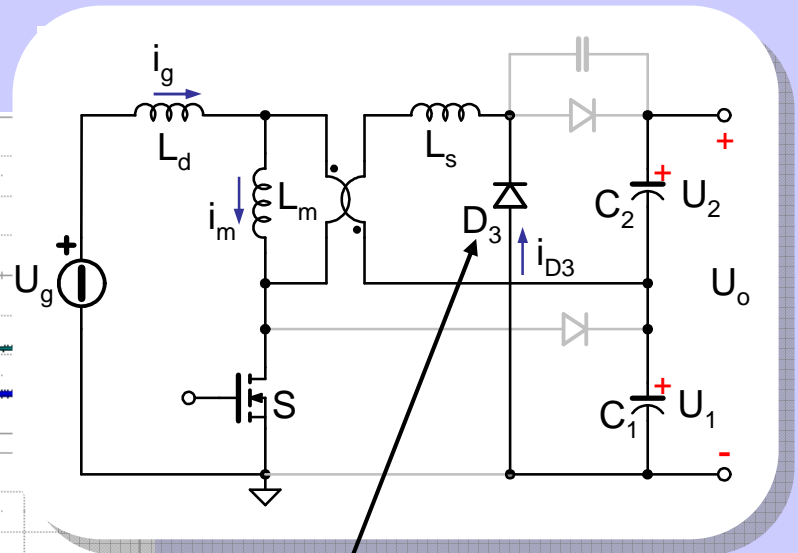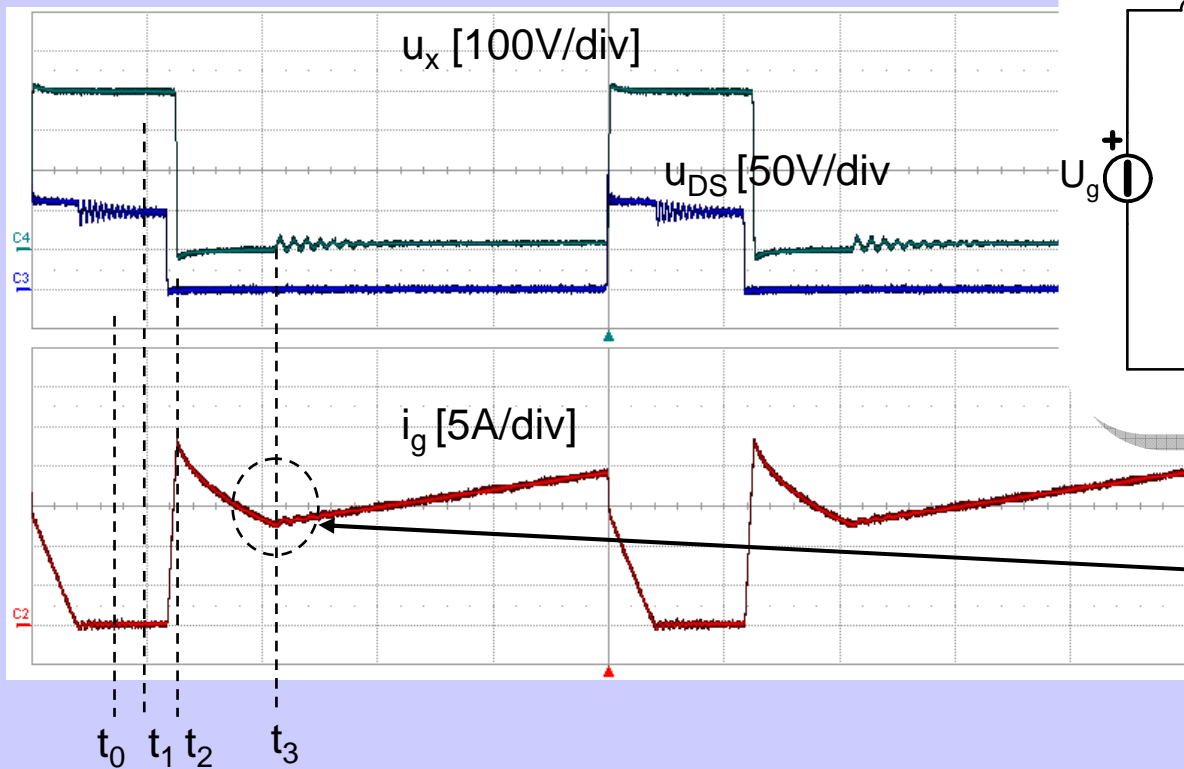
# Experimental Results

$$U_g = 25 \text{ V}, U_o = 400 \text{ V}, P_o = 300 \text{ W}$$




$D_3$  turns off during the switch on interval




# Measured Efficiency

$P_o = 200 \text{ W}$

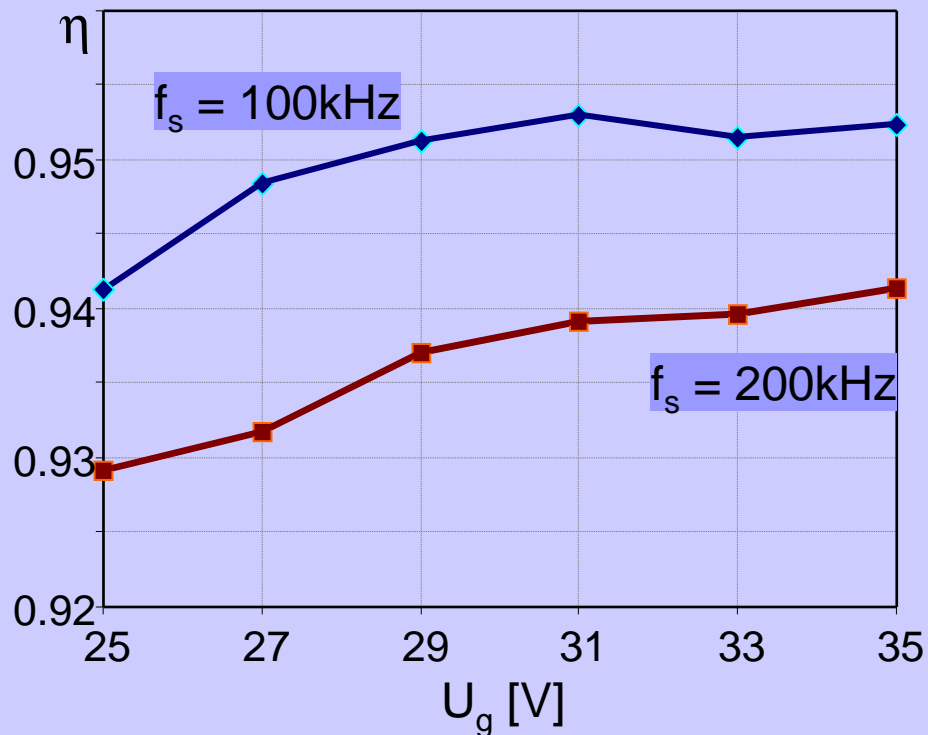


$P_o = 300 \text{ W}$

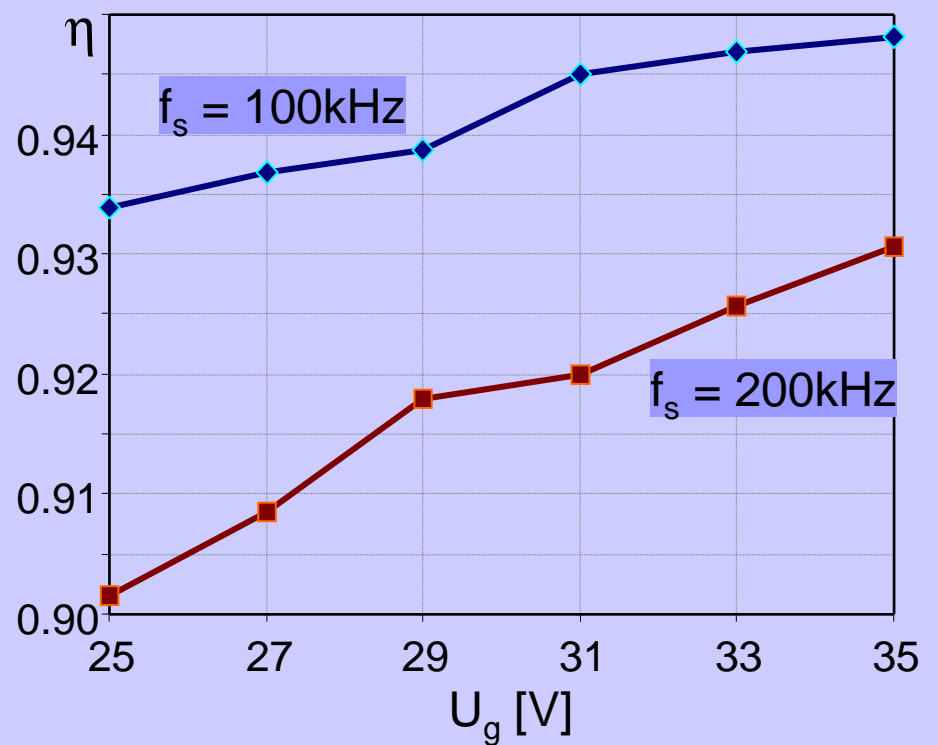




# Measured Efficiency

$f_s = 100 \text{ kHz}$

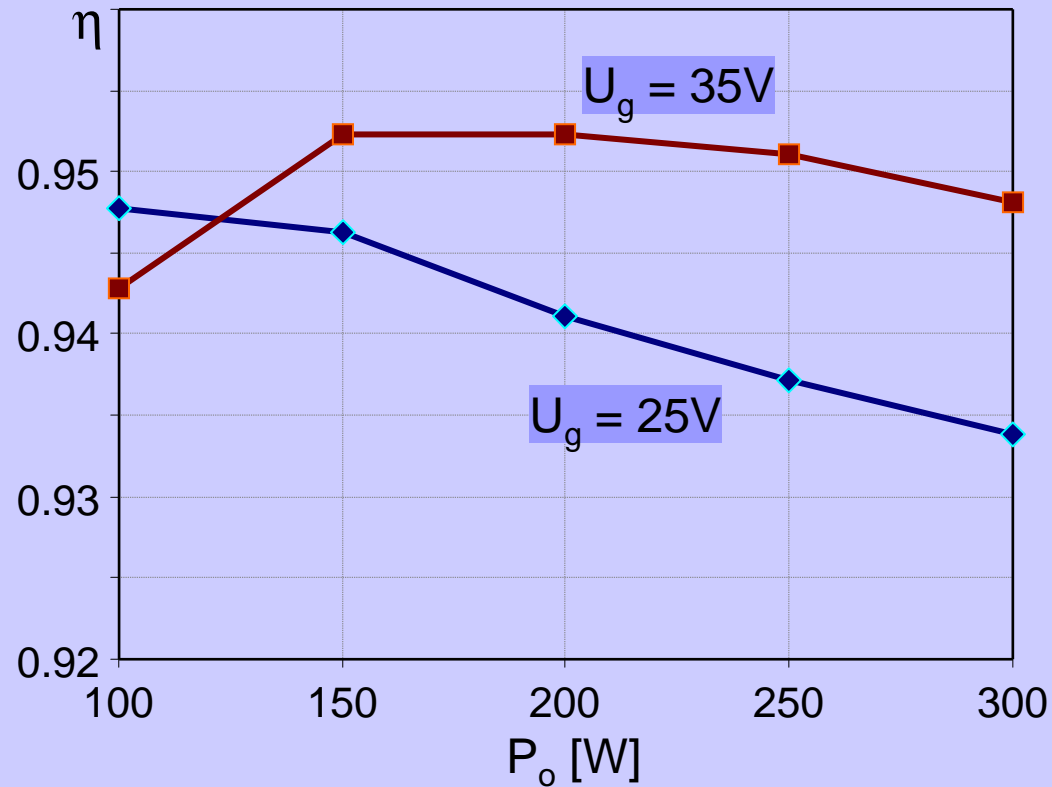



# IBF Converter with Voltage Multiplier

Voltage multiplier cell

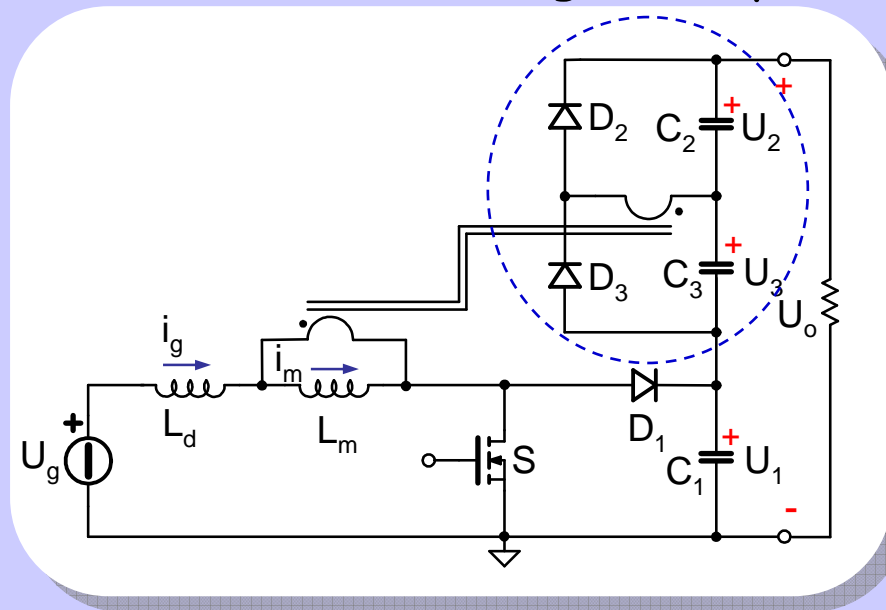
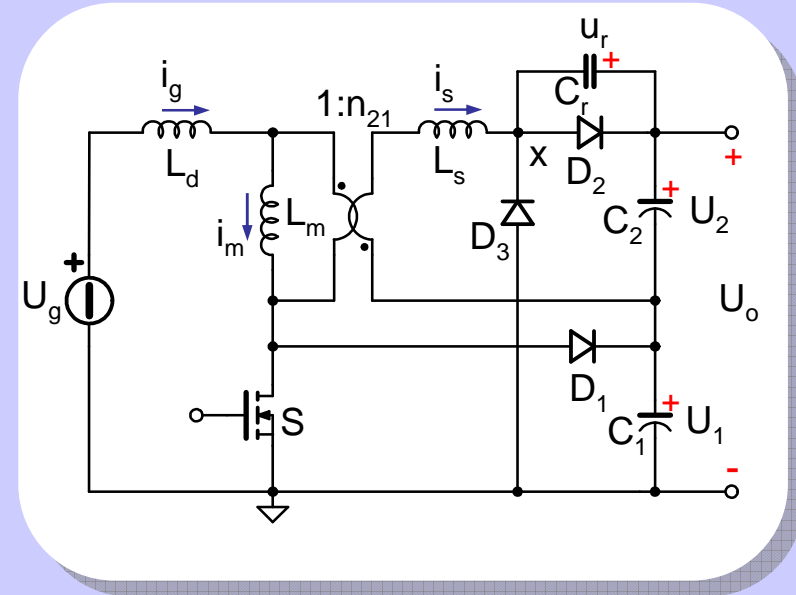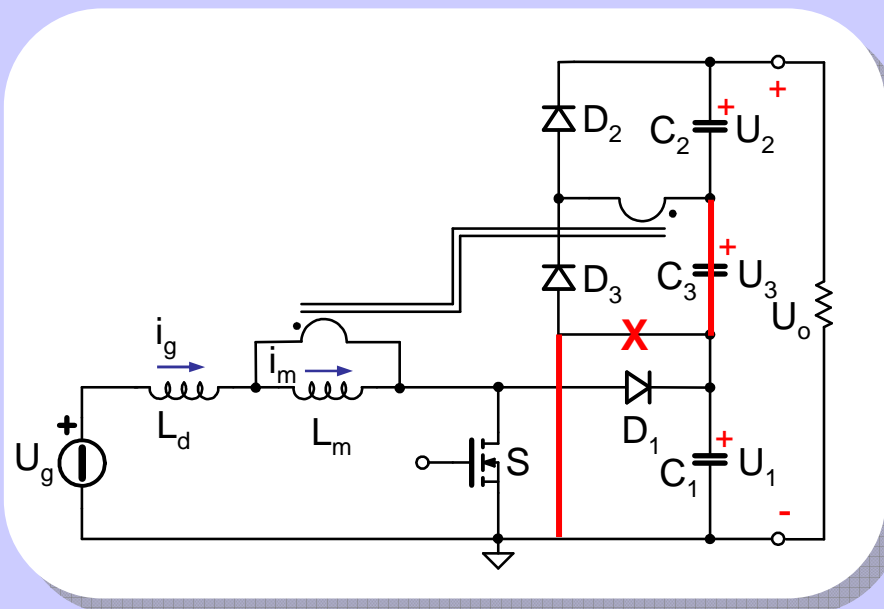
# IBF Converter with Voltage Multiplier



IBF converter with voltage multiplier cell  
versus modified IBF



Similar behavior with a **higher degree of freedom**  
in controlling the switch voltage stress
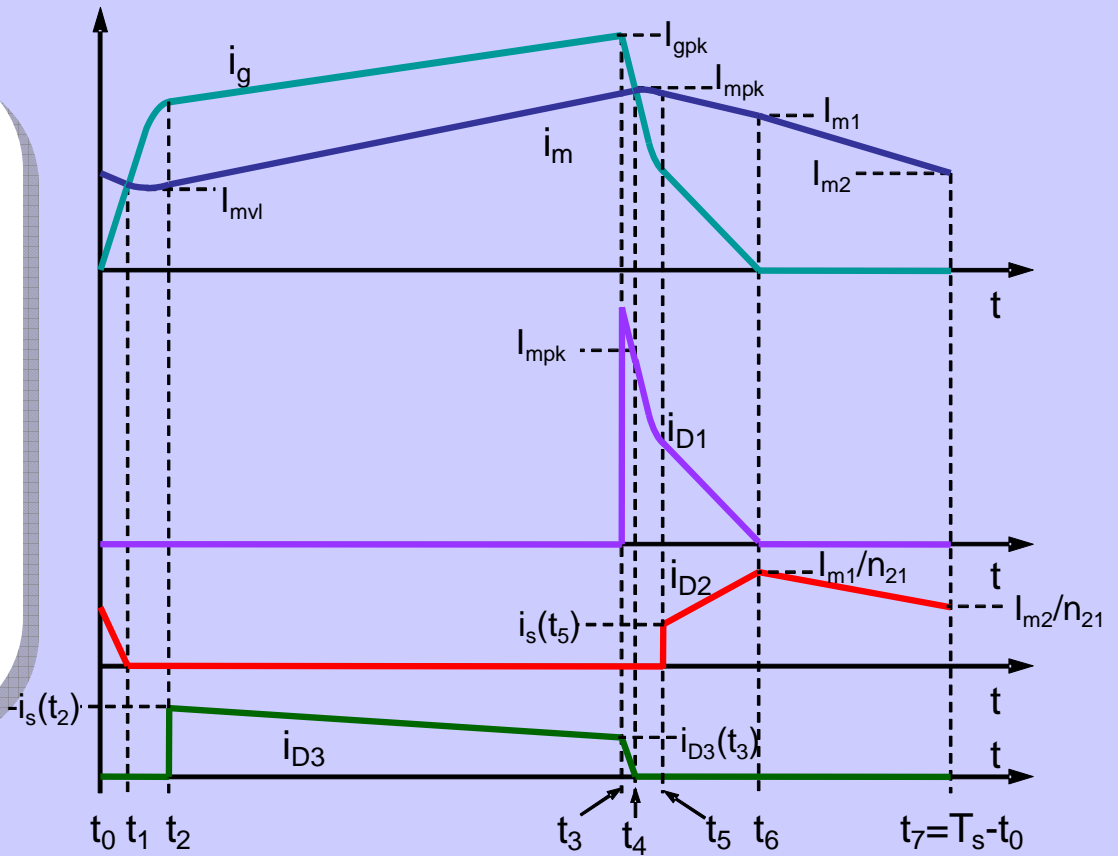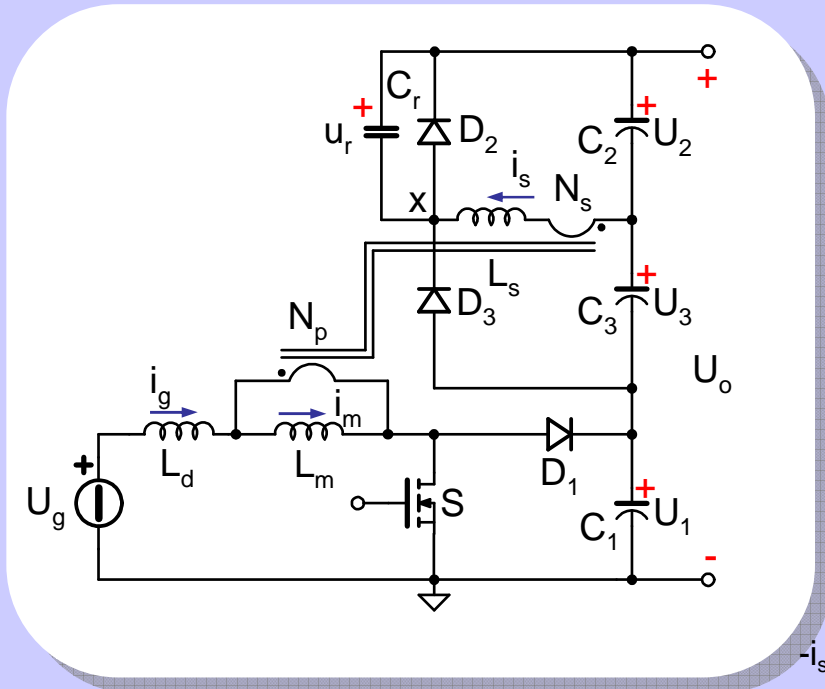
# Converter Waveforms

BOOST section in DCM and FLYBACK section in CCM



# Experimental Prototype

## Design example:

Input voltage:

$$U_g = 25 \div 35V$$

Output voltage:

$$U_o = 400V$$

Nominal output power:

$$P_o = 300W$$

Switching frequency:

$$f_s = 100kHz$$

Boost output:  $\longrightarrow$  150V rated mosfet

$$U_1 = 75V$$

Magnetizing inductance:

$$L_m = 20\mu H$$

Primary leakage inductance:

$$L_d = 0.4\mu H$$

Secondary leakage inductance:

$$L_s = 2\mu H$$

Based on desired current ripple and DCM-CCM mode at nominal power

From the design constraints:

$$M = U_o / U_g = 400/35 = 11.42$$


$$M_1 = U_1 / U_g = 75/35 = 2.143$$

Numerically solving:


$$d = 0.519, n_{21} = 4.589$$

$$M_2 = U_2 / U_g = 4.823$$

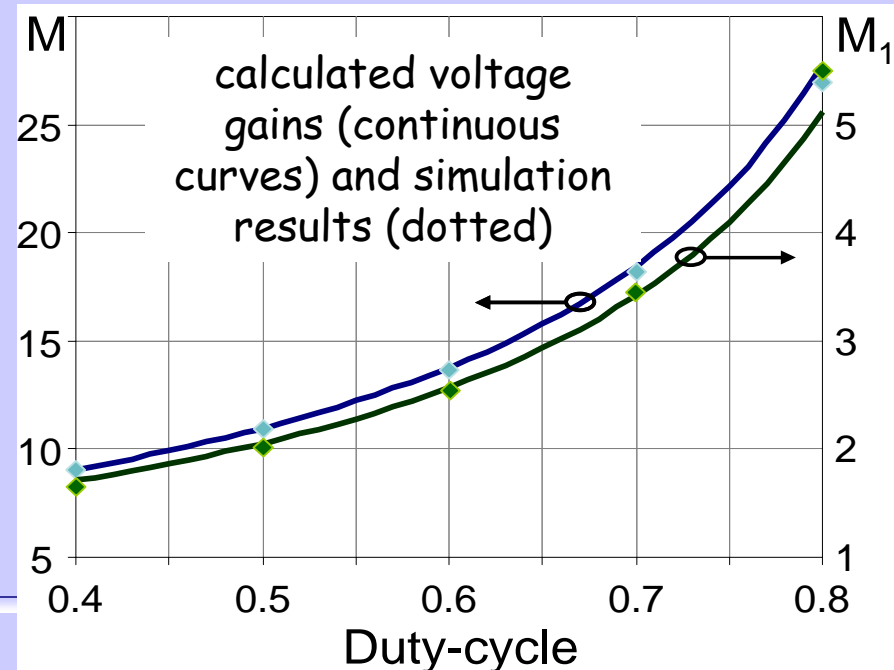
$$M_3 = M - M_1 - M_2 = U_3 / U_g = 4.454$$





# Experimental results

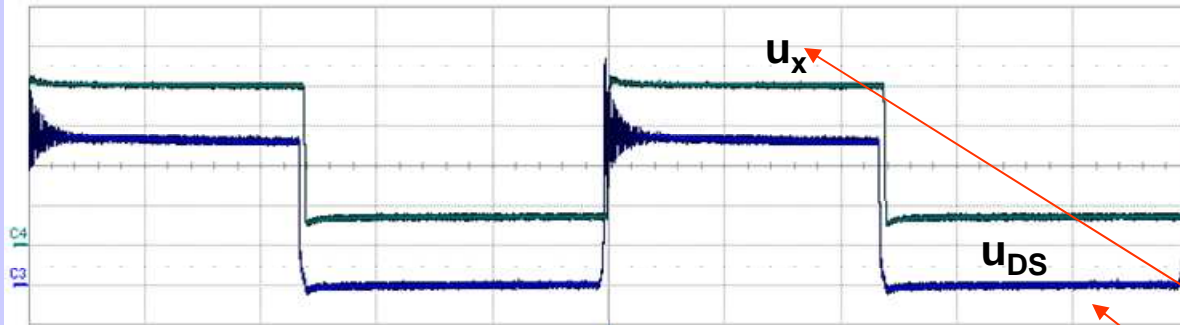

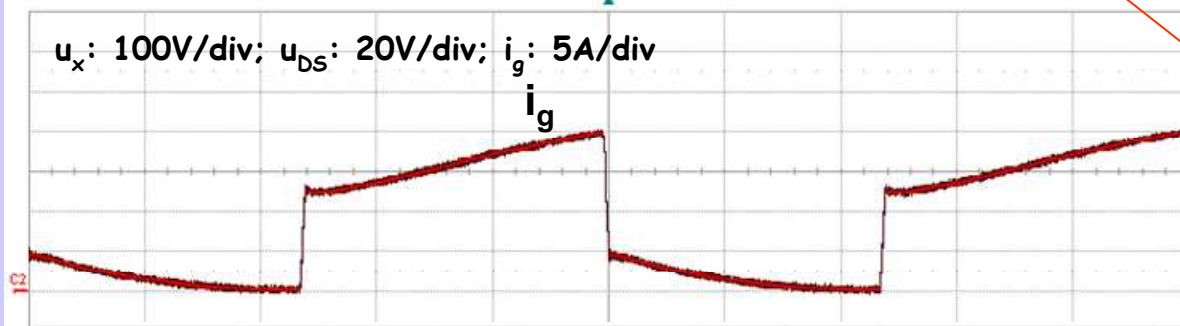Measured main waveforms in a switching period  
 $U_g = 35V$ ,  $V_o = 400V$ ,  
 $P_o = 300W$



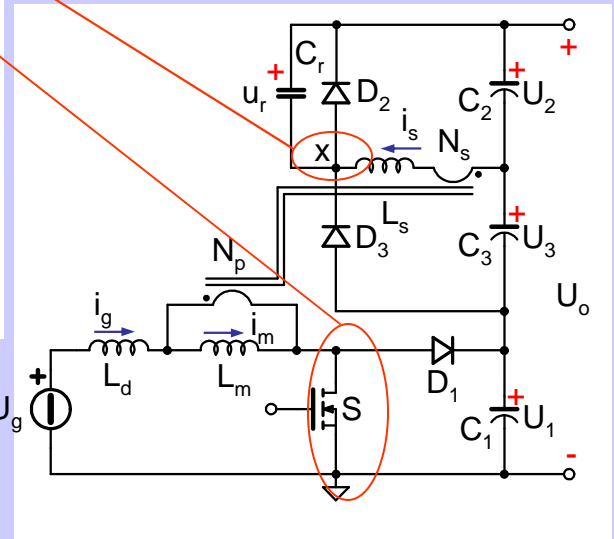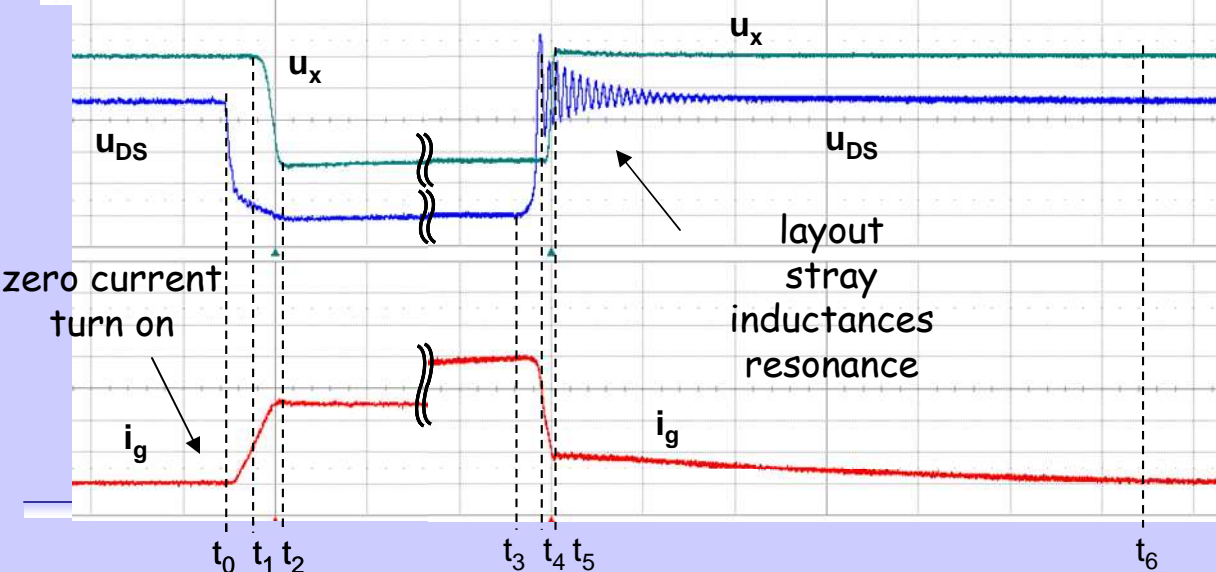$u_x: 100V/div$ ;  $u_{DS}: 20V/div$ ;  $i_g: 5A/div$



Details of turn on and turn off intervals



# Converter efficiency

The converter efficiency was measured as a function of input voltage, at  $P_o=300\text{W}$ , Fig.1, and at  $U_g=[25\text{V},35\text{V}]$  and variable output power, Fig. 2

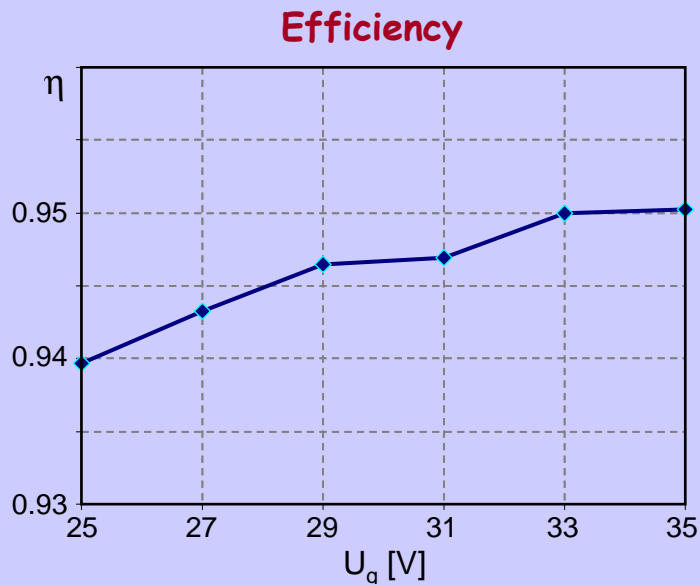


Fig.1


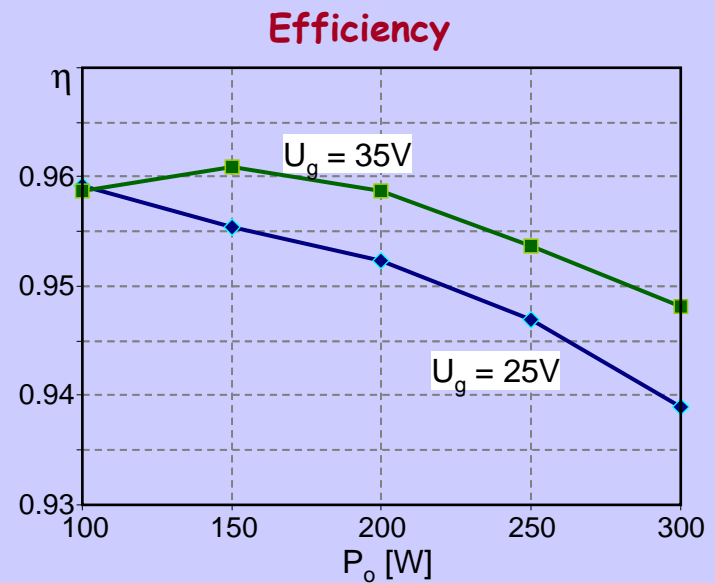



Fig.2

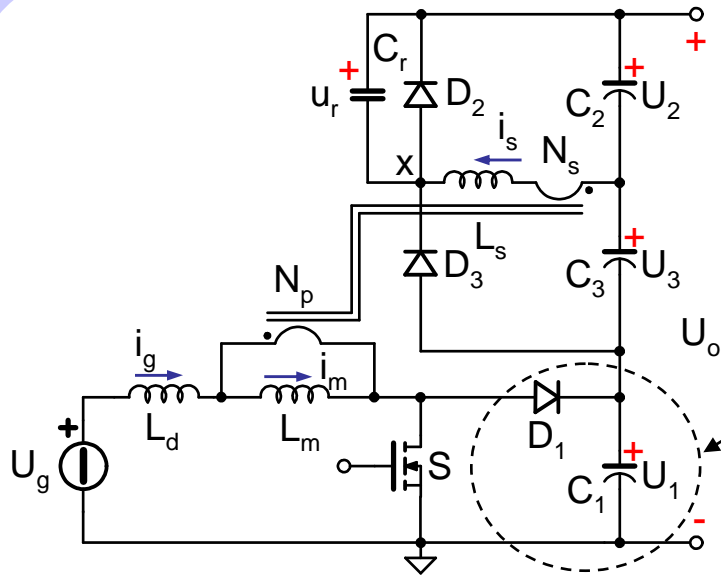
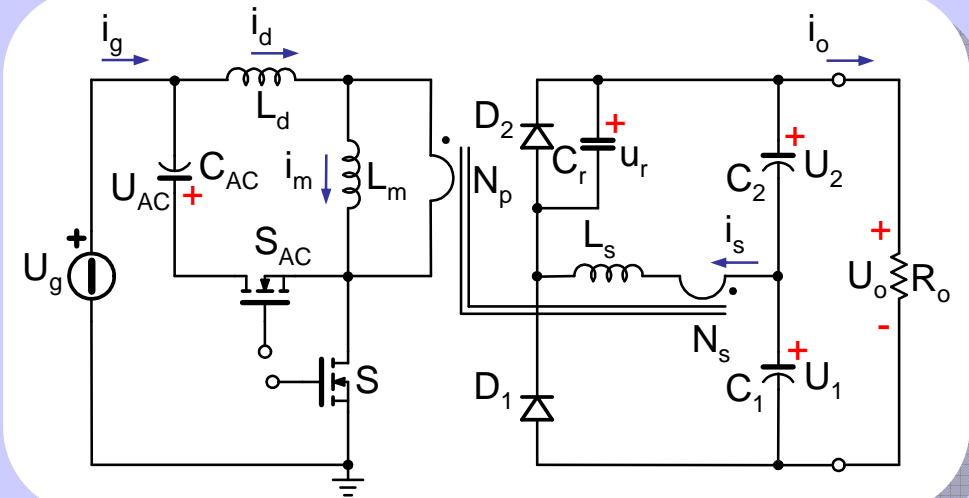
# Isolated IBF Converter



For **isolation**, the lossless snubber  $D_1$ - $C_1$  is substituted by an **active clamp**





# Isolated IBF Converter

---



## Advantages:

- ZVS turn on
- Soft diode turn off
- Reduces switch voltage stress
- Clean diode voltage waveforms without parasitic oscillations
- Energy transfer toward the output also during switch turn on interval
- Reduced active clamp circulating current

# Converter Operation

Hp: negligible capacitor voltage ripples

Interval  $T_{01} = t_1 - t_0$

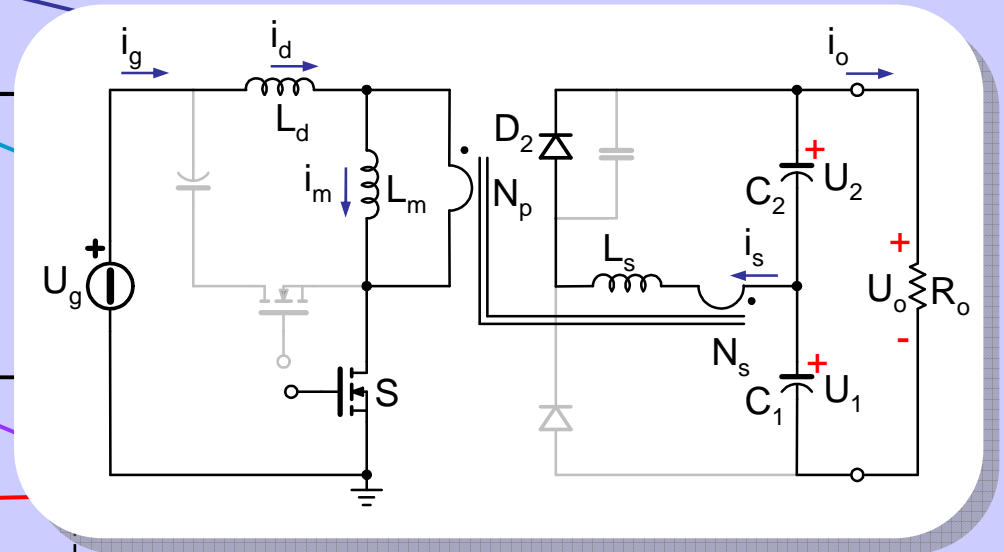
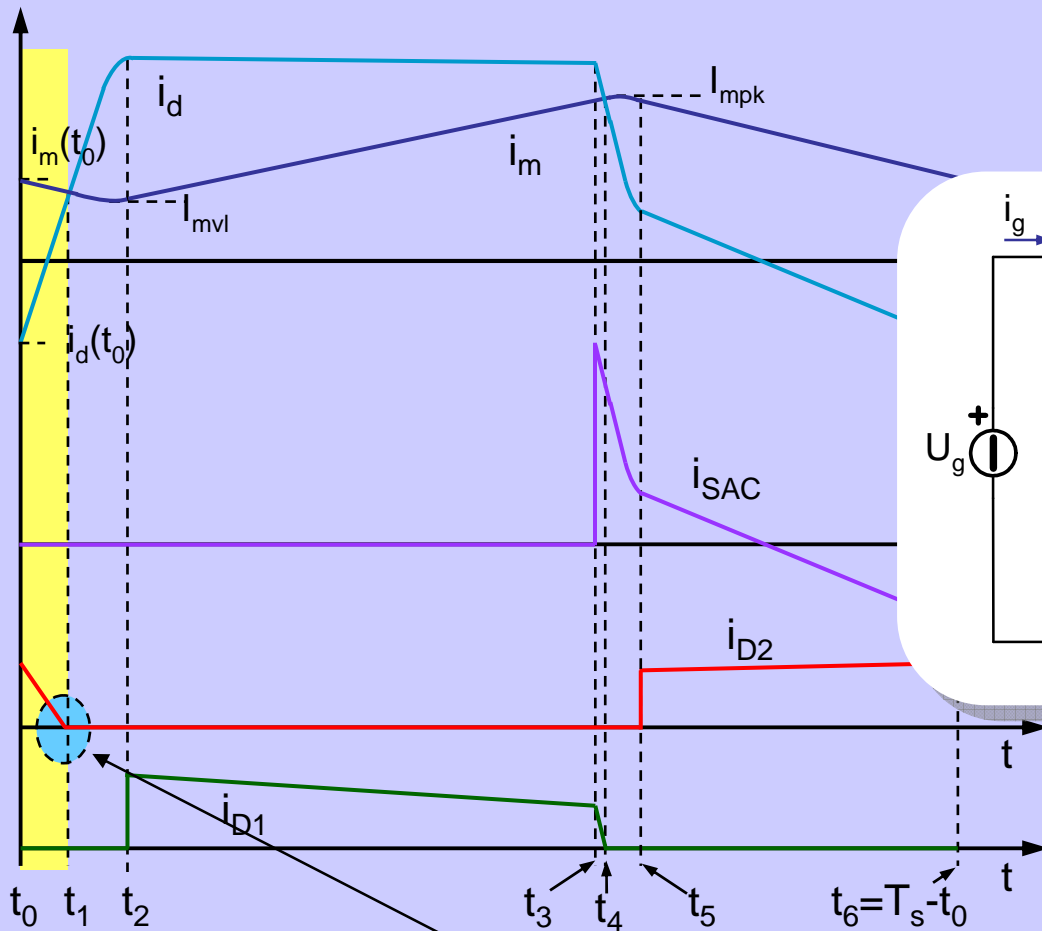


Soft  $D_2$  turn off

# Converter Operation

Hp: negligible capacitor voltage ripples



Interval  $T_{12} = t_2 - t_1$

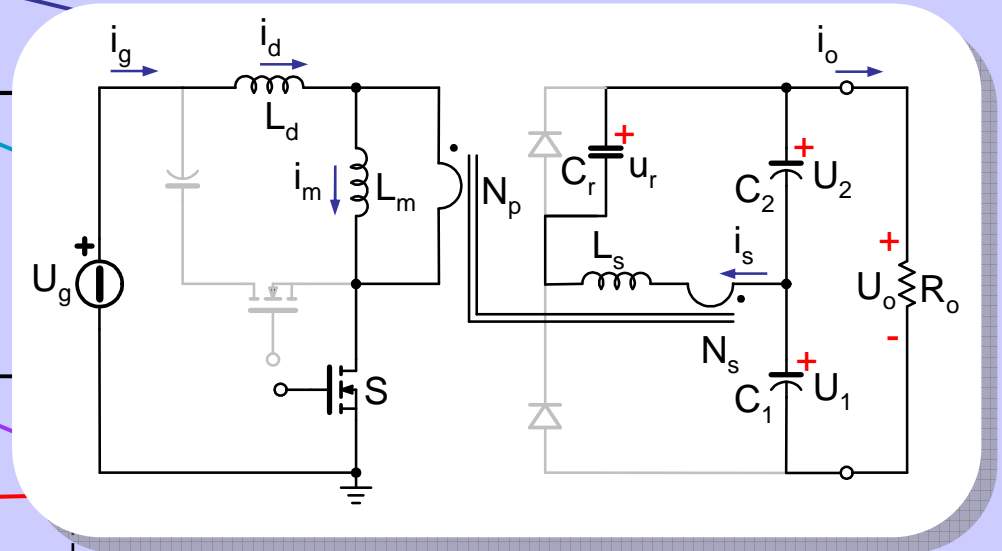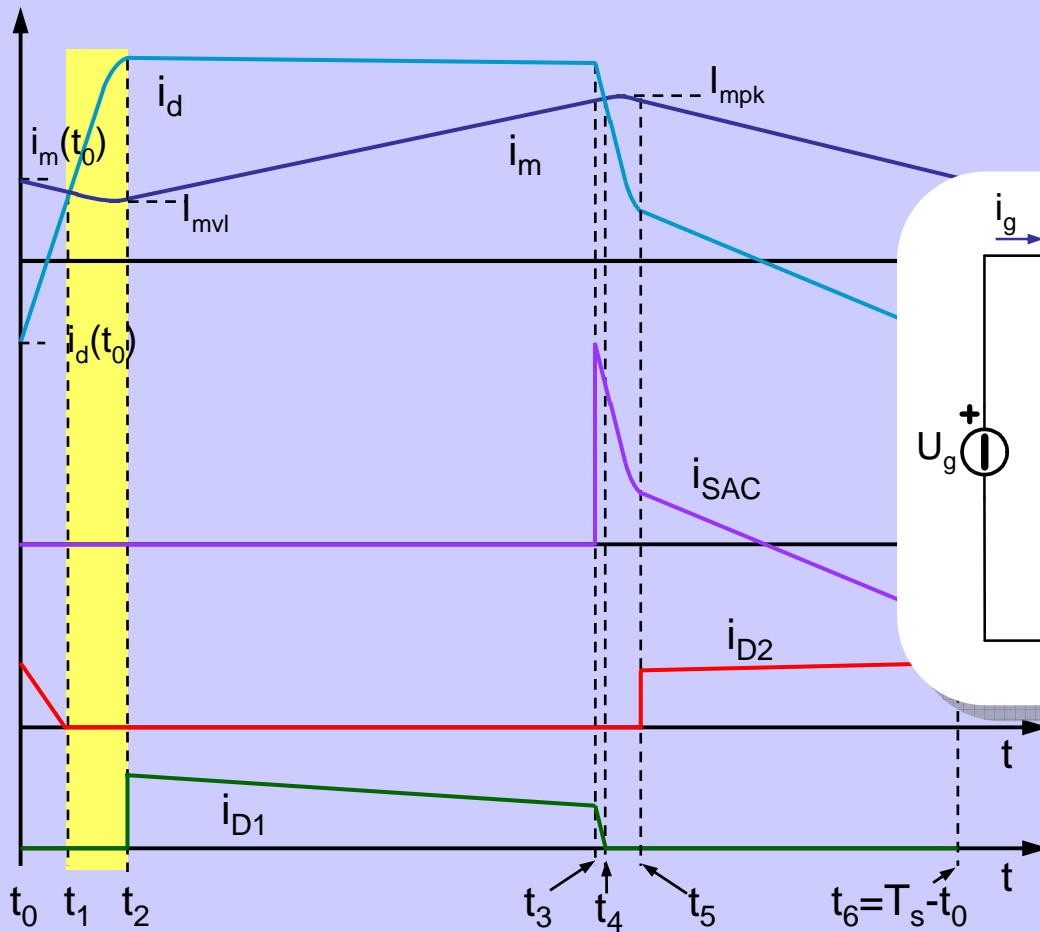

# Converter Operation

Hp: negligible capacitor voltage ripples

Interval  $T_{23} = t_3 - t_2$

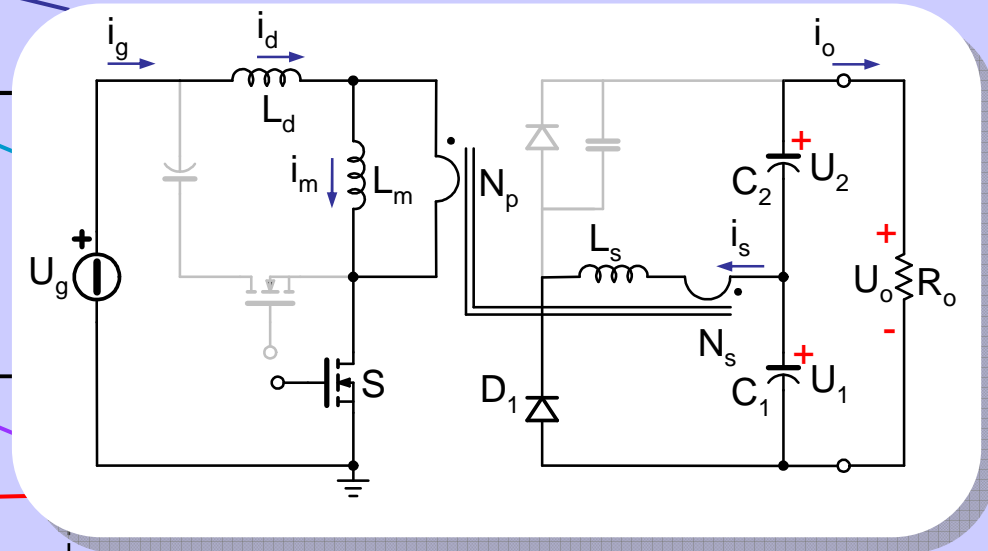
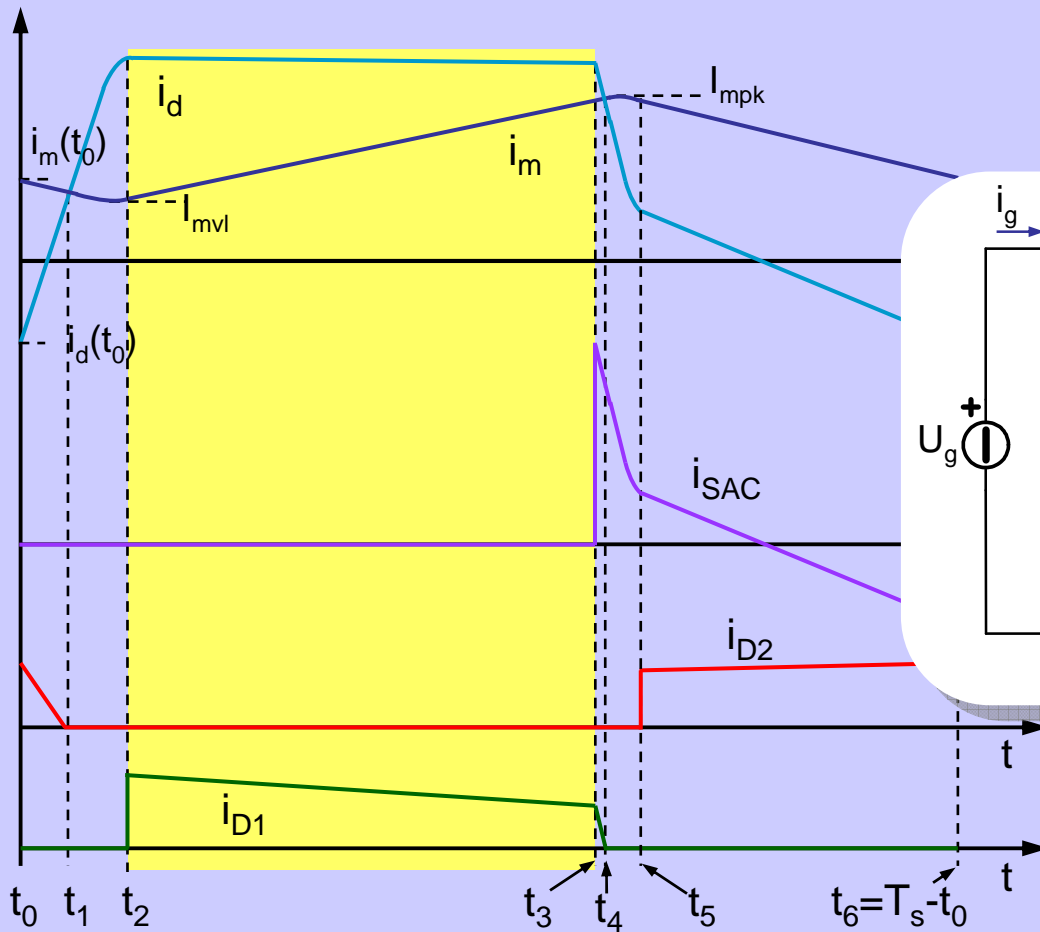


Note: actual  $i_{D1}$  slope can be either positive or negative

# Converter Operation

Hp: negligible capacitor voltage ripples

Interval  $T_{34} = t_4 - t_3$

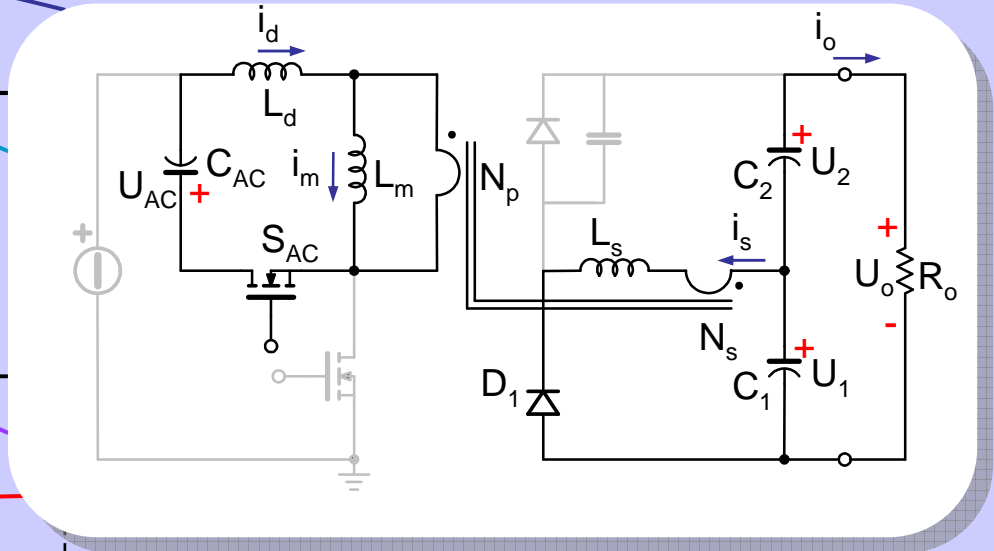
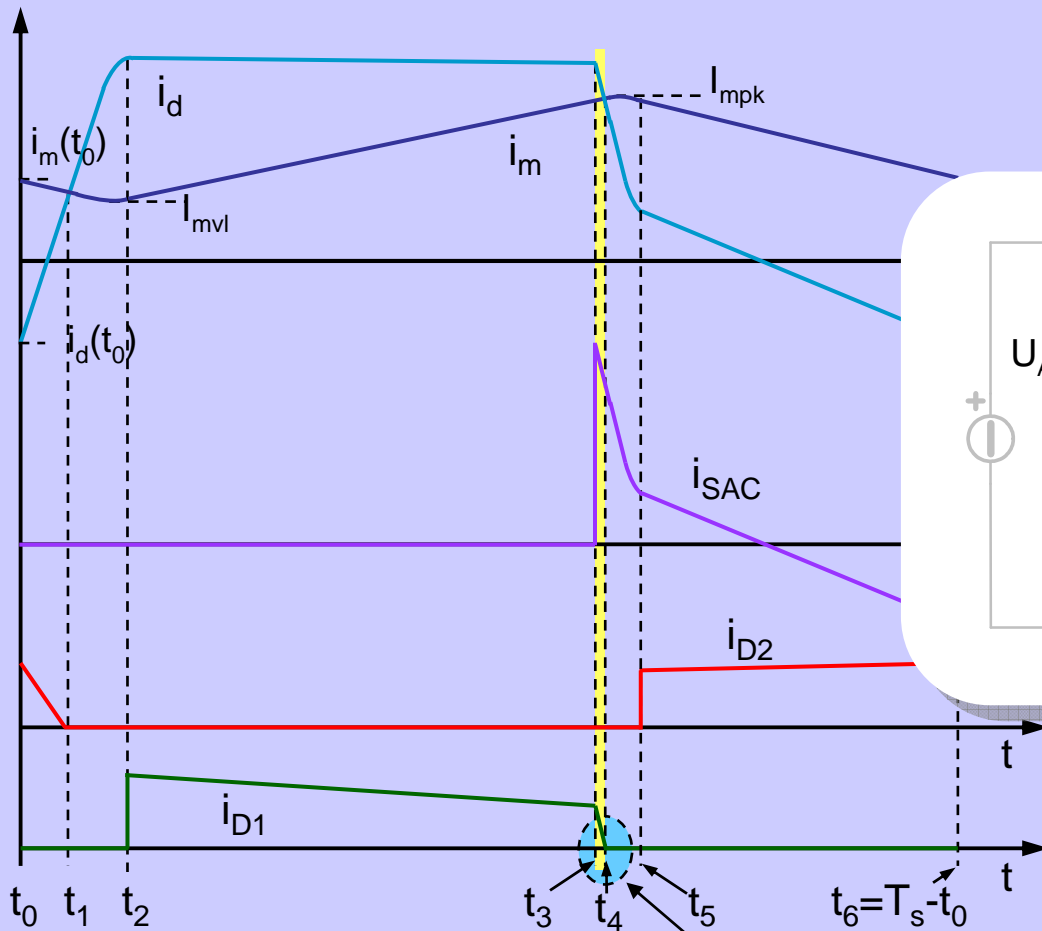


Soft  $D_1$  turn off

# Converter Operation

Hp: negligible capacitor voltage ripples

Interval  $T_{45} = t_5 - t_4$

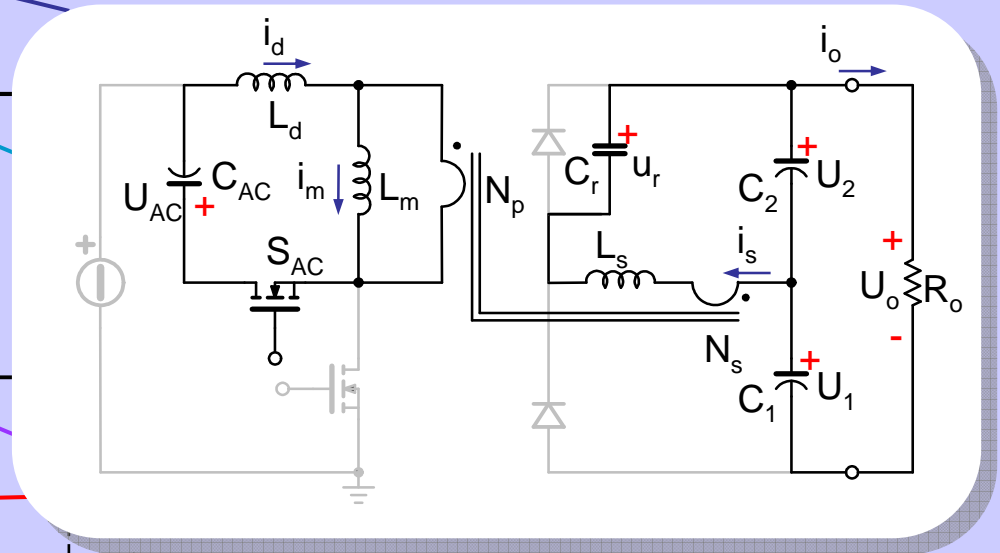
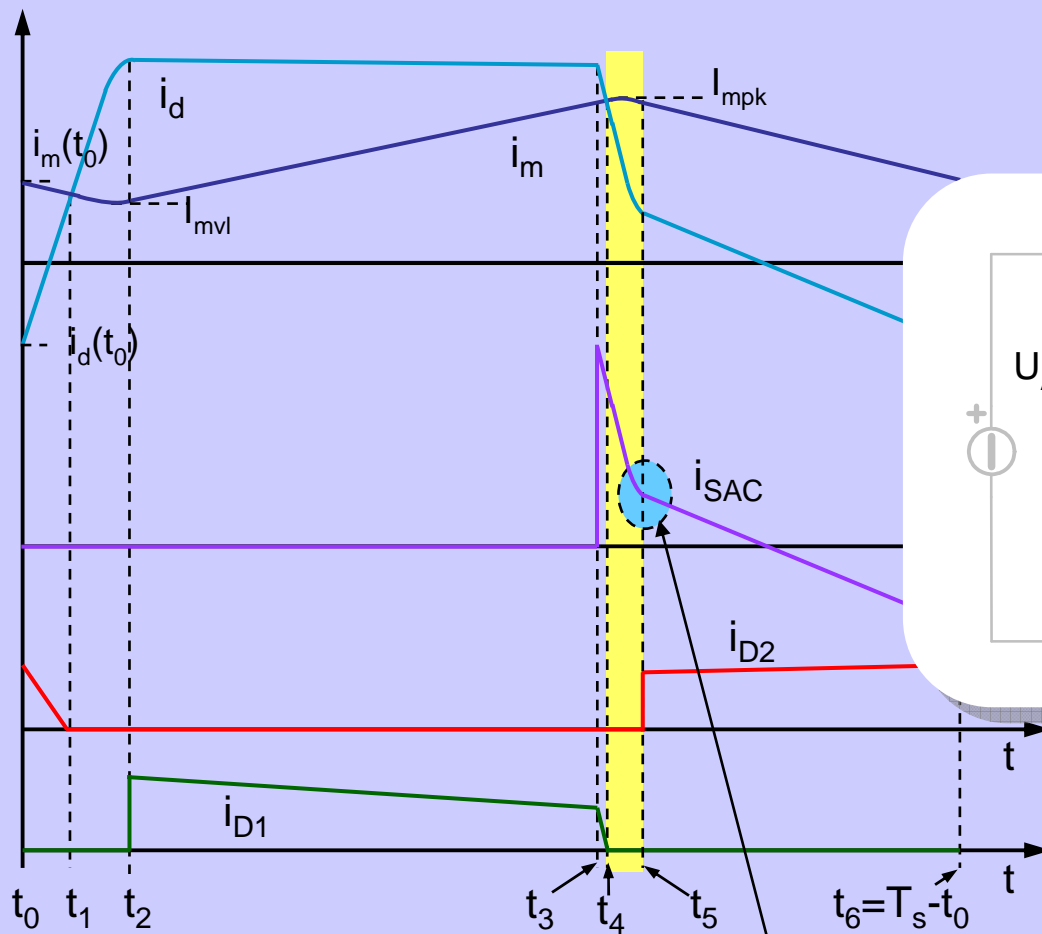


Reduced active clamp circulating current

# Converter Operation

Hp: negligible capacitor voltage ripples

Interval  $T_{56} = t_6 - t_5$

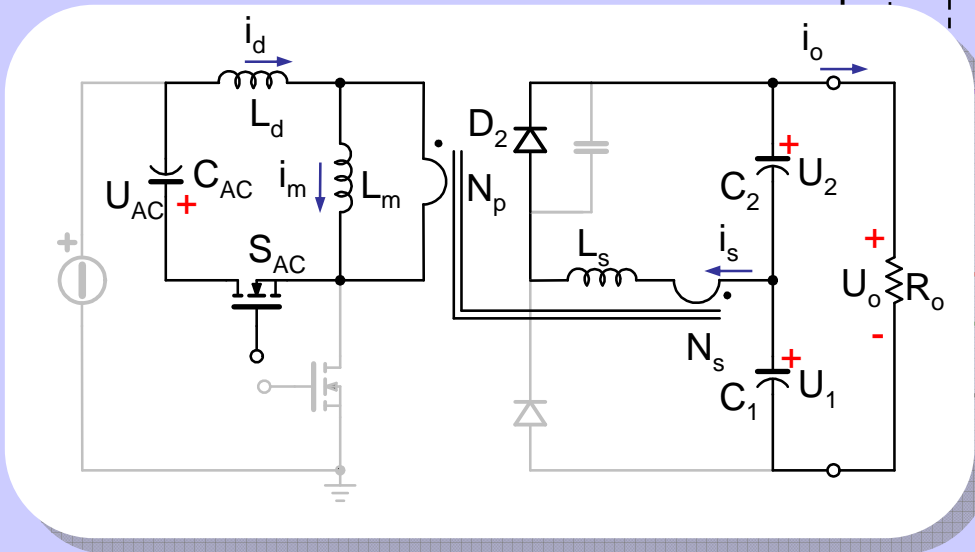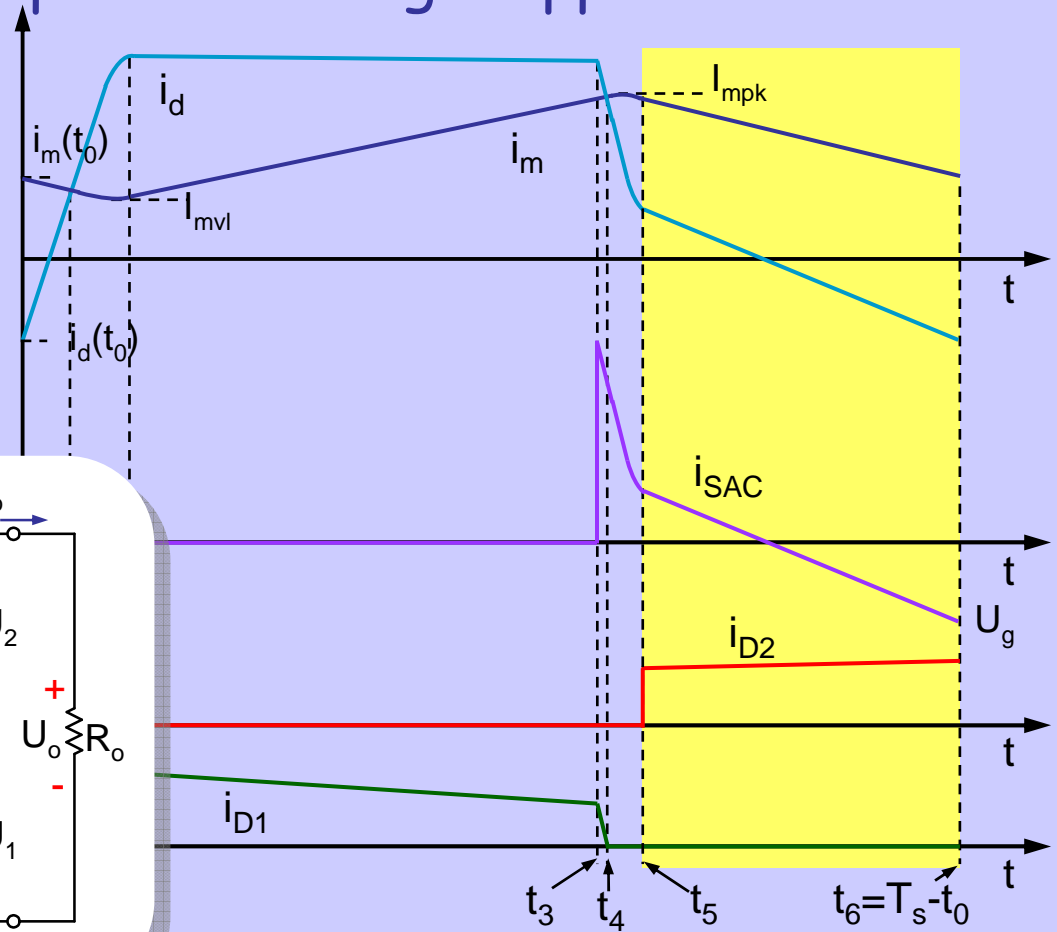






# Converter Parameters

---

- Input voltage:  $U_g = 25-35 \text{ V}$
- Output voltage:  $U_o = 400 \text{ V}$
- Nominal output power:  $P_o = 300 \text{ W}$
- Switching frequency:  $f_s = 100 \text{ kHz}$
- Magnetizing inductance:  $L_m = 20 \mu\text{H}$
- Primary leakage inductance:  $L_d = 0.4 \mu\text{H}$
- Secondary leakage inductance:  $L_s = 2 \mu\text{H}$
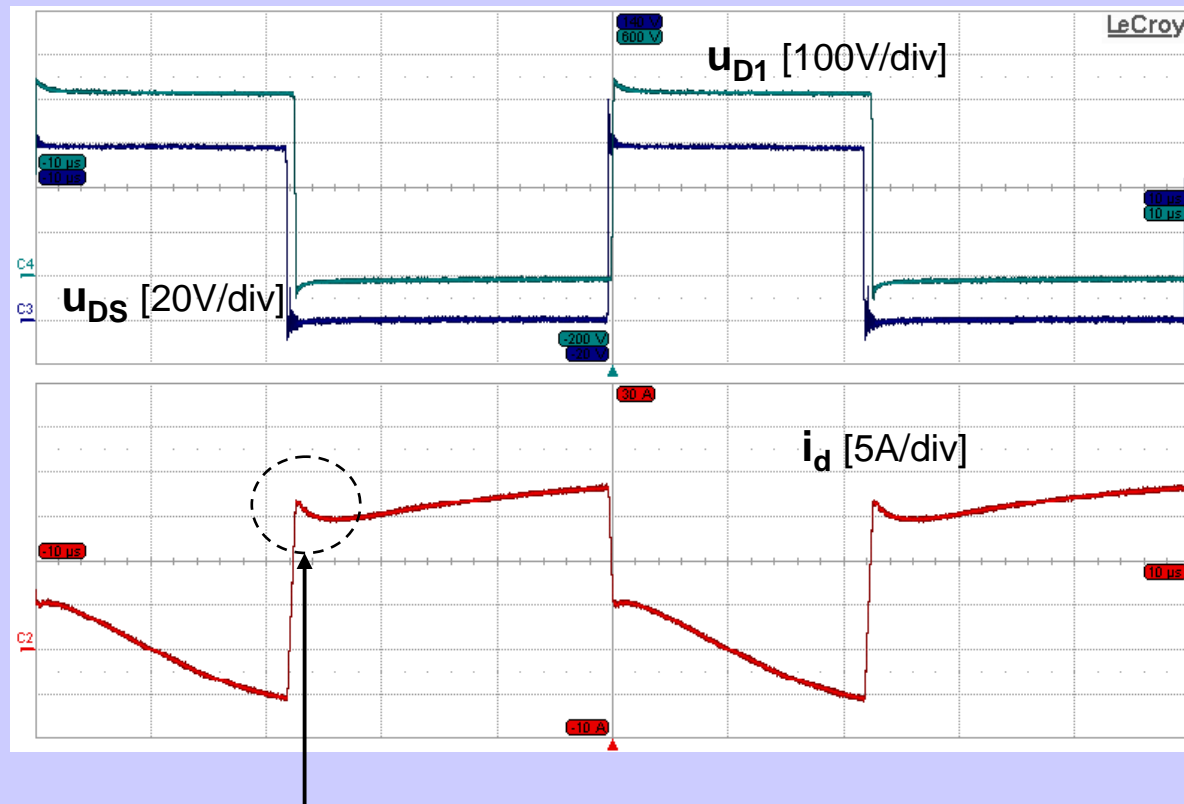
# Experimental Results


$$U_g = 35 \text{ V}, U_o = 400 \text{ V}, P_o = 300 \text{ W} (2\mu\text{s}/\text{div})$$



Peaking due to a small dip in the converter input voltage due to the fast current rise time

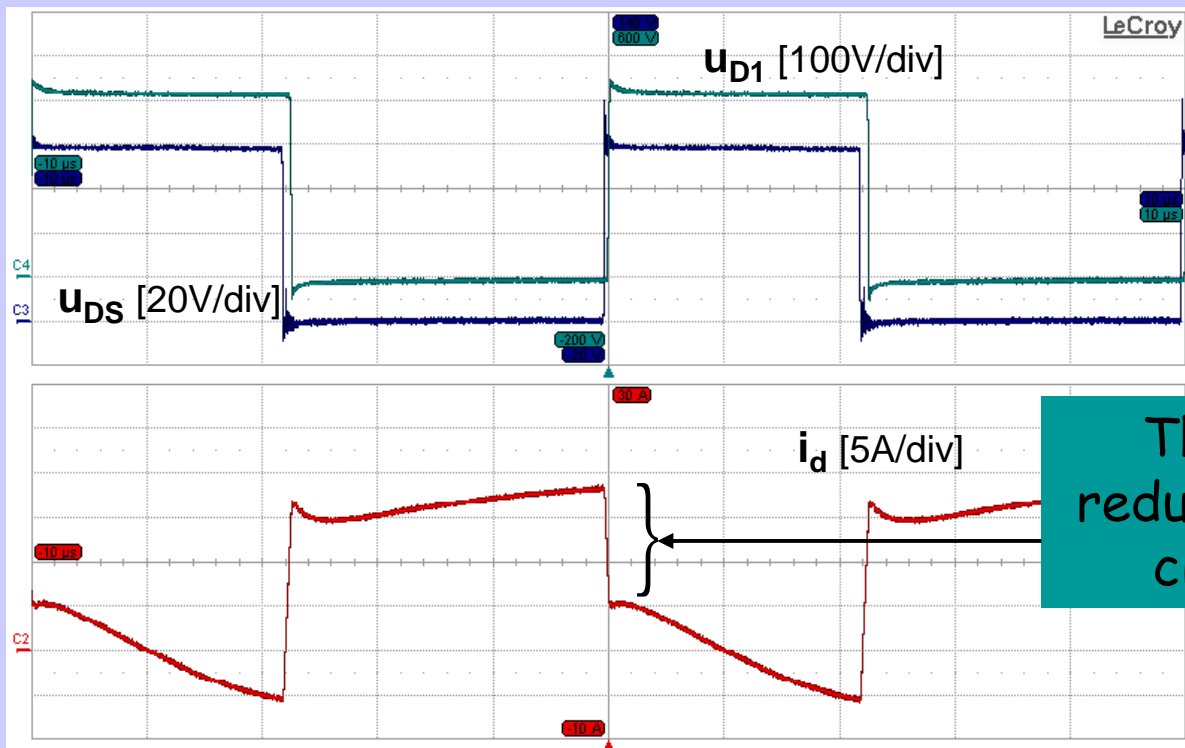
# Experimental Results

$$U_g = 35 \text{ V}, U_o = 400 \text{ V}, P_o = 300 \text{ W} (2\mu\text{s}/\text{div})$$



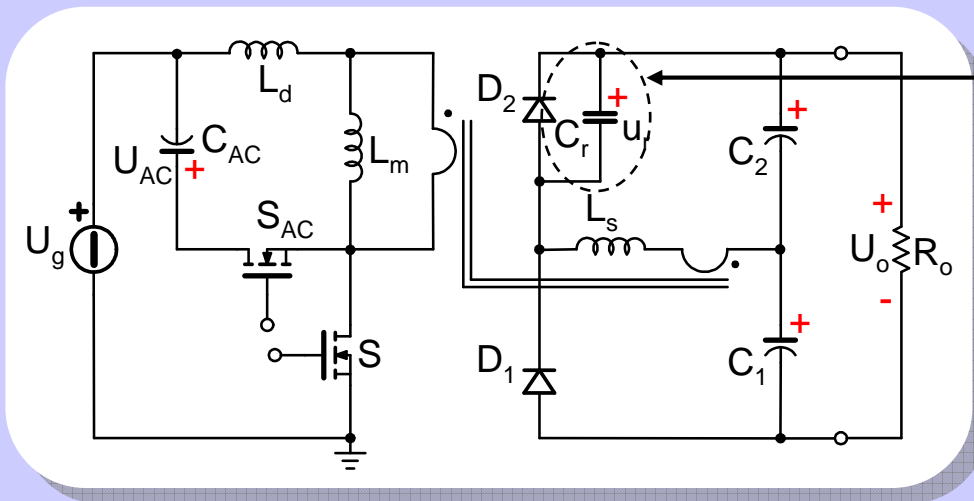
# Experimental Results

$$U_g = 35 \text{ V}, U_o = 400 \text{ V}, P_o = 300 \text{ W} (2\mu\text{s}/\text{div})$$



390 pF external capacitor added

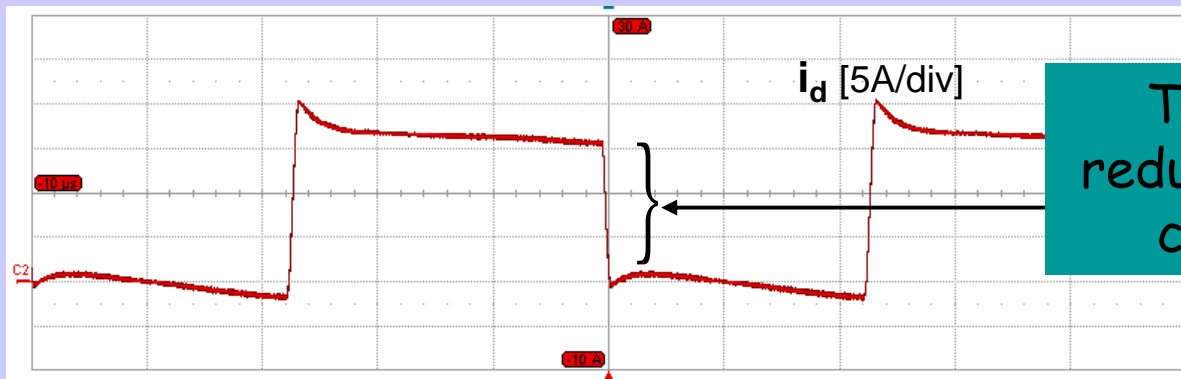


The resonant phase reduces the active clamp circulating current


# Detail of Main Switch Turn On

$$U_g = 35 \text{ V}, U_o = 400 \text{ V},$$

$$P_o = 300 \text{ W}$$

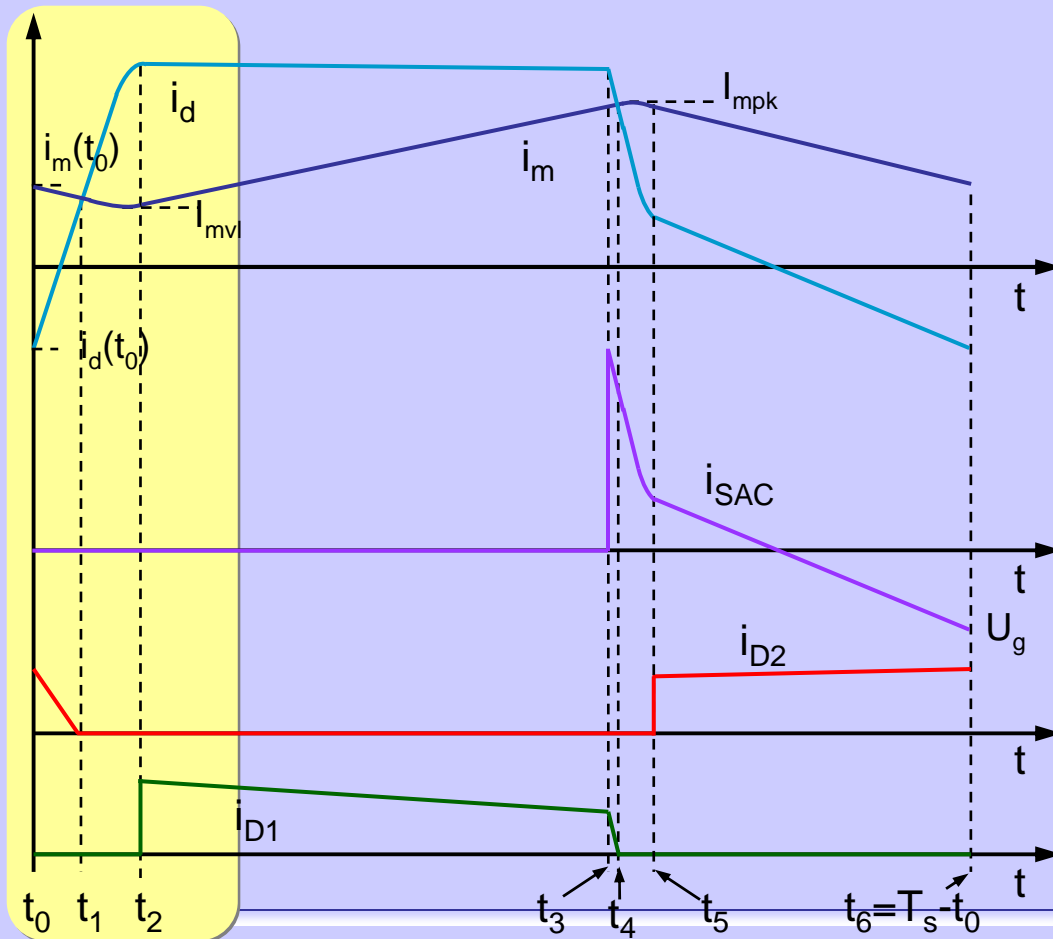


Time scale: 500ns/div

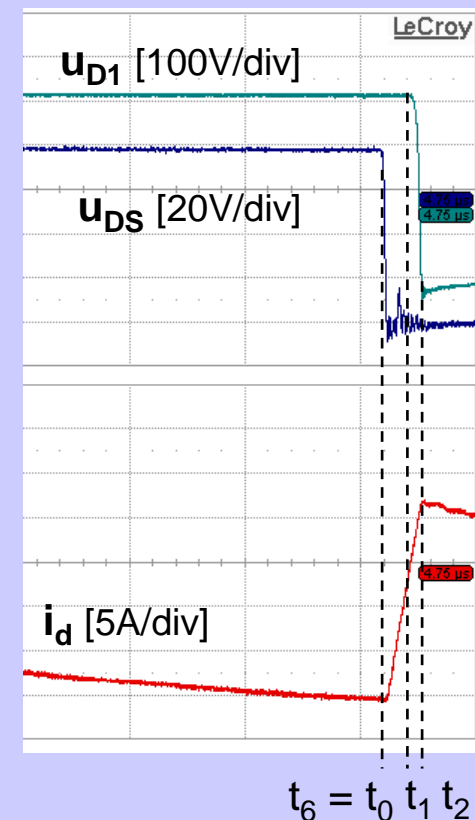


# Detail of Main Switch Turn Off

$$U_g = 35 \text{ V}, U_o = 400 \text{ V},$$

$$P_o = 300 \text{ W}$$

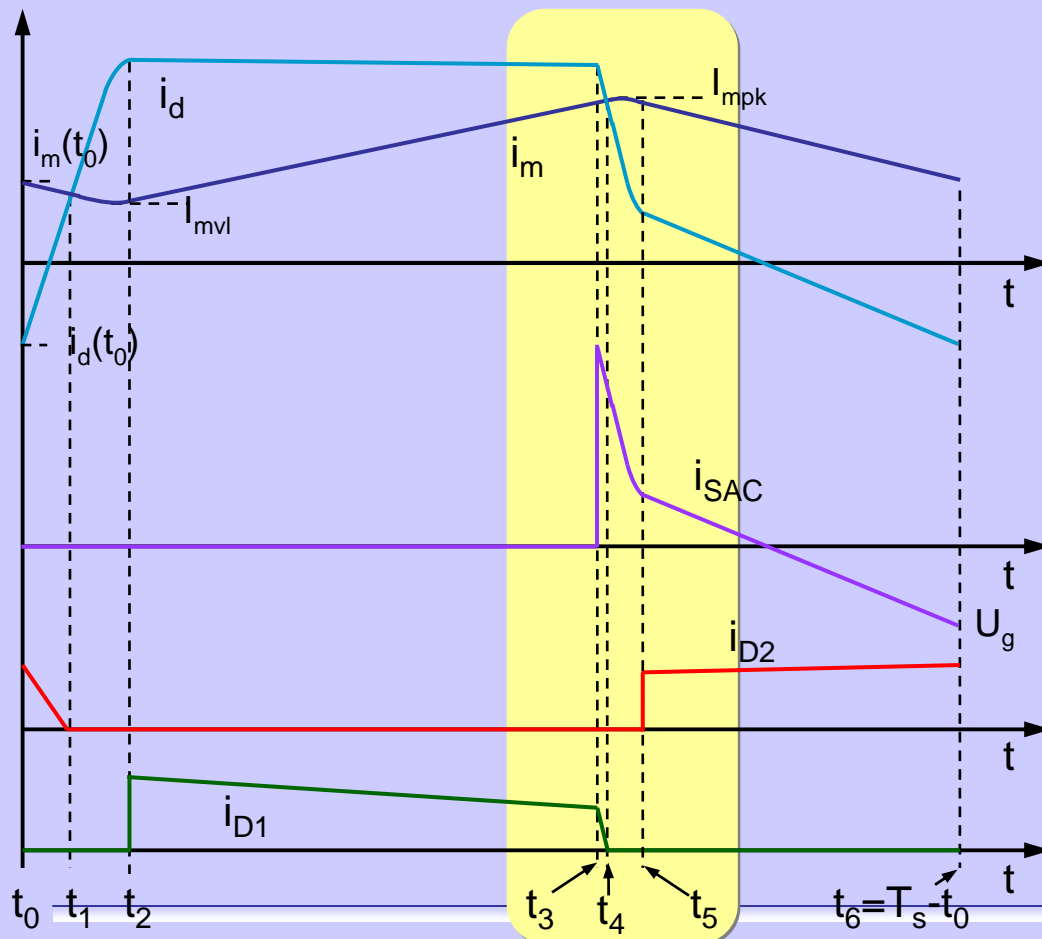


Time scale: 500ns/div

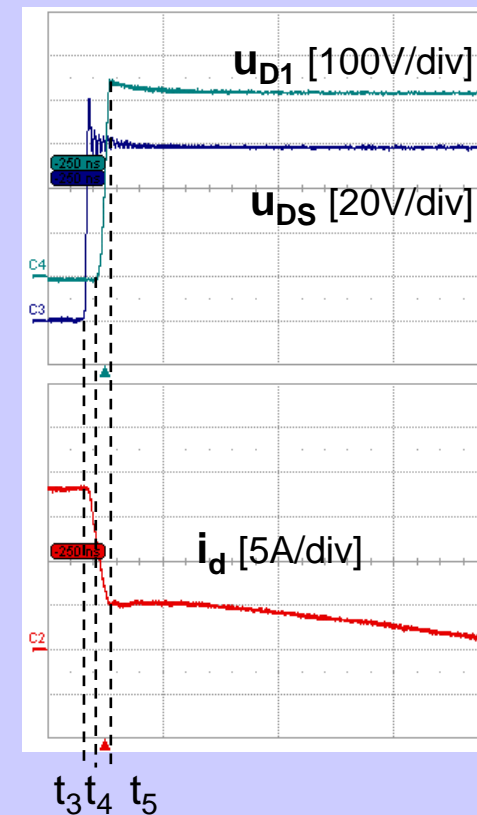


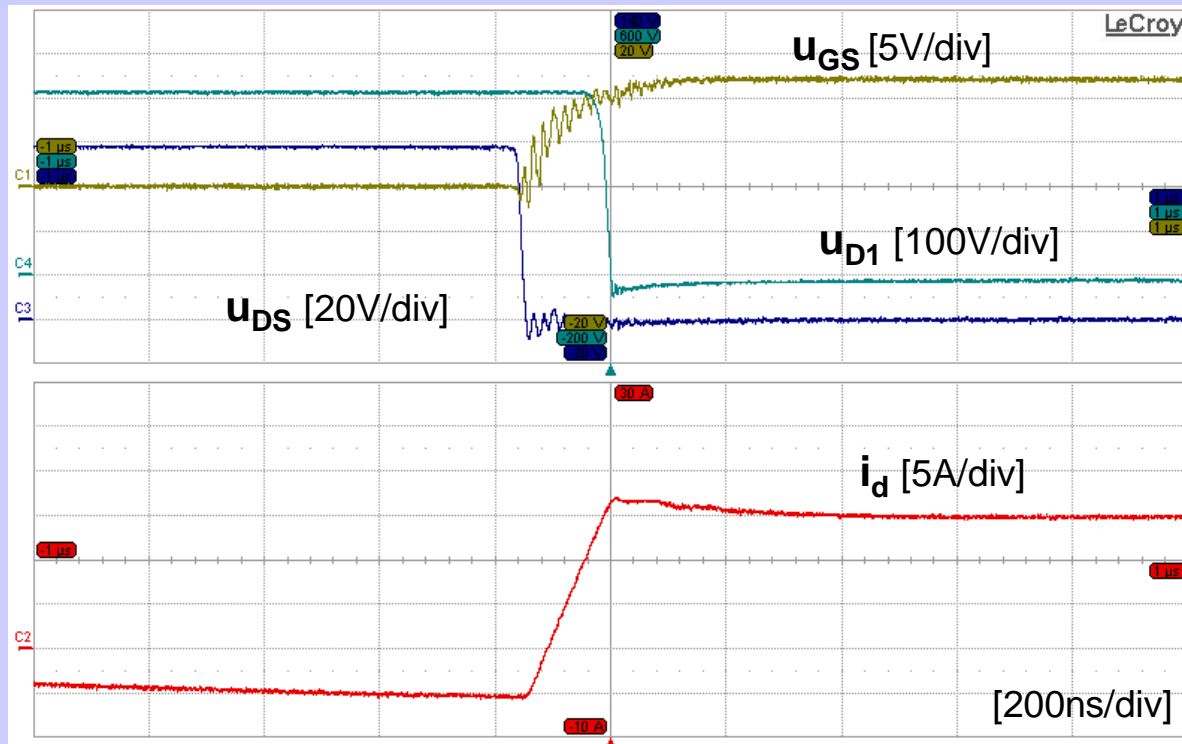
# Zero Voltage Switching

Detail of the main switch turn on  
(nominal output power)


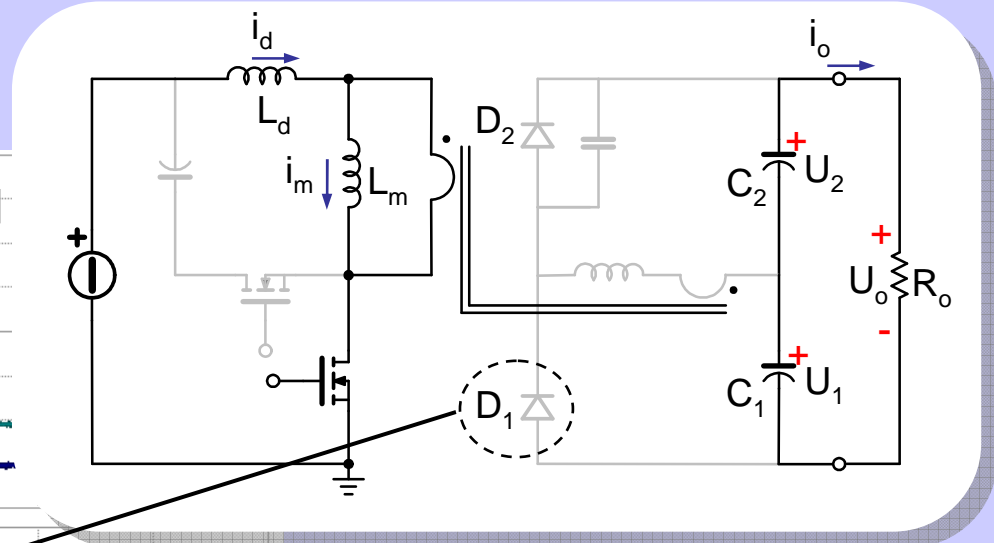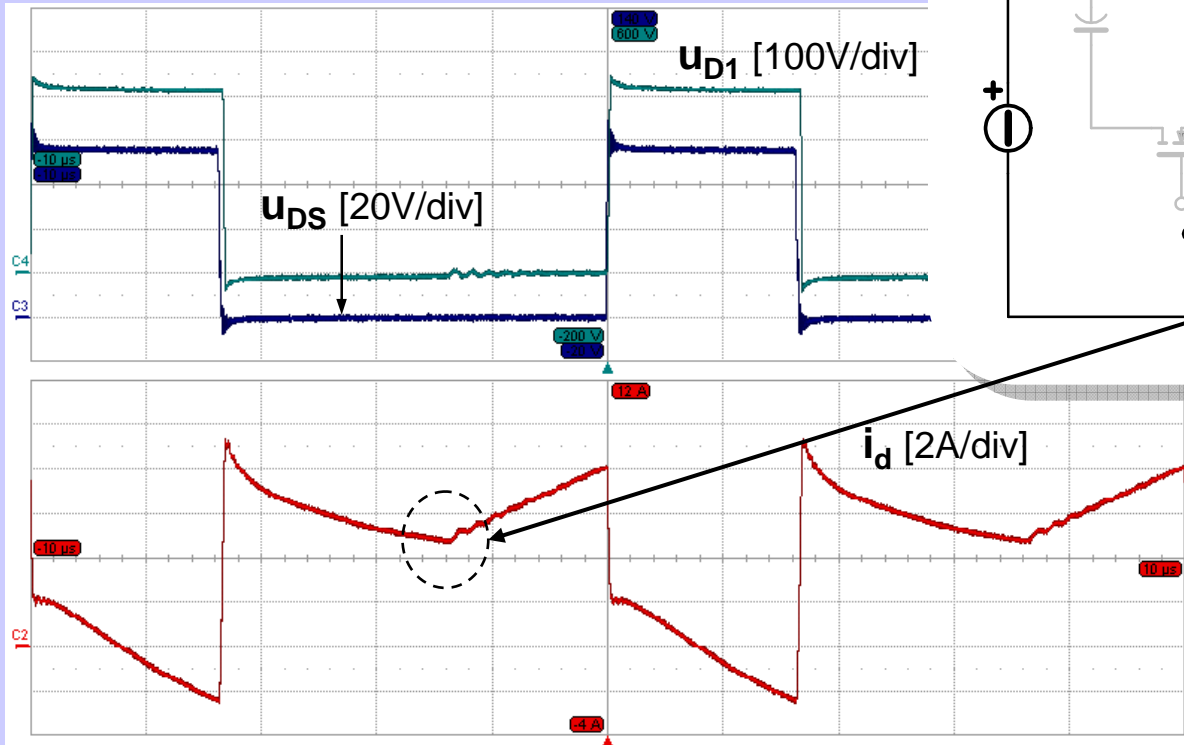
# Different Operating Mode

$$U_g = 25 \text{ V}, U_o = 400 \text{ V}, P_o = 100 \text{ W}$$





$D_1$  turns off during the switch on interval



# Measured Efficiency

Power stage only

$P_o = 300 \text{ W}$

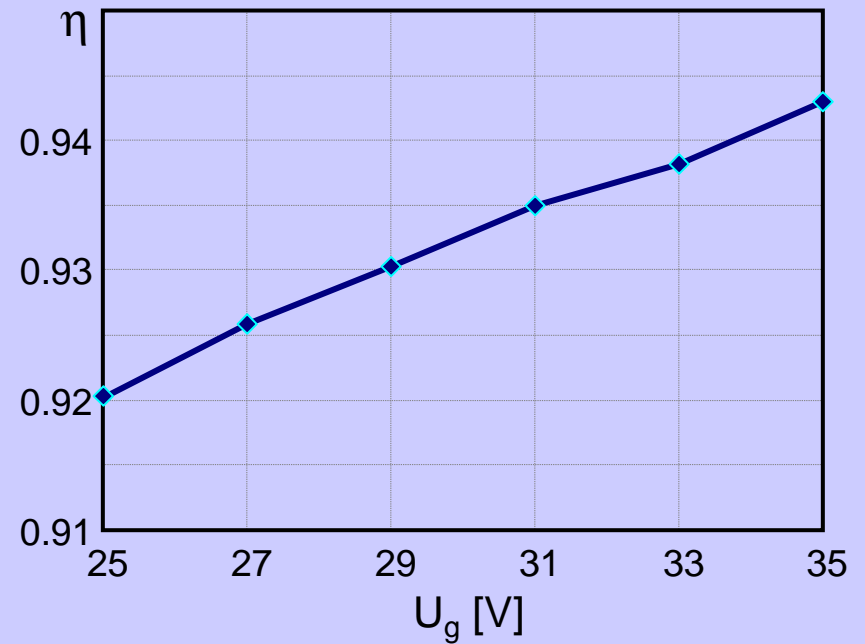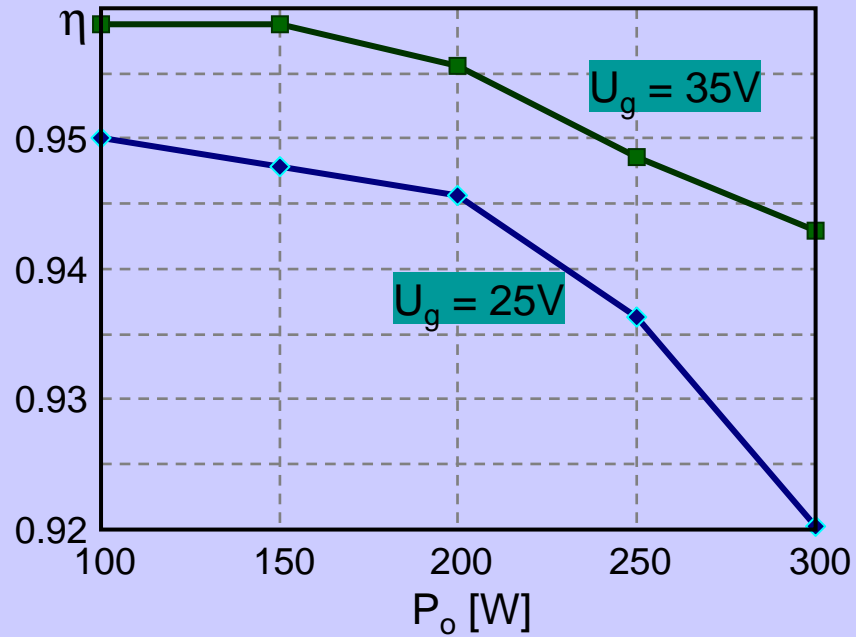

# Comments

---

- There are different topologies presented in literature whose behavior is very similar to the Integrated Boost-Flyback converter.
- These topologies have a drawback of a discontinuous input current waveform, that make the use of such converters for higher power levels at least problematic.
- For high power applications, a continuous input current represents a very nice feature