



Lesson 2

Uninterruptible Power Supply Multi-Loop Control Employing Digital Predictive Voltage and Current Regulators



Goal of the work

Investigation of **digital predictive voltage and current regulators** in **multi-loop configuration** for **UPS's**

Motivations:


- **high dynamic performance (i.e. low THD with distorting loads, low overshoot under step load changes, etc...);**
- **simple control design and implementation**




Presentation outline

- **Control technique derivation:**
 - **current loop**
 - **voltage loop**
- **Design criteria and implementation issues**
- **Simulation results**
- **Experimental results**

UPS system structure and model

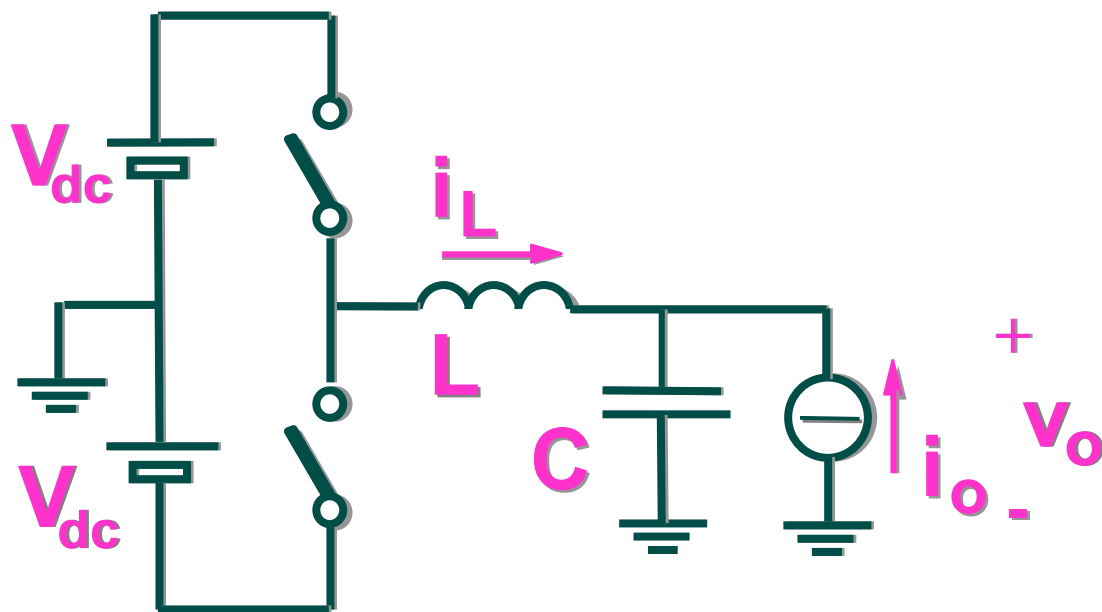

Single-phase scheme

 


Averaged model

Current control loop

The control equation **assumes** that:

$$i_L(k+1) = i_L(k) + \frac{T_s}{L} \cdot [v(k) - v_o(k)] \quad + \text{one sample delay}$$


Simple load model

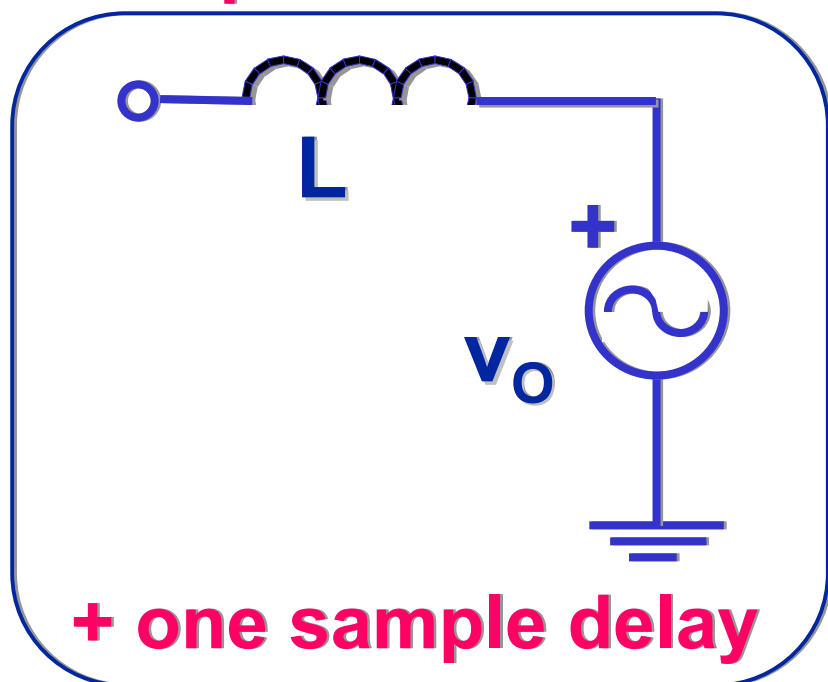

The model works **properly** in the UPS case if the **sampling frequency** is much higher (e.g. 15-20 times) than the **resonance frequency** of the output LC filter.

Current control loop


Review of deadbeat control

 

$$v_m(k+1) = \frac{L}{T_s} [i_L^*(k) - i_L(k)] - v_m(k) + v_o(k) + v_o(k+1)$$

Dead-Beat Current Control Equation (DBCCE)

Current control loop

 

Step response of the closed-loop current control.
Sampling frequency: 15 kHz

Two sample delay

Voltage control loop




- The **same** reasoning used for dead-beat current loop can be applied **also to the voltage loop**.
- A **key point** is to make the **sampling period of the voltage control equal to TWICE the sampling period of the current loop**.
- Thus, the **current closed loop control can be modeled as a simple delay (i.e. a two sampling period delay)**.

Voltage control loop

The control equation **assumes that:**

$$v_o(k+1) = v_o(k) + \frac{2 \cdot T_s}{C} \cdot [i_L(k) - i_o(k)] \quad + \text{one sample delay}$$


Simple load model

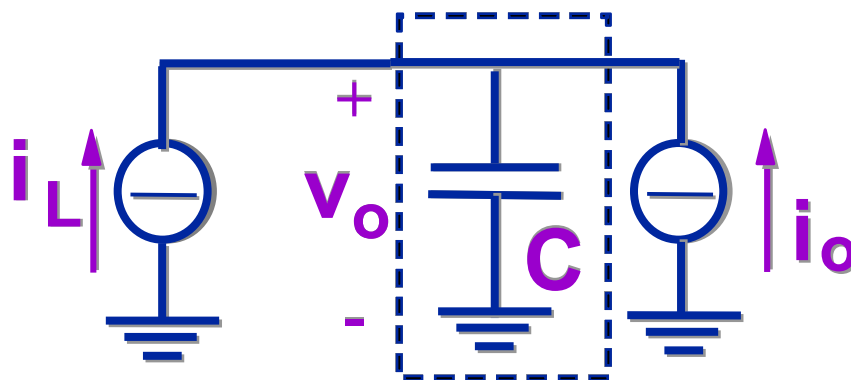

Dead-Beat Voltage Control Equation (DBVCE)

$$i_L^*(k+1) = \frac{C}{2 \cdot T_s} \cdot [v_o^*(k) - v_o(k)] - i_L(k) - i_o(k) - i_o(k+1)$$

Voltage control loop

 

Step response of the closed-loop voltage control.
Sampling frequency: 7.5 kHz

Two sample delay



Voltage control loop

Load current estimation

- The load current **does not need to be measured**
- The following **dead-beat (system poles in the origin) estimation** is derived (**DBEE**):

$$\tilde{i}_o(k-1) = \frac{C}{T_s} \cdot [v_o(k) - v_o(k-1)] - i_L(k-1) \quad (*)$$

- Estimation with **system poles away from the origin** implies a **IIR low-pass filter** on the estimated current (*)
- **Practically, a moving average (FIR) filter with 4 taps** was used

Voltage control loop

Control refinements



- **Feedforward of capacitor current reference** (obtained from output voltage reference).
- **Feedforward of the estimated load current.**
- **Interpolation between samples** (reduction of oscillations on inverter voltage at half of the sampling frequency).
- **Detuning of voltage control** (voltage estimation at instant $k+1$ with system pole away from the origin (low-pass filtering action) - **lower sensitivity to noise**).

Voltage control loop

Control refinements

Feedforward of the estimated load current (DBEE) allows the voltage dynamic equation to re-written:

$$v_o(k+1) = v_o(k) + \frac{2 \cdot T_s}{C} \cdot [i_L(k) - i_o(k)]$$



h is the index for $2T_{sw}$ sampling period

$$v_o(h+1) = v_o(h) + \frac{2T_s}{C} \cdot i_c^*(h-1)$$




Voltage control loop

Control refinements

Feedforward of also the **capacitive current** allows **DBVCE** to be re-written:

$$\Delta i_c^*(h) = \frac{C}{2 \cdot T_s} \cdot [v_o^*(h) - v_o(h)] - \Delta i_c^*(h-1)$$

 Where Δi_c^* stands for the **deviation** of the i_c^* **current** from its **feed-forwarded value**.



Voltage control loop

Control refinements

Linear interpolation can be used to re-construct the "missing" current sample. This modifies again the voltage dynamic equation:


$$v_o(h+1) = v_o(h) + \frac{T_s}{C} \cdot \left[\frac{5}{2} i_c^*(h-1) - \frac{1}{2} i_c^*(h-2) \right]$$

and generates the following control equation:

$$\Delta i_c^*(h) = \frac{2C}{5T_s} \cdot [v_o^*(h) - v_o(h)] - \frac{4}{5} \Delta i_c^*(h-1) + \frac{1}{5} \Delta i_c^*(h-2)$$


Voltage control loop

Control timing

 


Voltage control

Current control

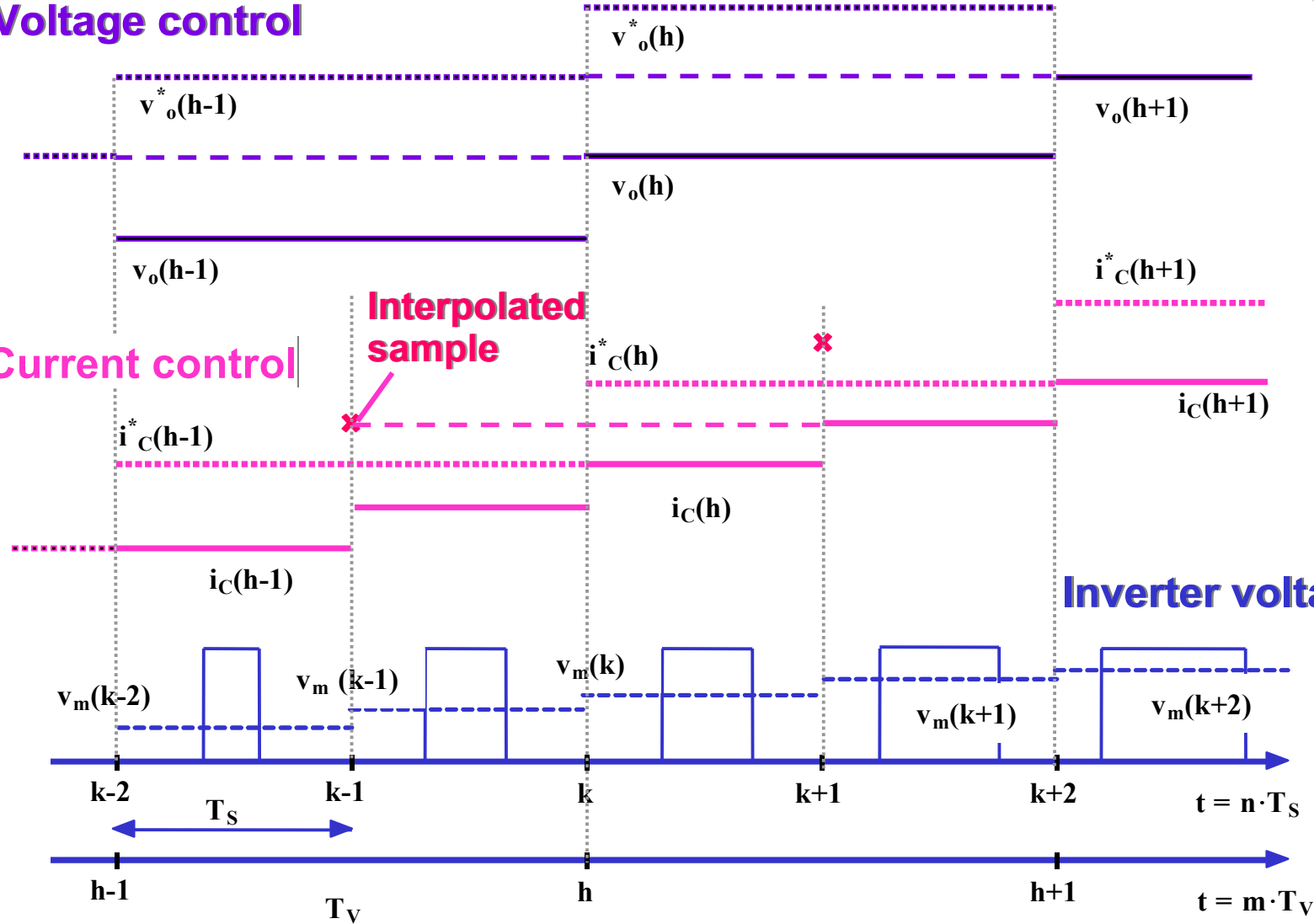


Voltage control loop

Effects of Interpolation

 

Average voltage generated by VSI

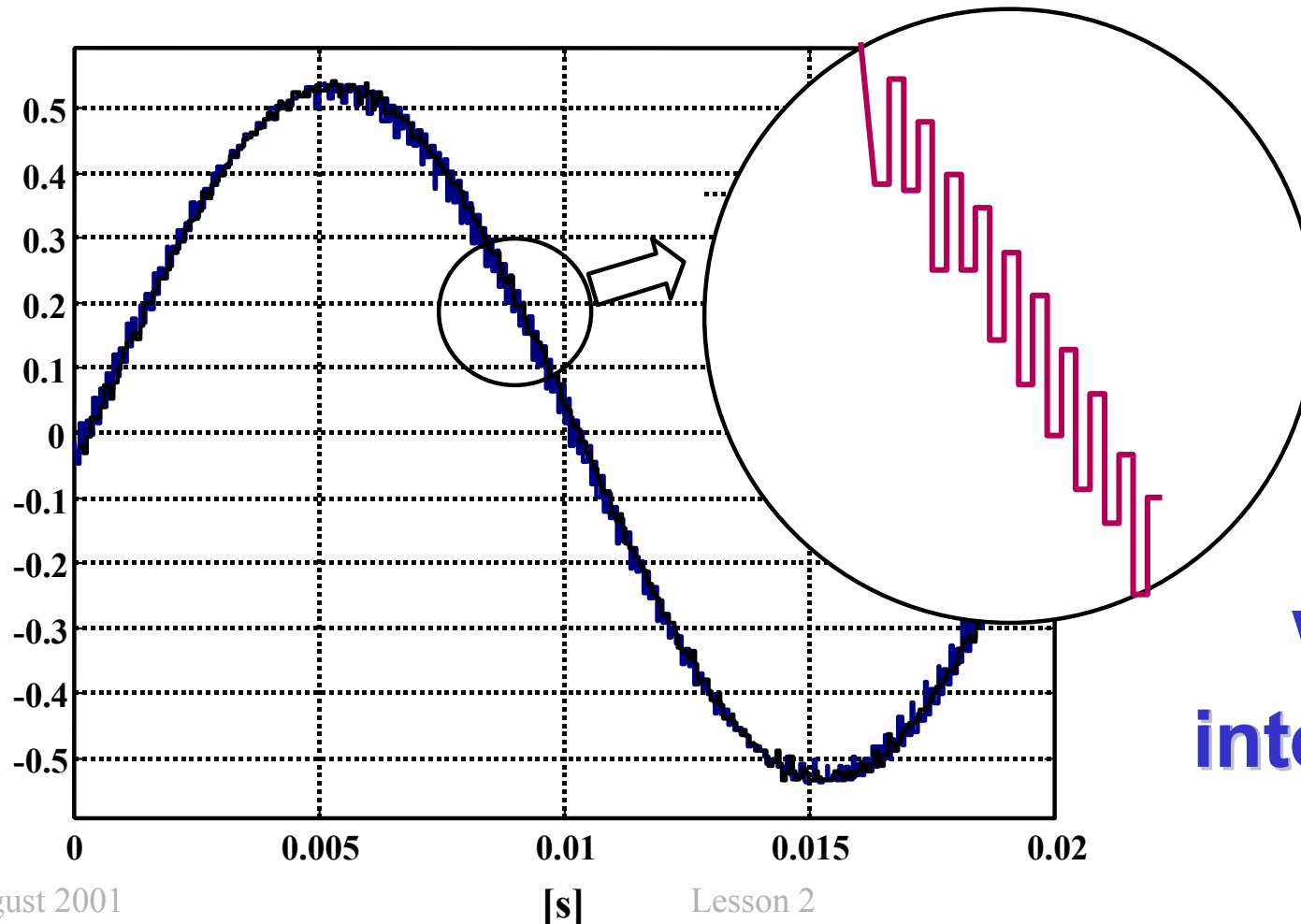


**without
interpolation**

Voltage control loop

Effects of Interpolation

Average voltage generated by VSI

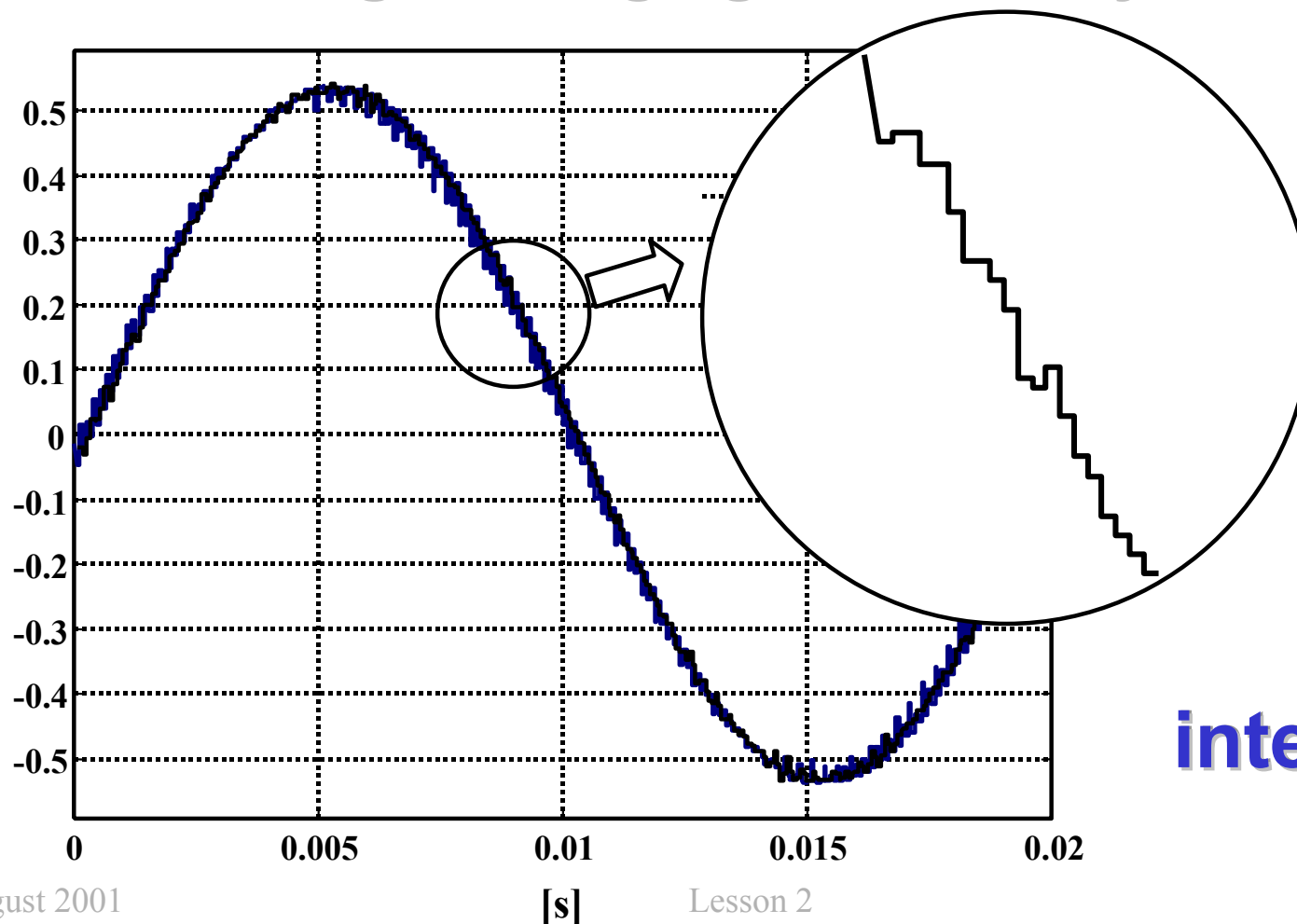


with
interpolation

Voltage control loop

Load current estimation


Actual and estimated load current

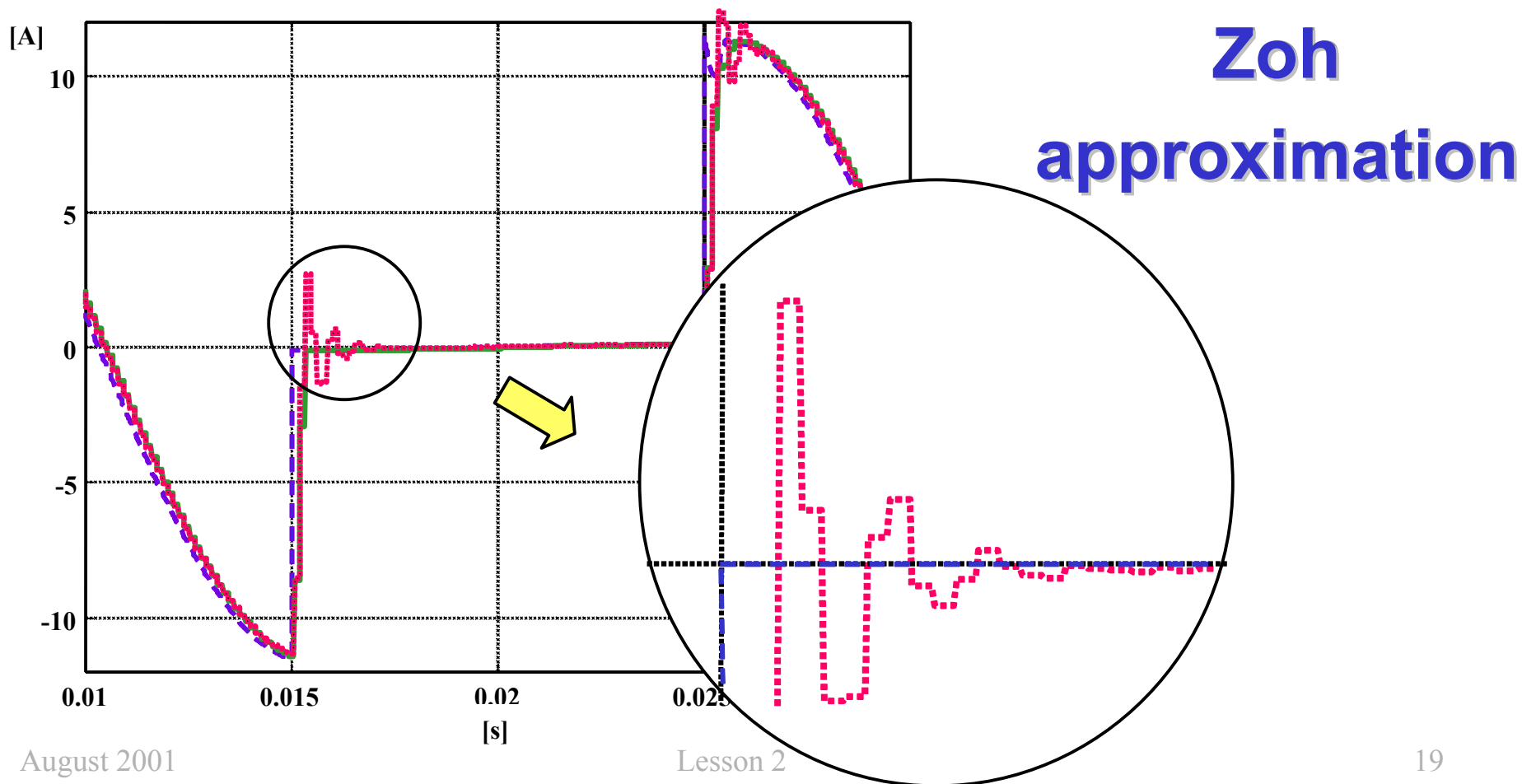

Voltage control loop

Load current estimation

Actual and estimated load current

 

Voltage control loop

De-tuning



To improve the controller's robustness it is possible to de-tune the voltage loop. This implies the allocation of the controller pole away from the origin of the complex plane.

$$\Delta v_o(h+1) = \Delta v_o(h) + \frac{2T_s}{C} \cdot \Delta i_c^*(h-1)$$

Voltage dynamic equation for the deviations from the ideal trajectory.

Voltage control loop

De-tuning



The control law which ensures a dead-beat response is simply given by:

$$\Delta i_c^*(h) = -\frac{C}{2T_s} \Delta \hat{v}_o(h+1)$$

where $\Delta \hat{v}_o$ represents the estimated output voltage deviation (due to calculation delay we can't use the actual deviation).

Voltage control loop

De-tuning




The estimator can have the classical Luenberger structure. K_s allows to select the pole location.

$$\Delta \hat{v}_o(h+1) = \Delta \hat{v}_o(h) + \frac{2T_s}{C} \cdot \Delta i_c^*(h-1) + K_s (\Delta v_o(h) - \Delta \hat{v}_o(h))$$


If the pole is located in the origin (dead-beat estimator) we have the usual DBVCE for the deviation. Otherwise we have a de-tuned controller with a first order response.

Control block diagram

 


Output filter capacitor and load model

Control block diagram

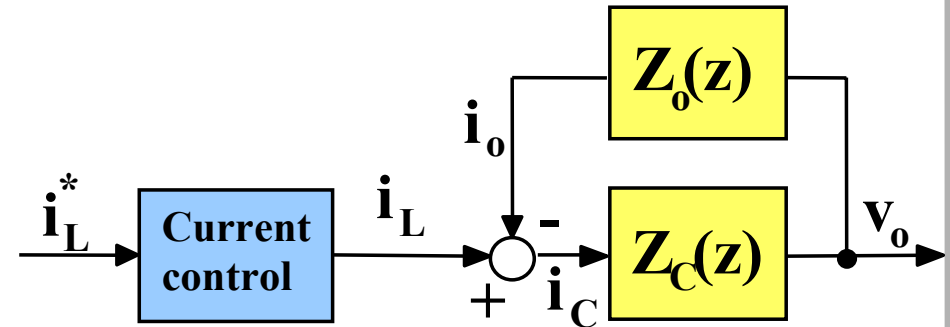


Deadbeat current control

Control block diagram

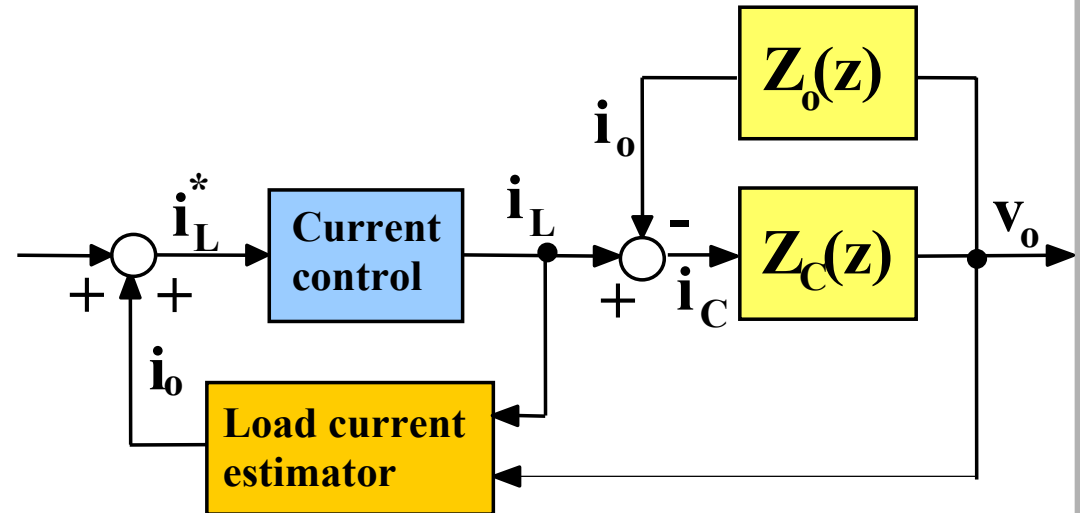


Feedforward of the estimated load current

Control block diagram

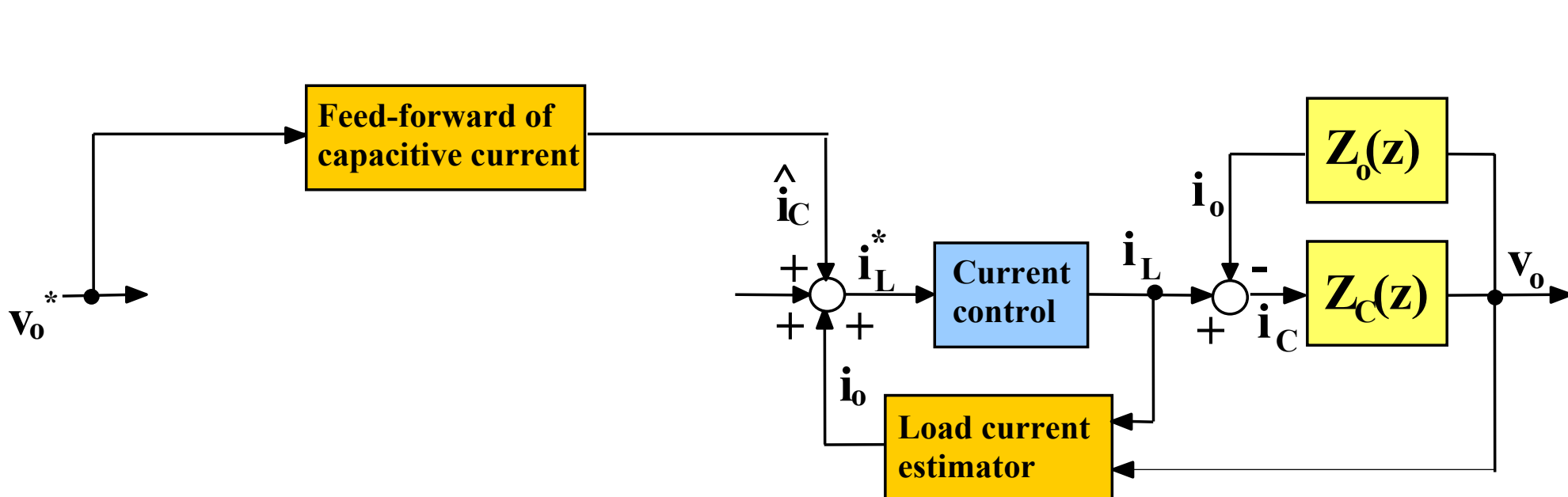


Feedforward of capacitor current reference

Control block diagram

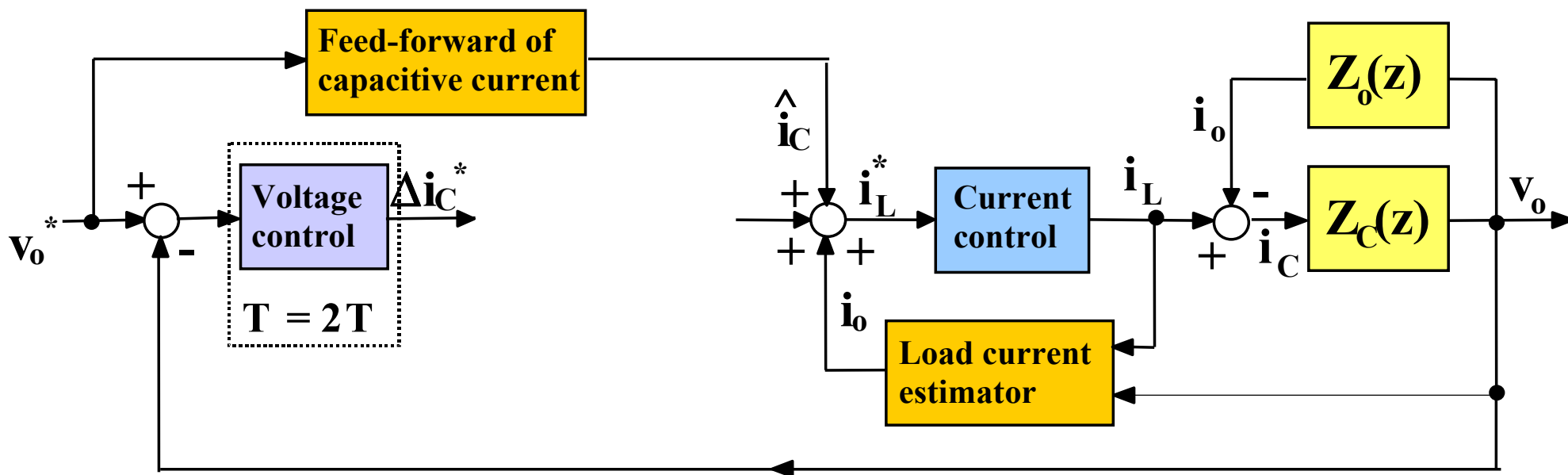


Deadbeat voltage control

Control block diagram

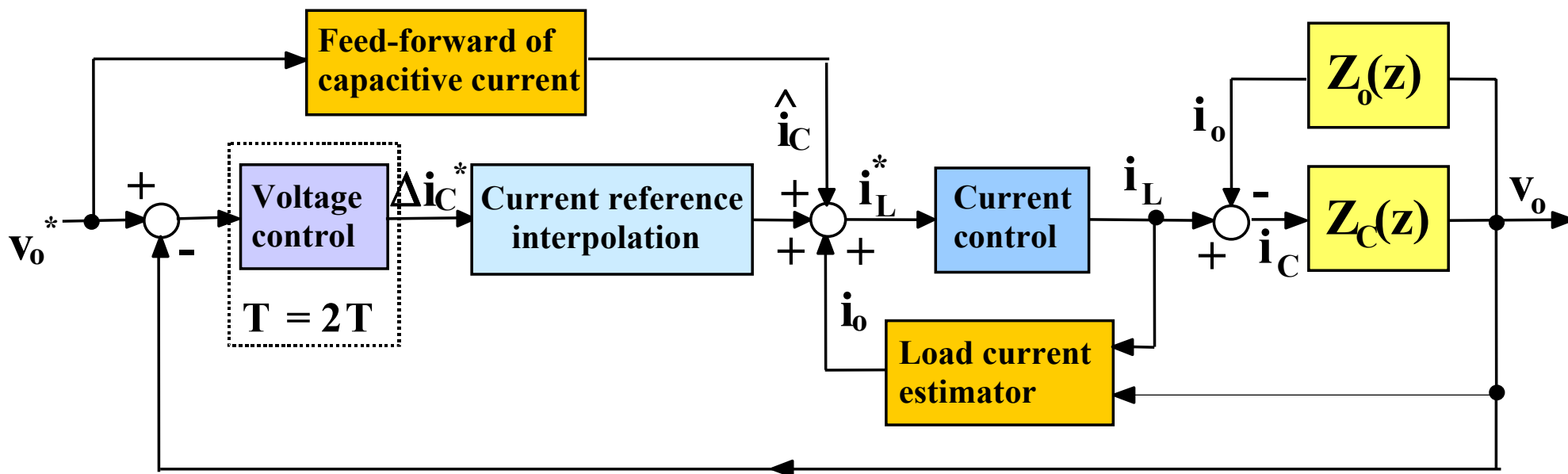

Capacitor current reference interpolation

Control block diagram

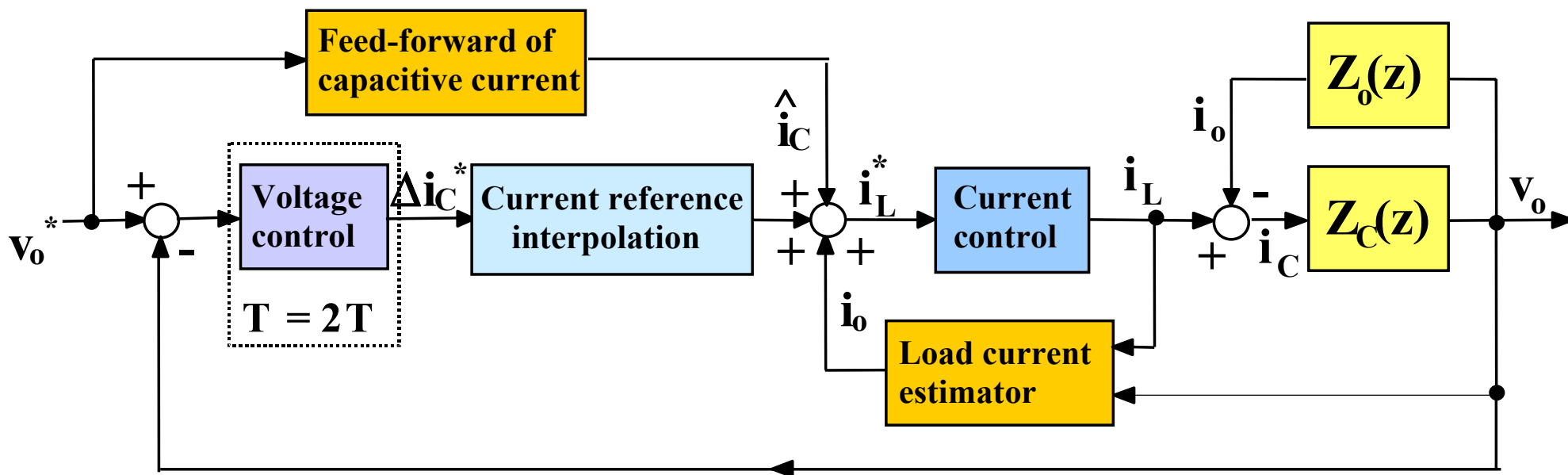



Final scheme

Control implementation



- **The control program is implemented by means of a floating point DSP:**
 - **ADSP21062: 33 Mips, 30 ns instruction cycle**
- **The power converter is controlled by a motion control oriented fixed point DSP:**
 - **ADMC401: 26 Mips, 38.5 ns instruction cycle**
- **The two units are interfaced by means of a dual port RAM (1kword). A suitable communication protocol is implemented.**

Control implementation

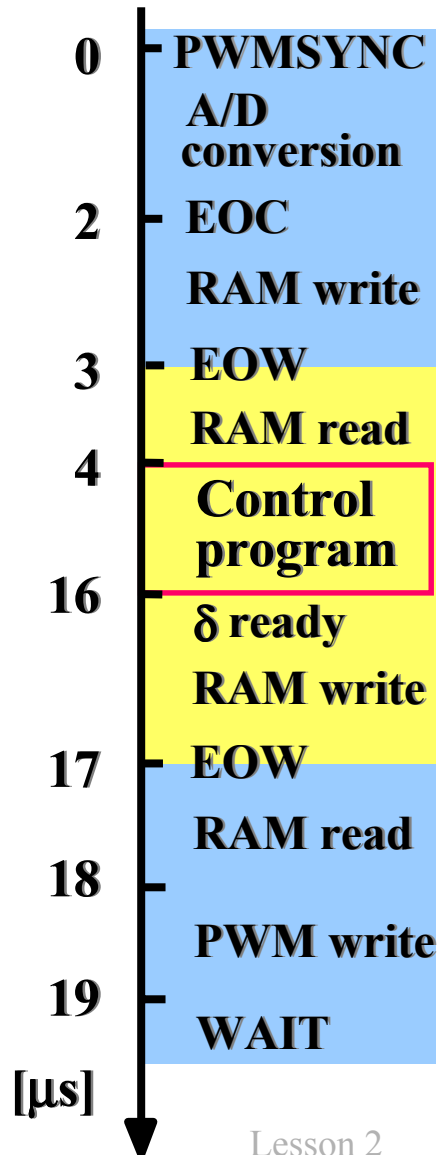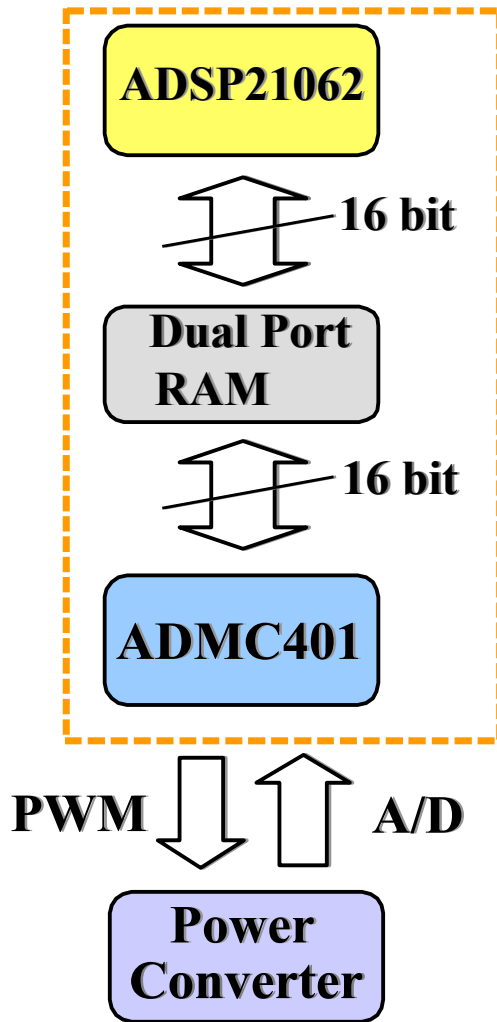


Scheme and timing of the control system

Control implementation



- **The control program is written in C language, and the AD C-compiler for the ADSP 21062 is used.**
- **Given the very high performance of the DSP unit, no timing problem is encountered, even for very complex algorithms and 20 kHz operating frequency.**
- **Data exchange between the two units is dealt with by means of simple data memory write (DM) instructions.**

Timing of the control algorithm

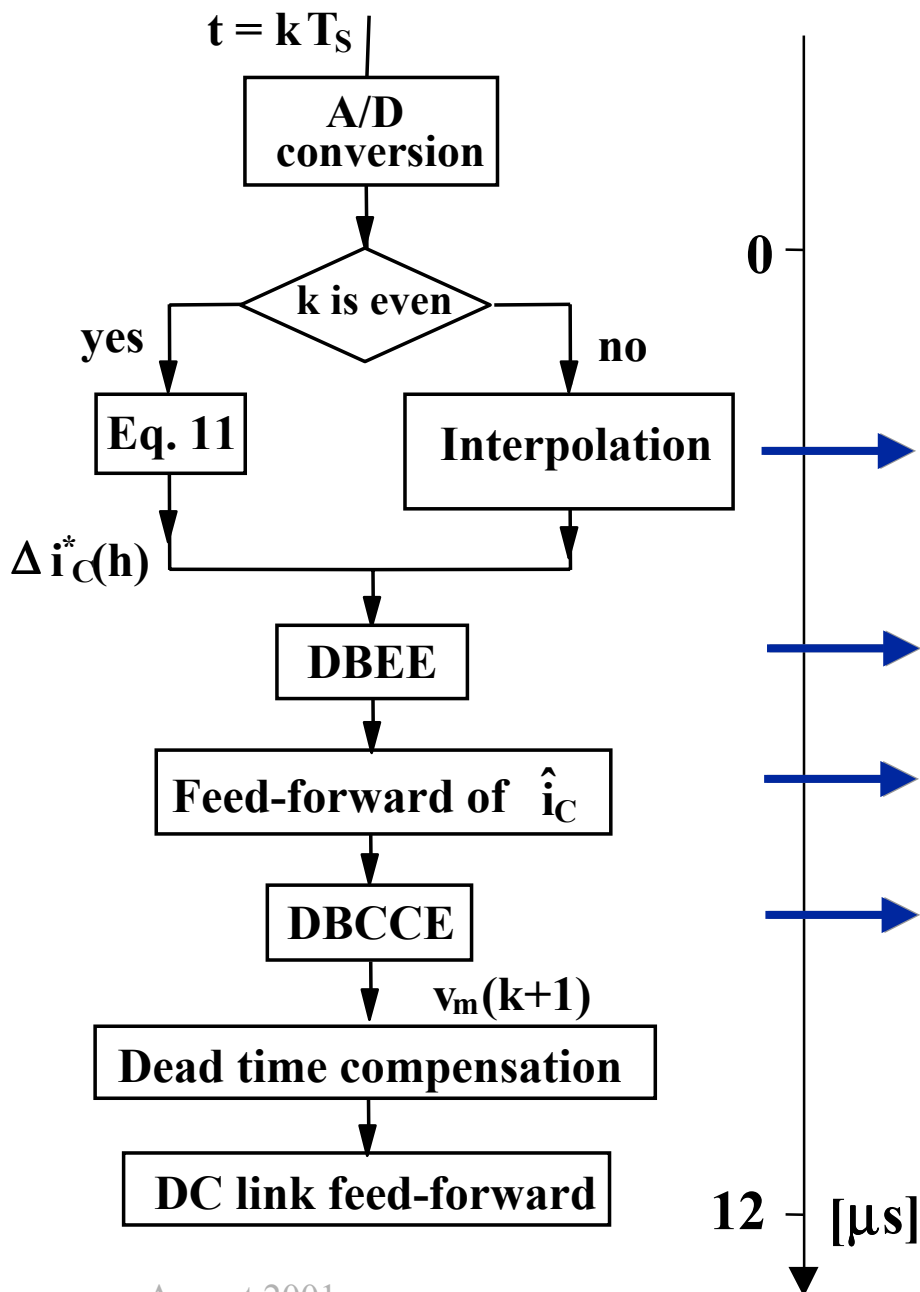

Dead-beat voltage control interpolation

Load current estimation

Capacitor current estimation

Dead-beat current control

50% increase compared to PI control

Experimental results



Experimental prototype's parameters


Nominal output power	P_o	1	[kVA]
Nominal output voltage	V_{oRMS}	115	[V]
Minimum load DF	$\cos \phi$	0.8	
DC link voltage	V_{DC}	250	[V]
Output frequency	f_o	50	[Hz]
Output inductor	L	1.8	[mH]
Output capacitor	C	120	[μF]
Switching frequency	f_s	15	[kHz]

Experimental results



Tek Stop: 100kS/s

376 Acqs

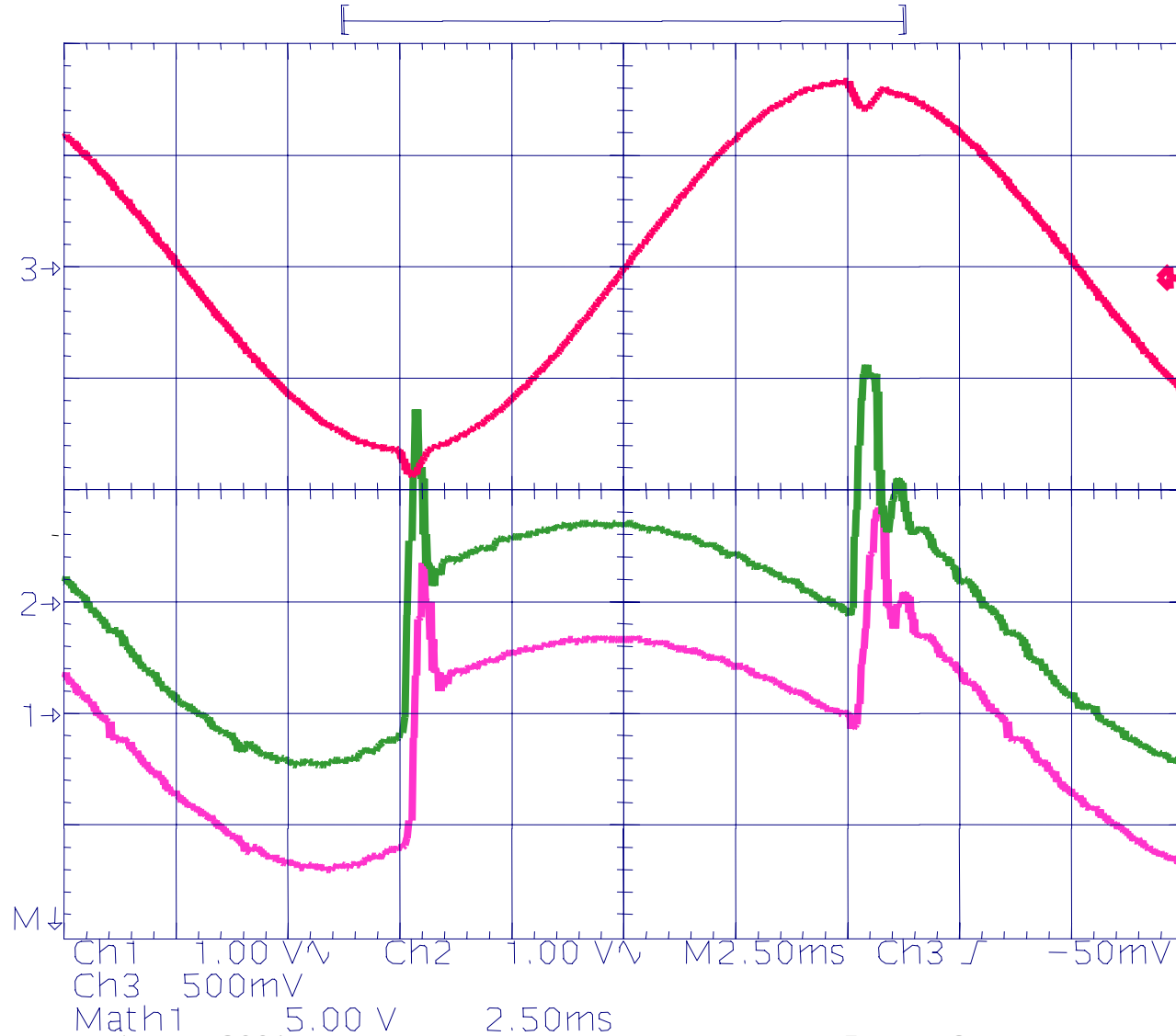


**Step load variations
100% - 0%**

**Output voltage
[100V/div]**

**Current reference
[10A/div]**


**Actual current
[10A/div]**

Experimental results

 

Tek Stop: 100kS/s

12 Acqs

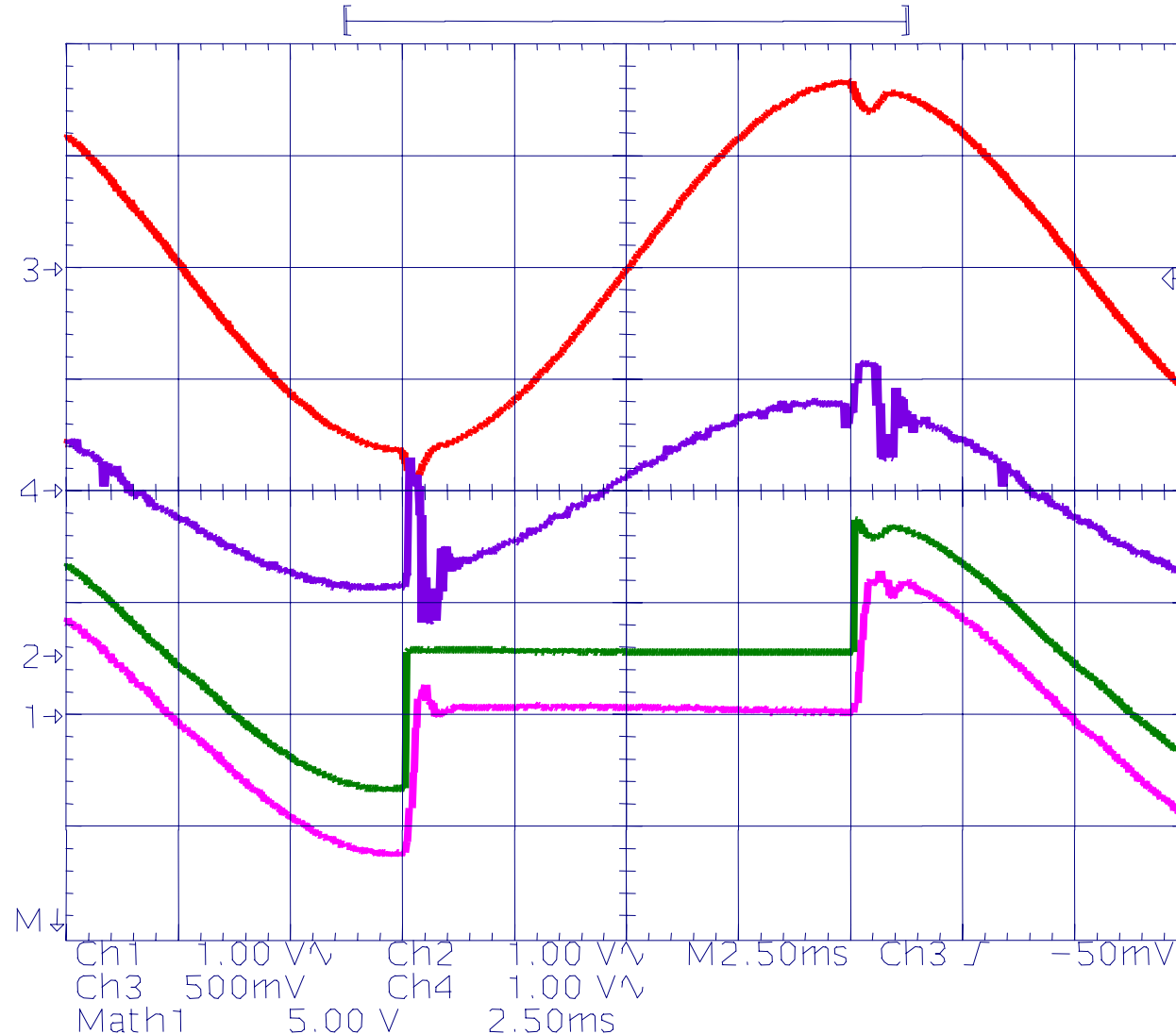

**Step load
variations
100% - 0%**


**Output voltage
[100V/div]**

**Reference voltage
[200V/div]**

**Load current
[10A/div]**


**Estimated current
[10A/div]**

Experimental results

 

Tek Stop: 100kS/s

94 Acqs

 

Distorting load

Output voltage
[100V/div]

Reference voltage
[200V/div]

Load current
[10A/div]

Estimated current
[10A/div]


THD=3.4%

Experimental results



Tek Stop: 100kS/s

150 Acqs

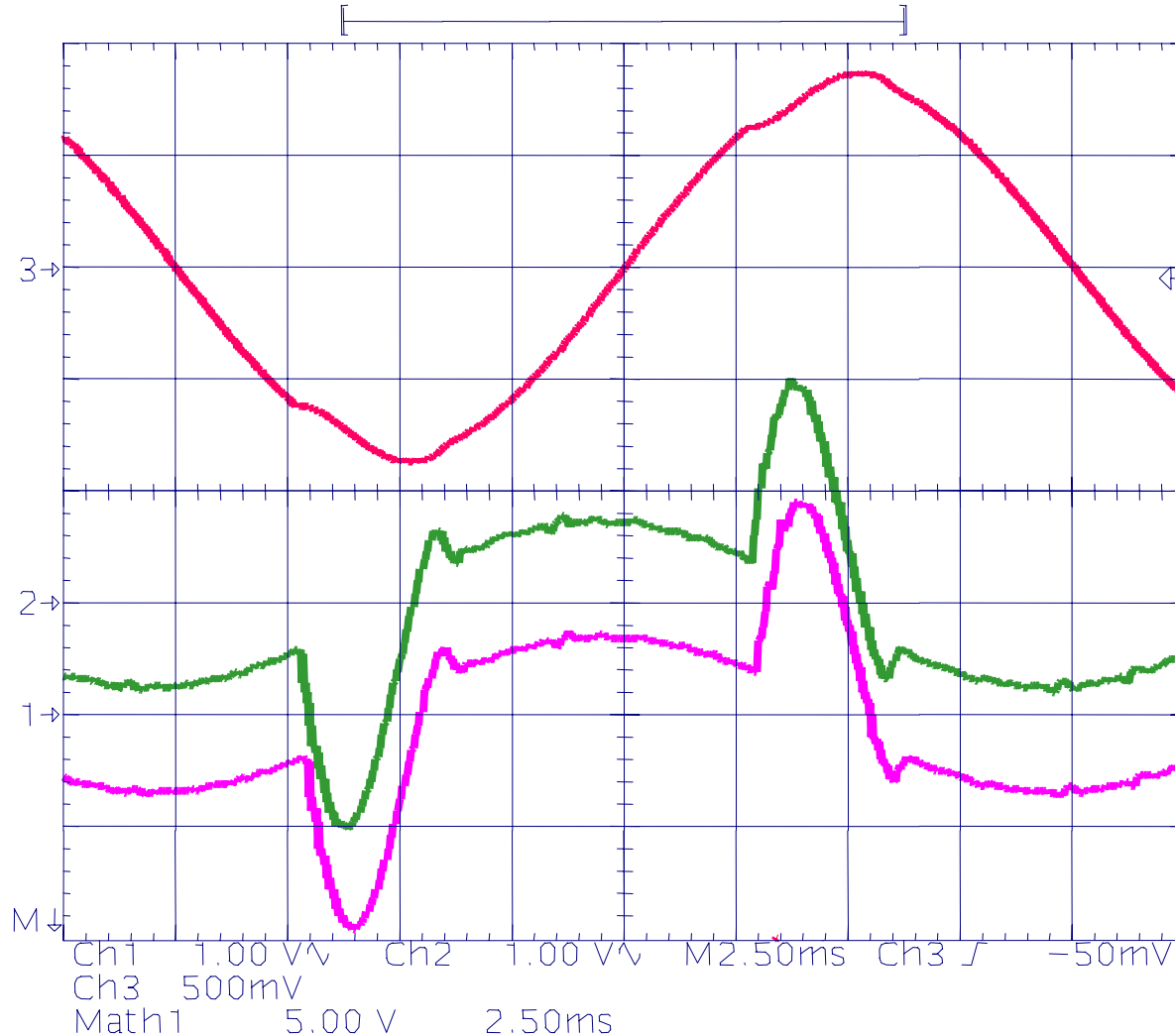

Distorting load


**Output voltage
[100V/div]**

**Current reference
[10A/div]**

**Actual current
[10A/div]**


THD=3.4%

Experimental results

 

Tek Stop: 100kS/s

94 Acqs

 

**Distorting load
PI control**

**Output voltage
[100V/div]**

**Current reference
[10A/div]**

**Actual current
[10A/div]**

THD=6.0%



Reference

S. Buso, S.Fasolo, P. Mattavelli, “Uninterruptible Power Supply Multi-Loop Control Employing Digital Predictive Voltage and Current Regulators”, Applied Power Electronics Conference (APEC) Proc., Anaheim, California, 4-8 March, 2001, pp. 907-913.