



## Lesson 3

# **Digitally-Controlled Single-Phase AC/DC Integrated PWM Converter**



# Goal of the work

Development of a **new topology** of single phase insulated ac/dc converter featuring:


- **high power factor**
- **full control of the output dc voltage**
- **high-frequency insulation transformer**
- **high-frequency line filter inductor.**




# Presentation Outline

- **Converter topology**
  - operation modes
  - structural constraints
- **Design procedure**
- **Control strategy**
  - analog control
  - digital control
- **Experimental results**


# Basic AC/DC Topology

 

# Integrated Converter Topology

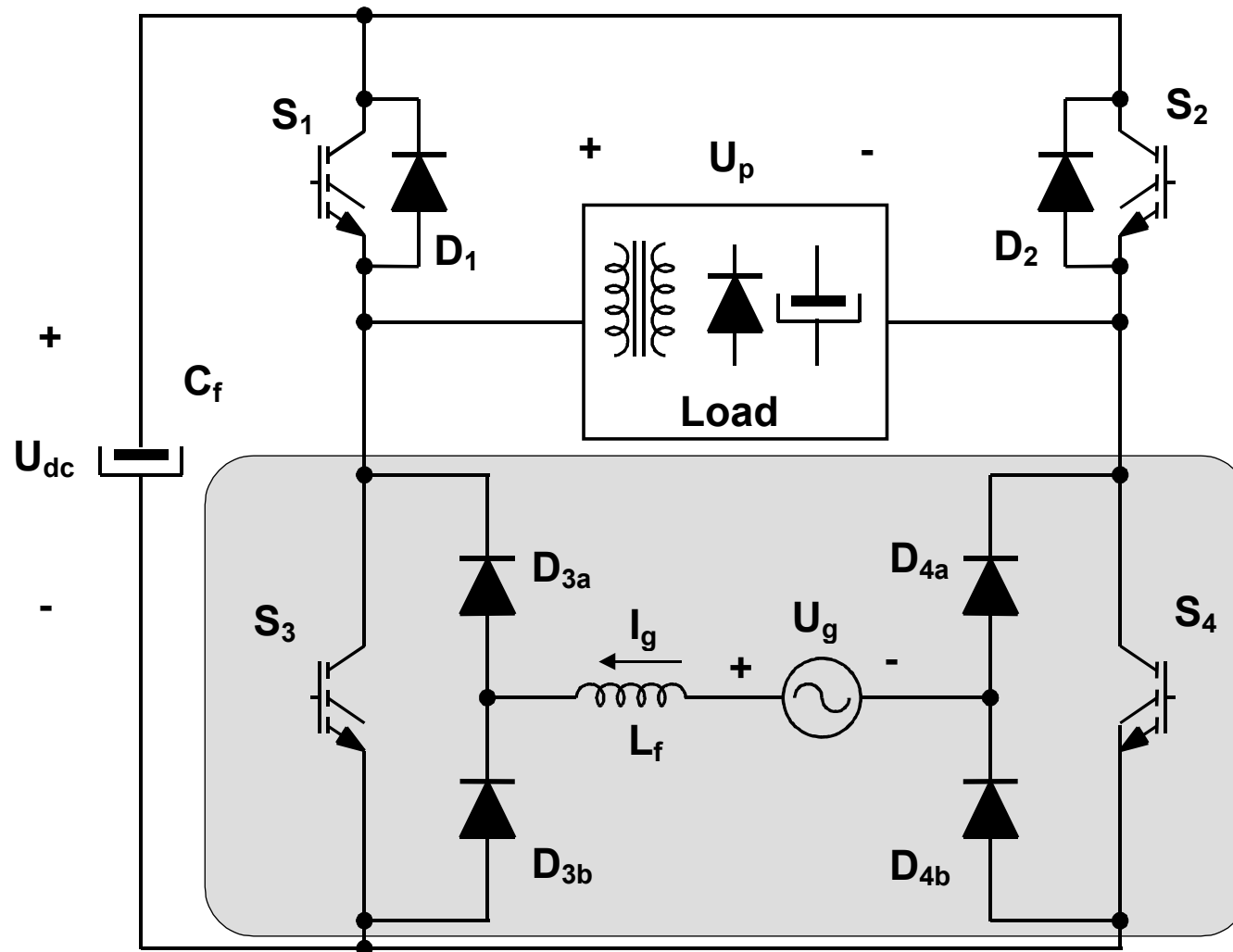

# Converter Modes of Operation

 


Switches are driven so as to generate **powering** and **free-wheeling** phases.

Free-wheeling phases are obtained closing the two **high-side** or the two **low-side** switches.

The two free-wheeling phases have **opposite effect** on the converter input current thus allowing control of the current waveform.

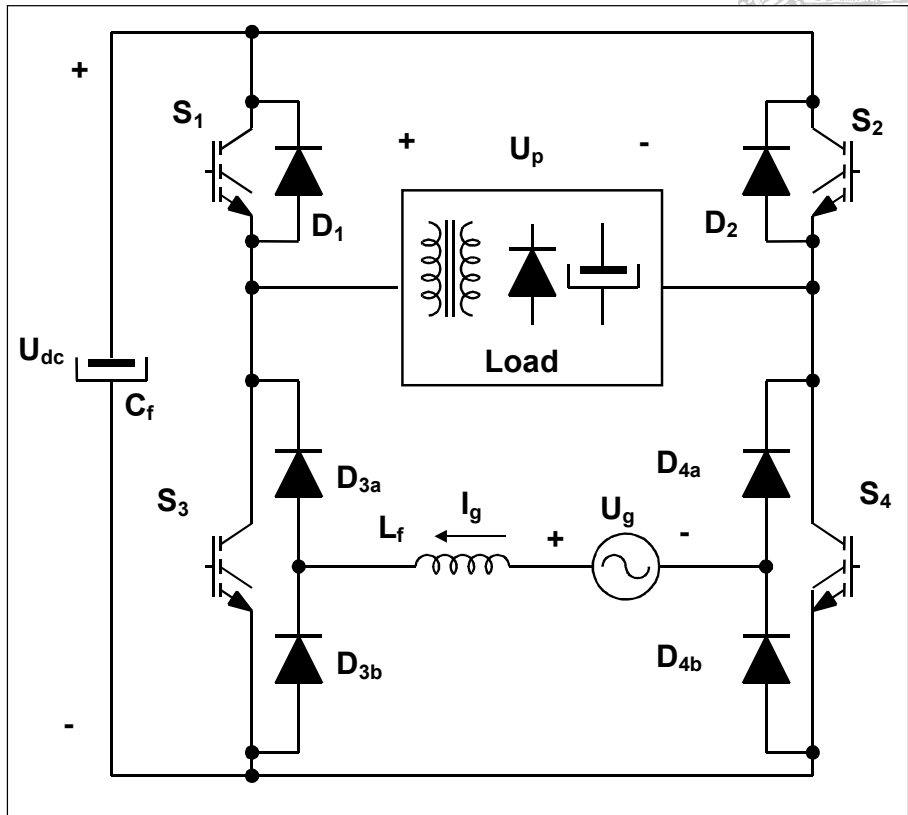The converter **integrates the PFC and inverter stages** but loses some degree of control. This **limits the line (or load) side performance**.



# Converter Operation Table

Switches ON	Diodes ON	$U_g$	$U_p$	$I_g$
$S_1$ - $S_2$	$D_1, D_{3a}, D_{4b}$	$> 0$	0	decrease
$S_3$ - $S_4$	$D_{3a}, D_{4b}$	$> 0$	0	increase
$S_1$ - $S_4$	$(D_1), D_{3a}, D_{4b}$	$> 0$	$+U_{dc}$	decrease
$S_2$ - $S_3$	$D_{3a}, D_{4b}$	$> 0$	$-U_{dc}$	increase
$S_1$ - $S_2$	$D_2, D_{3b}, D_{4a}$	$< 0$	0	increase
$S_3$ - $S_4$	$D_{3b}, D_{4a}$	$< 0$	0	decrease
$S_1$ - $S_4$	$D_{3b}, D_{4a}$	$< 0$	$+U_{dc}$	decrease
$S_2$ - $S_3$	$(D_2), D_{3b}, D_{4a}$	$< 0$	$-U_{dc}$	increase

# Operation Constraints



- The duration of the powering phases must be the same to avoid output transformer saturation.
- The modulation period,  $T_{sw}$ , is then divided into three phases:
  - positive powering phase: duration  $M/2 \cdot T_{sw}$
  - negative powering phase: duration  $M/2 \cdot T_{sw}$
  - free-wheeling phase: duration  $(1 - M) \cdot T_{sw}$
- During the free-wheeling phase, input current control is possible.



# Operation Constraints

The input current can be controlled **only during the free-wheeling phases** of the load side control.



When the modulation index **M** is **high**, the available time for the input current control is **small**.

$$M = \frac{U_o}{U_{dc}}$$

The input **current control** is possible **only when**:

$$U_{gmin} < |U_g(\theta)| < U_{gmax}, \text{ where } \left\{ \begin{array}{l} U_{gmin} = \frac{M}{2} \cdot U_{dc} \\ U_{gmax} = \left(1 - \frac{M}{2}\right) \cdot U_{dc} \end{array} \right.$$


# Operation Constraints

  

**Average ac voltage at converter input and corresponding input current control angle  $\phi$**
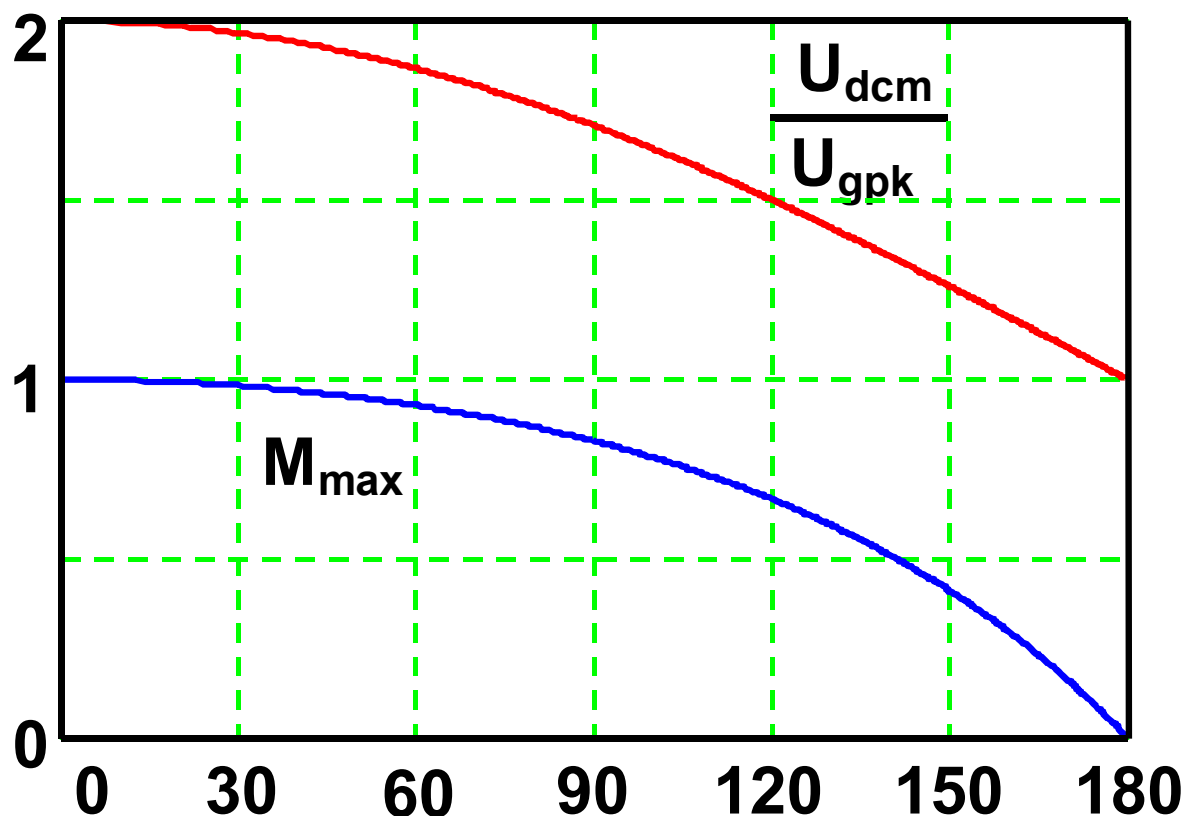
# Operation Constraints

Maximum allowed duty-cycle  $M$  and dc link voltage to peak input voltage ratio as a function of the line current control angle  $\phi$



$$\phi = 120^\circ$$

$$M_{MAX} = 0.67$$

$$U_{dc\_max} = 1.5 U_{g\_pk}$$

# Converter Design

From the **previous graphs** the following design procedure can be adopted:

- Select **maximum dc link voltage**, based on switches' voltage rating;
- Given the **peak line voltage**, the design diagram allows to determine the maximum achievable **M value**;
- The same diagram also allows to determine the **line control angle  $\phi$** , that should be equal or higher than  $120^\circ$ , to get a satisfactory PF and current THD.

# Converter Design



## Passive components' selection:

- Given the desired input current ripple, input inductance is given by:

$$L_f = \frac{U_{dc}}{4 \cdot f_{sw} \cdot \Delta I_{Lpp}}$$


$U_{dc}$  = dc link voltage

- Given the desired low frequency output voltage ripple, the dc link capacitor can be selected according to:

$$C_f = \frac{P_{out}}{2 \cdot \pi \cdot f_{line} \cdot \Delta U_{dcpp} \cdot U_{dc}}$$

$P_{out}$  = output power

# Converter Design

 

The **maximum stresses** for the active components are:

- **Voltage stress equal to the DC link voltage**
- **Current stress for the upper switches as in any standard inverter**
- **Current stress for the lower switches and diodes is the sum of inverter load side and line side currents**





# Converter Control

- We considered both an analog and a digital control technique.
- The analog solution is based on a standard PFC controller and on a modified phase-shift modulator for full-bridge converters.
- The digital solution is based on a dead-beat type of control equation and on a custom digital PWM modulator.
- In both cases the output voltage may be controlled by a standard regulator (e.g. PID).

# Analog Converter Control




## Analog PWM modulator

  




# Analog Converter Control

## Control of the free-wheeling phase

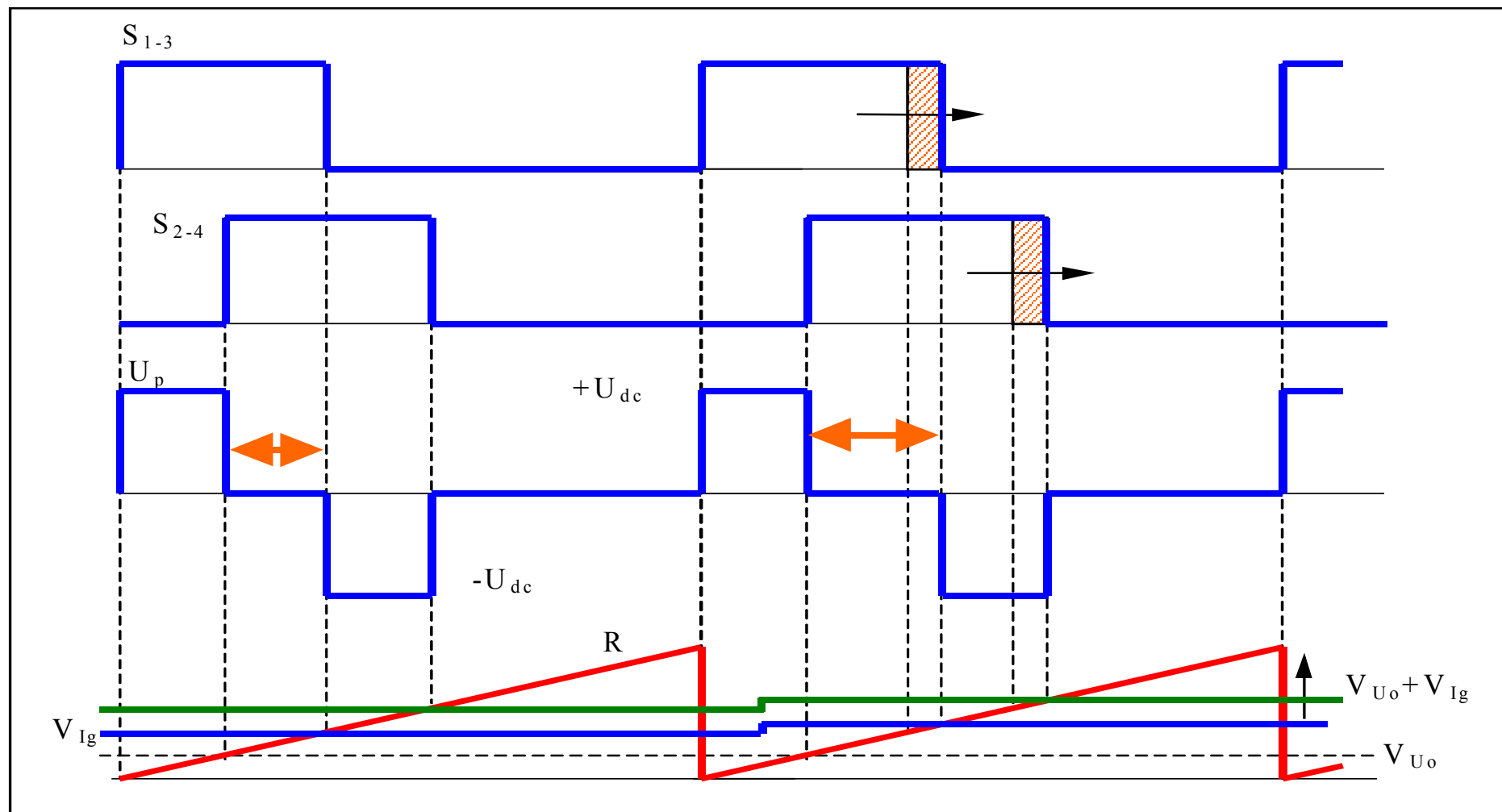

# Analog Converter Control

 

**Symmetrical  
positioning of  
switching pulses  
requires two  
additional  
commutations**



# Analog Converter Control

- The **input variables** of the PWM modulator, i.e.  $V_{Uo}$  and  $V_{Ig}$ , must be provided by the output voltage and input current regulators.
- The **output voltage regulator** may be any of those used for forward converters. A simple solution might be **voltage mode control** with **PID** regulator.
- The **input current regulator** may be a standard **average current PFC controller** with analog multiplier.



# Digital Converter Control

- Digital implementation requires significant computational power to allow input current, DC link voltage and output voltage control.
- Flexibility in the PWM modulator is required to implement the non-standard modulation strategy.
- Texas Instruments TMS320F240 DSP is the hardware platform selected for the practical implementation.



# Digital Converter Control

**The control system is organized as follows:**

- **Digital PWM**
- **Input current control loop**
- **Output voltage control loop (not implemented)**
- **DC link voltage control loop**




# Digital control block diagram

# Digital PWM



- The **PWM** implementation uses **one of the three** DSP internal counters. It is programmed for a period of **50  $\mu$ s (20kHz)**.
- **Three PWM outputs** are used to generate the logic state of two inverter legs.
- The **CMP** input registers of the PWM units are loaded with values which are related to the load duty-cycle (**M**) and line “duty-cycle”  **$\gamma$** .
- The duty-cycles are generated by **external loops** (output voltage and line current loops).

# Digital PWM

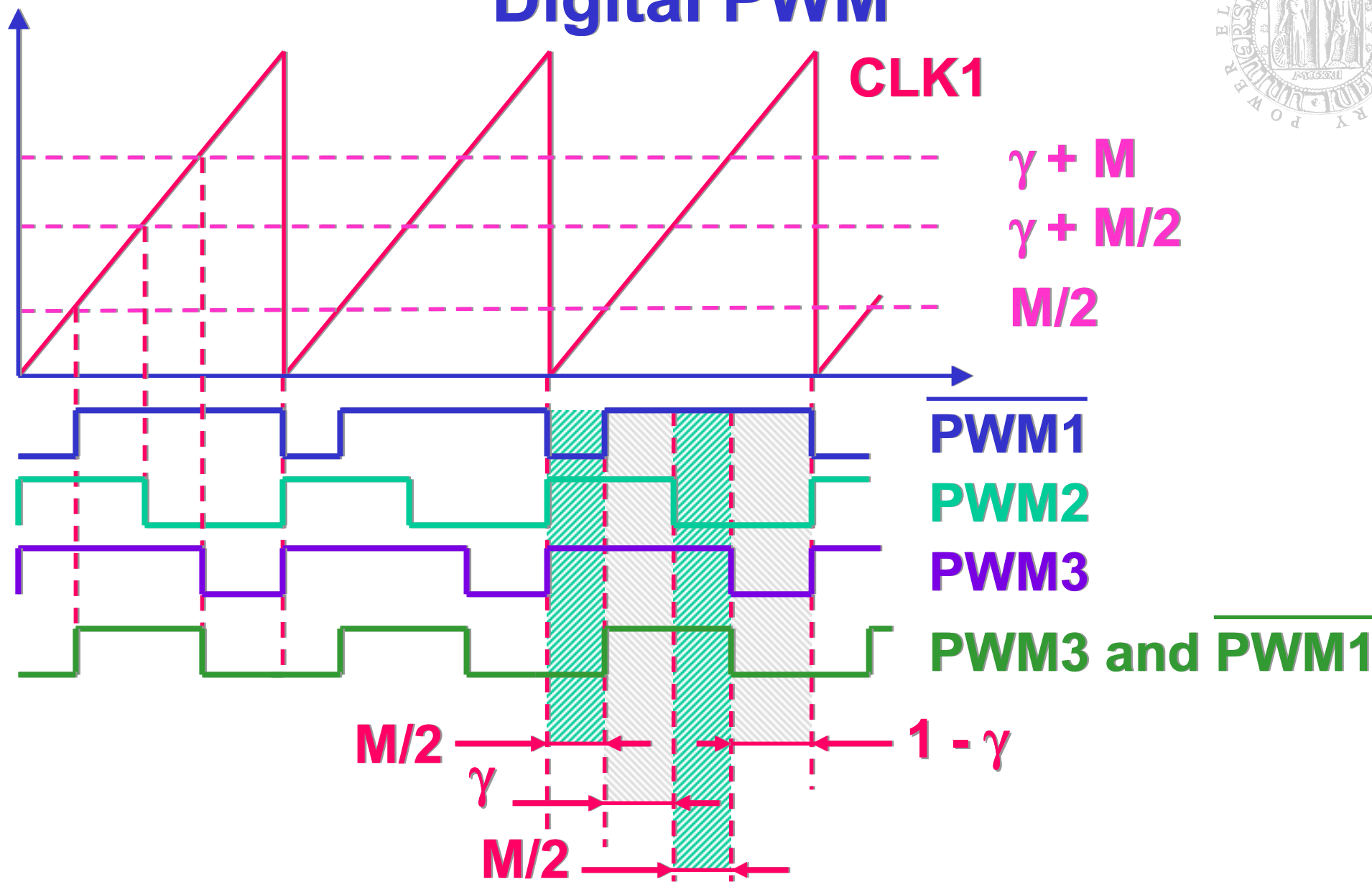



# Digital PWM

- This solution allows simultaneous and independent variation of the input variables.
- Its response time is equal to one modulation period (worst case).
- The constraint

$$\gamma_{\max} = 1 - M$$

requires the definition of a strategy to deal with the interactions between the two loops.

# Digital PWM




- The strategy we applied is to give the **highest priority to the output voltage control loop.**
- When the output voltage controller requires a **sudden variation of the parameter  $M$ , this is performed even if input current control is lost.**
- The input current controller must be **capable of tolerating this momentary control losses without generating persisting oscillations and/or instabilities.**
- These problems arise **only in the presence of transients at the load side.**

# Digital PWM

Tek Stop: 2.50MS/s

33 Acqs

 

$S_{1-3}$  logic state

$S_{2-4}$  logic state

$M$  step variation

Dynamic response of the PWM modulator

# Input current control

- The input current dynamic equation is the following:

$$i_g(t) = \frac{1}{L_f} \cdot \int_0^t U_{L_f}(\tau) d\tau = \frac{1}{L_f} \cdot \int_0^t U_g(\tau) - U_{ac}(\tau) d\tau$$

- This can be discretized by assuming the voltage to be constant between sampling instants (zero order hold discretization).

# Input current control

- The **input inductor average voltage** in a modulation period can be easily found to be:

$$U_{L_f} = U_g - U_{dc} \cdot [M/2 + \delta \cdot (1 - M)]$$

- Consequently, the **current variation** in a modulation period is given by:

$$i_g(k+1) - i_g(k) = U_g(k) \cdot \frac{T_{sw}}{L_f} + \\ - \left[ \frac{M}{2} + \delta(k) \cdot (1 - M) \right] \cdot U_{dc}(k) \cdot \frac{T_{sw}}{L_f}$$

# Input current control

- The quantity  $\delta \cdot T_{sw}$  is the duration of the upper (or positive) free-wheeling phase.
- It is possible to calculate  $\delta(k+1)$  so as to force the current  $i_g$  to reach its reference at instant  $k+2$ .
- This generates the following control equation:

$$\delta(k+1) = -\delta(k) - \left[ g_{eq} \cdot |U_g(k)| - |i_g(k)| \right] \cdot \frac{L_f}{T_{sw} \cdot U_{dc} \cdot (1-M)} + \frac{2 \cdot |U_g(k)|}{(1-M) \cdot U_{dc}} - \frac{M}{1-M}.$$

# Input current control

- The control equation assumes that

$$i_g(k+2) = g_{eq} \cdot U_g(k)$$

i.e.  $U_g$  is **slowly varying** with respect to the control period.

- $G_{eq}$  is the converter **equivalent input conductance**. This is generated by the **DC link voltage control loop**.

# Input current control

- The **control equation** is difficult to implement because it implies the execution of **divisions**.
- The variation of the DC link voltage can be neglected, i.e.  $U_{dc} \cong \text{constant}$ .
- The **variation of M** can be dealt with defining a new control variable:

$$\gamma(k) = [1 - M(k)] \cdot \delta(k)$$

- While  $\delta$  can vary from 0 to 1  $\gamma$  can vary from 0 to 1-M.



# Input current control

- The control equation can be re-written in terms of the  $\gamma$  variable.
- This way, only MAC instructions can be used.

$$\gamma(k+1) = -\gamma(k) - \left[ g_{eq} \cdot |U_g(k)| - |i_g(k)| \right] \cdot \frac{L_f}{T_{sw} \cdot U_{dc}} + \frac{2 \cdot |U_g(k)|}{U_{dc}} - M(k).$$

- This is the implemented current control equation.
- The absolute value is required to deal with  $U_g < 0$ .

# Current control simulation




**Simulation of the proposed input current digital control was performed.**

## Converter Parameters


<b>Line voltage</b>	<b><math>U_g</math></b>	<b><math>240 \pm 10\%</math></b>	<b><math>V_{RMS}</math></b>
<b>Output power</b>	<b><math>P_o</math></b>	<b>5</b>	<b>kW</b>
<b>Switching frequency</b>	<b><math>f_{sw}</math></b>	<b>20</b>	<b>kHz</b>
<b>Input inductor</b>	<b><math>L_f</math></b>	<b>1</b>	<b>mH</b>
<b>DC link capacitor</b>	<b><math>C_f</math></b>	<b>800</b>	<b><math>\mu F</math></b>

# Current control simulation

 


**Input current  
in a line half-  
period**

# Current control simulation

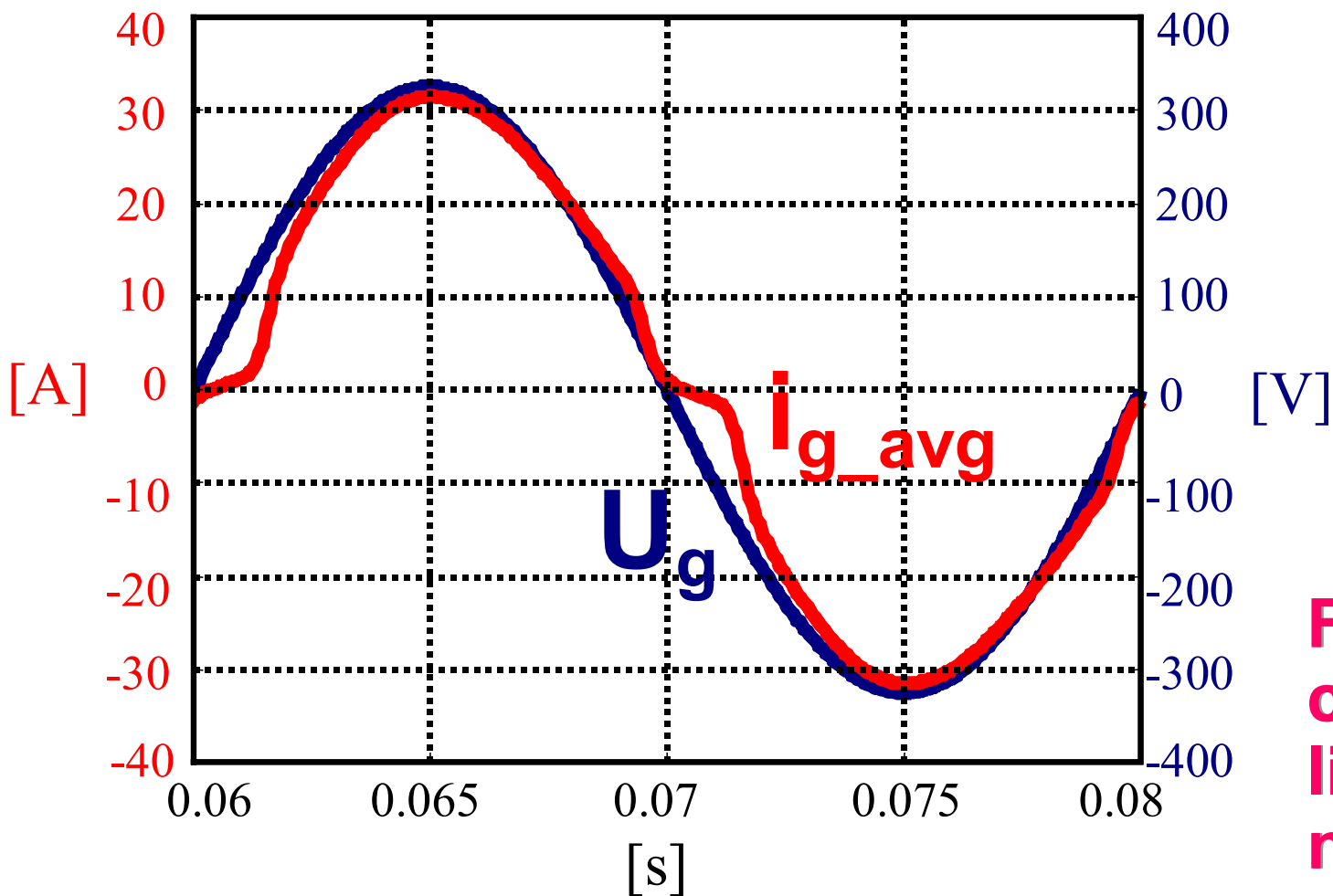


**Filtered line current and line voltage at nominal output power**

# Current control simulation

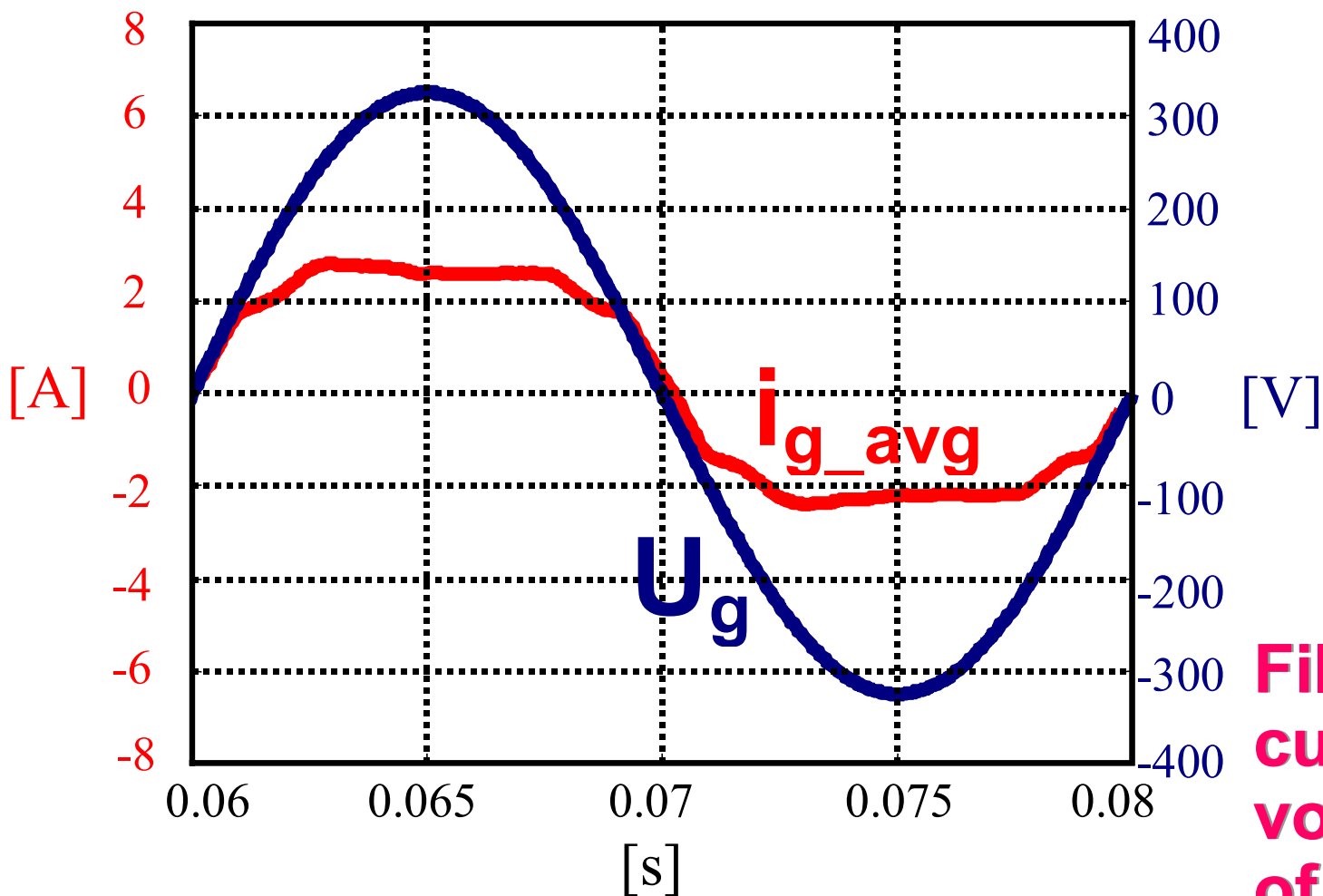

**Filtered line current and line voltage at 10% of nominal output power**

# Current control simulation

 

**Input current  
control step  
response**




# DC link voltage control

- The **DC link voltage control** can be implemented quite straightforwardly.
- It is a simple **PI regulator** designed on the **equivalent load resistance** and **DC link capacitor**, as in any conventional PFC.
- The **bandwidth** is limited to **10 - 15 Hz** to avoid **input current distortion**.
- **Sampling frequency** can be **reduced accordingly**. In our implementation we used **1 kHz**.

# DC link voltage control

Tu

From: U(1)

 


**Open loop gain  
Bode plot.**

**$F_{cr} = 15\text{Hz}$**

**$m_f = 70^\circ$**



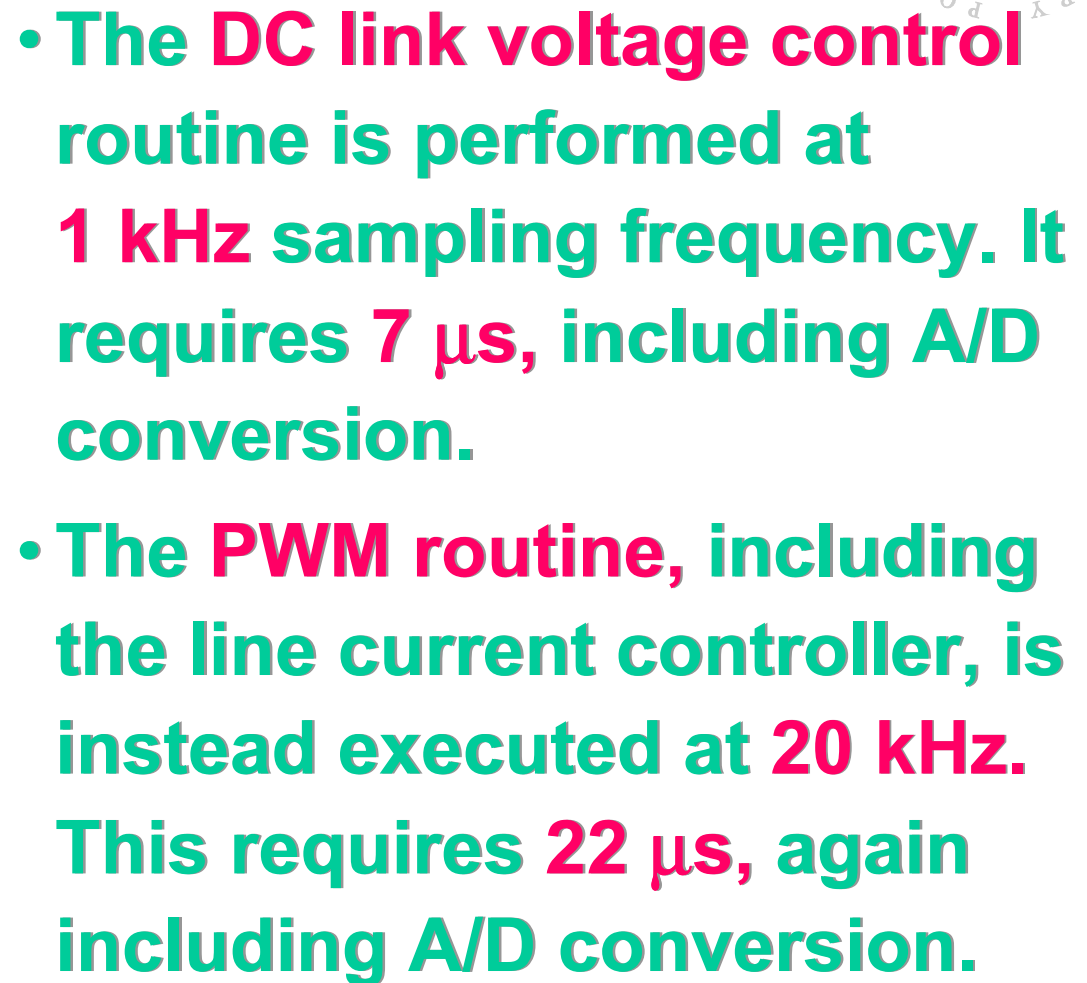


# PWM implementation



Tek Stop: 2.50MS/s

33 Acqs

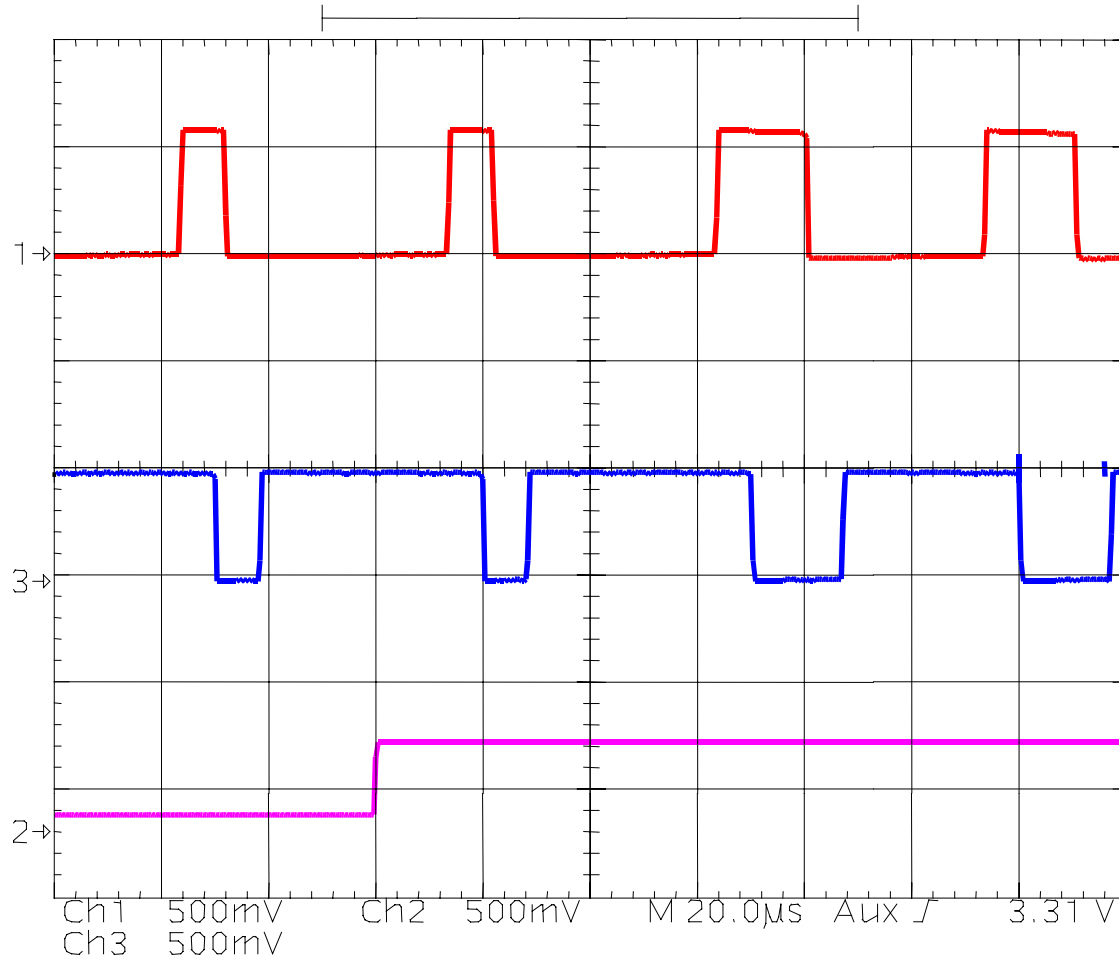

**S<sub>1-3</sub>**

**S<sub>2-4</sub>**

**M**

# Experimental results

**A prototype of the proposed converter was built to test the digital controller.**


## Converter Parameters

<b>Line voltage</b>	$U_g$	$110 \pm 10\%$	$V_{RMS}$
<b>Output power</b>	$P_o$	0.5	kW
<b>Switching frequency</b>	$f_{sw}$	20	kHz
<b>Input inductor</b>	$L_f$	1.8	mH
<b>DC link capacitor</b>	$C_f$	500	$\mu F$

# Experimental results

Tek Stop: 50.0kS/s

63 Acqs

 

**PF = 0.98**

**THD = 0.15**


**M = 0.3**

**$P_{out} = 0.3$  kW**

**$U_g$  40V/div**

**$i_g$  2A/div**

# Experimental results

 

**PF = 0.96**

**THD = 0.35**

**M = 0.5**

**$P_{out} = 0.45$  kW**


**$U_g$  40V/div**

**$i_g$  2A/div**

# Experimental results

Tek Stop: 50.0kS/s

377 Acqs

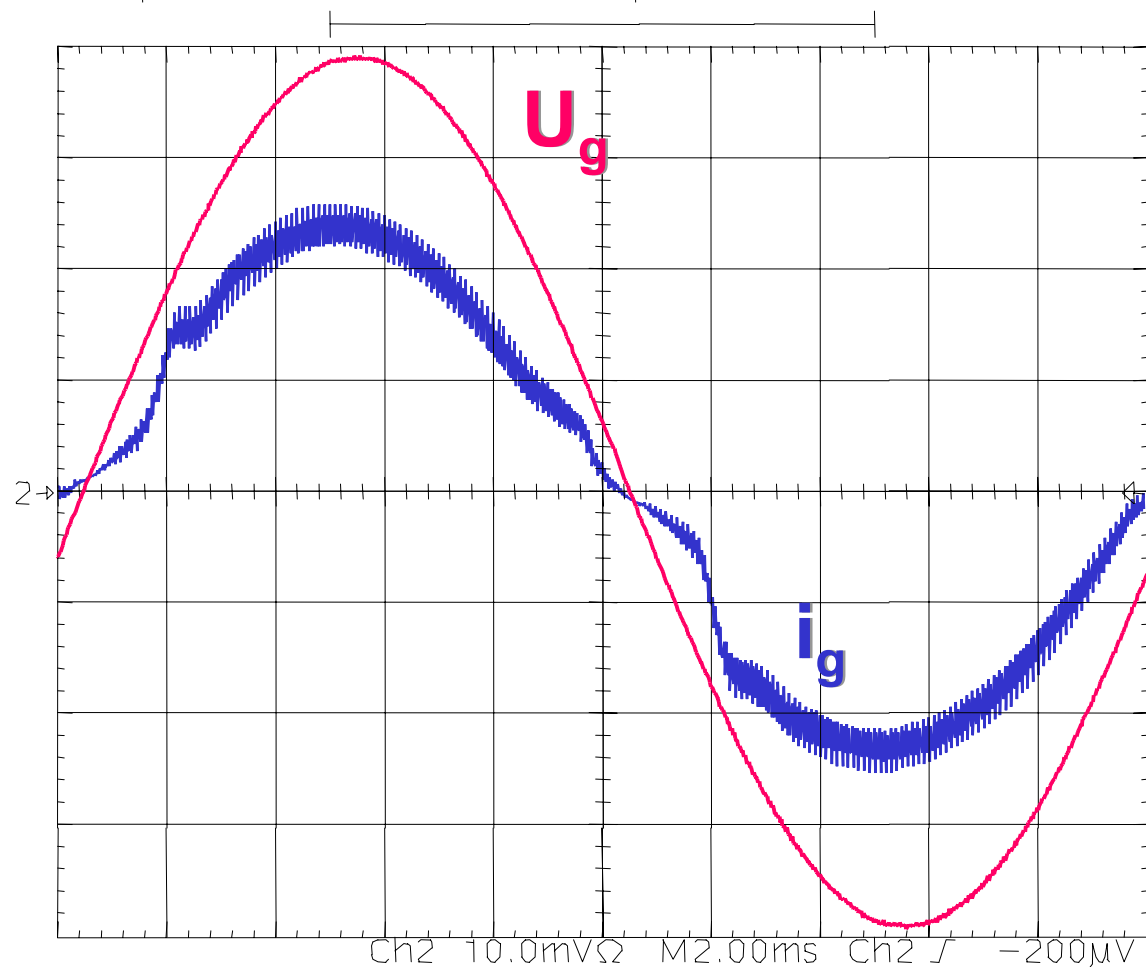

**PF = 0.97**

**THD = 0.25**

**M = 0.4**

**$P_{out} = 0.35$  kW**

**$U_g$  40V/div**

**$i_g$  2A/div**



# Reference

**L. Rossetto, S. Buso: “Digitally-Controlled Single-Phase AC/DC Integrated PWM Converter”, IEEE IAS Annual Meeting 2001, in press.**