

LISTA 3 - EE530

①

DADOS:

3) (1) $V_T = 26 \text{ mV}$

(2) $I_{C1} = I_{C2}$

(3) $V_{BE1} = V_{BE2} = 20 \text{ mV}$

$$I_C \approx \frac{A_{EQ} D_n n_i^2}{N_E W_B} \cdot e^{\frac{V_{BE}}{V_T}}$$

De (2)

$$\frac{A_{E1} (q \cdot D_n \cdot n_i^2)}{N_E W_B} \cdot e^{\frac{V_{BE1}}{V_T}} = A_{E2} \cdot \frac{q \cdot D_n \cdot n_i^2}{N_E W_B} \cdot e^{\frac{V_{BE2}}{V_T}}$$

$$\Rightarrow \frac{A_{E2}}{A_{E1}} = \frac{e^{V_{BE1}/V_T}}{e^{V_{BE2}/V_T}} = e^{(V_{BE1} - V_{BE2})/V_T} = e^{\frac{20 \text{ mV}}{26 \text{ mV}}}$$

$$\boxed{\frac{A_{E2}}{A_{E1}} \approx 2,16}$$

9) EDGE OF ACTIVE REGION $\rightarrow V_C = V_B$


$$V_{CC} = R_C I_C + V_C$$

$$V_{CC} = R_C I_S e^{V_B/V_T} + V_B$$

$$V_{CC} = 500 \cdot 5 \cdot 10^{-16} \cdot e^{V_B/26 \text{ mV}} + V_B = 2 \text{ V}$$


POR MÉTODOS NUMÉRICOS

$$\boxed{V_B \approx 760 \text{ mV}}$$

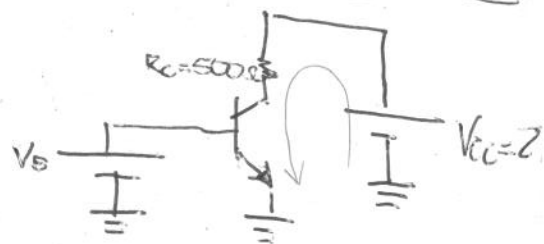

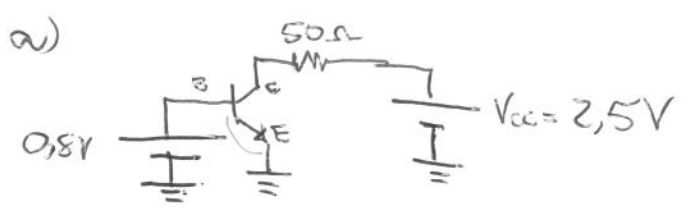4.21)

$V_A \rightarrow \infty \therefore r_o \rightarrow \infty \quad I_S = 8 \cdot 10^{-16} \text{ A} \quad \beta = 100$



$V_{BE} = 0,8V \rightarrow I_C = I_S \cdot e^{V_{BE}/V_T} \rightarrow I_C = 18,5 \text{ mA}$

$V_{CE} = V_{CC} - R_C I_C \rightarrow V_{CE} = 1,58V$

$\therefore$ modo ativo


$\rightarrow$ Parâmetros de pequenos sinais

$g_m = I_C / V_T = 710 \text{ mS}$

$r_{\pi} = \beta / g_m = 141 \Omega$

$r_o \rightarrow \infty$

DESENHO MODELO π -HÍBRIDO

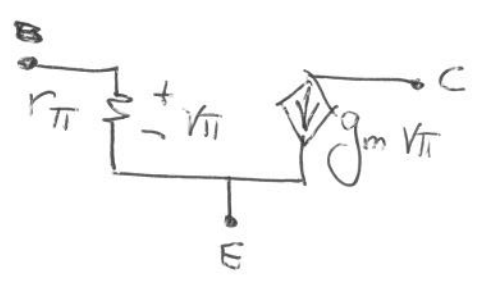

b) $I_B = 10 \mu\text{A}$

$I_C = \beta I_B = 1 \text{ mA}$

$V_{BE} = V_T \ln(I_C / I_S) = 724 \text{ mV}$

$V_{CE} = V_{CC} - R_C I_C = 1,5V$

$\therefore$ modo ativo

Para Pequenos Sinais

$g_m = I_C / V_T = 38,5$

$r_{\pi} = \beta / g_m = 2,6 \text{ K}\Omega$

$r_o \rightarrow \infty$

c) $I_E = \frac{V_{CC} - V_{BE}}{R_C} = \frac{1 + \beta}{\beta} I_C$

$I_C = \frac{\beta}{\beta + 1} \frac{V_{CC} - V_T \ln(I_C / I_S)}{R_C}$

$I_C = 1,74 \text{ mA}$

$V_{BE} = V_T \ln(I_C / I_S) = 733 \text{ mV}$

Modo ATIVO

$g_m = I_C / V_T = 38,5 \text{ mS}$

$r_{\pi} = \beta / g_m = 2,6 \text{ K}\Omega$

$r_o = \infty$

(29)



a) Sendo $I_C = 1\text{mA}$ $V_B = ?$

$$I_C = I_S e^{V_B/V_T} \rightarrow V_B = V_T \ln(I_C/I_S)$$

$$V_B = 26\text{mV} \ln(10^{-3}/3 \cdot 10^{-17})$$

$$\boxed{V_B \approx 809,6\text{mV}}$$

(3)

$$V_A = 5\text{V}$$

$$V_{CE} = 1,5\text{V}$$

$$I_C = 1\text{mA}$$

$$V_B = ?$$

$$I_C = I_S e^{V_B/V_T} \left(1 + \frac{V_{CE}}{V_A}\right)$$

$$10^{-3} = 3 \cdot 10^{-17} \cdot e^{V_B/V_T} \left(1 + \frac{1,5}{5}\right)$$

$$e^{V_B/V_T} = \frac{10^{-3}}{3,9}$$

$$V_B = 26\text{mV} \ln\left(\frac{10^{-3}}{3,9}\right) \approx 802,8\text{mV}$$

(37) $I_{S1} = 3I_{S2} = 6 \cdot 10^{-16}\text{A}$

$$I_1 = I_{S1} \cdot \exp\left(\frac{V_{BE1}}{V_T}\right) = 6 \cdot 10^{-16} \cdot \exp\left(\frac{300}{26}\right) \rightarrow I_1 = 6,155 \cdot 10^{-11}$$

$$I_2 = I_{S2} \exp\left(\frac{V_{BE2}}{V_T}\right) = 2 \cdot 10^{-16} \left(\frac{820}{26}\right) \rightarrow I_2 \approx 10\text{mA}$$

$$I_X = I_1 + I_2 \approx 10\text{mA}$$

4.44) $I_S = 3 \cdot 10^{-17} A$; $\beta = 100$ $V_A = \infty \rightarrow \beta \rightarrow \infty$

(4)

a) $I_B = 2 \mu A$

$I_C = \beta I_B = 200 \mu A$

$V_{EB} = V_T \ln(I_C / I_S) = 768 mV$

$V_{EC} = V_{CC} - I_E \cdot (2K) = V_{CC} - \left(\frac{1+\beta}{\beta} \right) I_C \cdot (2K) = 2,1V$

∴ MODO ATIVO

$g_m = I_C / V_T = 7,69 mS$

$r_{\pi} = \beta / g_m = 13 K\Omega$

b) $I_E = \frac{V_{CC} - V_{EB}}{5K} \rightarrow \left(\frac{1+\beta}{\beta} \right) I_C = \frac{V_{CC} - V_T \ln(I_C / I_S)}{5K}$

∴ $I_C = 390 \mu A$

$V_{EB} = 782 mV$

$V_{EC} = V_{EB} = 782 mV$

MODO DIRETO

$g_m = I_C / V_T = 13,1 mS$

$r_{\pi} = \beta / g_m = 7,64 K\Omega$

c) $I_E = \frac{1+\beta}{\beta} I_C = 0,5 mA \rightarrow I_C = 495 \mu A$

$I_C = 495 \mu A$

$V_{EB} = 971 mV \rightarrow \text{FORMULA}$

$V_{EC} = V_{EB} = 971 mV$

CONT DO ITEM "C"

$g_m = \frac{I_C}{V_T} = 19 mS$

$r_{\pi} = \beta / g_m = 5,25 K$