

$$5.7) \beta = 100 \quad I_S = 6 \cdot 10^{-16} \text{ A} \quad V_A = \infty$$

$$a) \quad V_{CC} - 100K \cdot I_B = V_{BE} = V_T \ln(I_C/I_S)$$

$$V_{CC} - 100K \cdot \frac{1}{\beta} I_C = V_T \ln(I_C/I_S)$$

$$\boxed{I_C = 1,754 \text{ mA}}$$

$$V_{BE} = V_T \ln(I_C/I_S) = 796 \text{ mV}$$

$$V_{CE} = V_{CC} - 500 \cdot I_C = 1,62 \text{ V} \quad \therefore \text{forward active}$$

$$b) \quad I_{E1} = I_{E2} \Rightarrow V_{BE1} = V_{BE2} !$$

$$V_{CC} - I_{B1}(100K) = 2V_{BE1}$$

$$V_{CC} - \frac{1}{\beta} I_{C1}(100K) = 2V_T \ln(I_C/I_S)$$

$$I_{C1} = I_{C2} = 1,035 \text{ mA}$$

$$V_{BE1} = V_{BE2} = 733 \text{ mV}$$

$$V_{CE1} = V_{CC} - I_C(1K) - V_{CE2} = 733 \text{ mV}$$

Q_1 e $Q_2 \rightarrow$ BORDA DA REGIÃO DE SATURAÇÃO

$$c) \quad V_{CC} - I_B(100K) = V_{BE} + 0,5$$

$$V_{CC} - \frac{I_C}{\beta}(100K) = V_T \ln(I_C/I_S) + 0,5 \text{ V} \rightarrow I_C = 1,262 \text{ mA}$$

$$V_{BE} = 738 \text{ mV}$$

$$V_{CE} = V_{CC} - I_C(1K) - 0,5 = 738 \text{ mV}$$

BORDA DA REGIÃO DE SATURAÇÃO

$$11) \beta = 100 \quad I_S = 6 \cdot 10^{-16} \text{ A} \quad V_A = \infty$$

(2)

a) $V_{CE} \geq V_{BE}$ para garantir modo ativo de operação

$$V_{CC} - I_C(2K) \geq V_{BE}$$

$$V_{CC} - I_C(2K) \geq V_T \ln(I_C/I_S)$$

$$\therefore I_C \leq 886 \mu\text{A}$$

$$\frac{V_{CC} - V_{BE}}{R_B} - \frac{\overset{V_T \ln(I_C/I_S)}{V_{BE}}}{3K} = I_B = \frac{I_C}{\beta}$$

$$R_B \left(\frac{I_C}{\beta} + \frac{V_T \ln(I_C/I_S)}{3K} \right) = V_{CC} - V_T \ln(I_C/I_S)$$

$$R_B = \frac{V_{CC} - V_T \ln(I_C/I_S)}{\frac{I_C}{\beta} + \frac{V_T \ln(I_C/I_S)}{3K}} \rightarrow \boxed{R_B \geq 7,04 K\Omega}$$

$$b) \frac{V_{CC} - V_{BE}}{R_B} - \frac{V_{BE}}{3K} = I_B = I_C/\beta$$

$$\therefore I_C = \beta \cdot \frac{V_{CC} - V_T \ln(I_C/I_S)}{R_B} - \beta \cdot \frac{V_T \ln(I_C/I_S)}{3K}$$

$$I_C = 1,19 \text{ mA}$$


$$V_{BE} = 735 \text{ mV}$$

$$V_{CE} = V_{CC} - I_C(2K) = 215 \text{ mV}$$

$$V_{BC} = V_{BE} - V_{CE} = 520 \text{ mV}$$

12) $\beta = 100$ e $V_A = \infty$

(3)

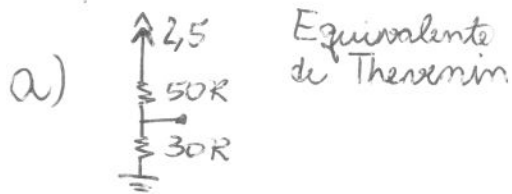

$$V_{TH} = 2,5 \cdot \frac{30}{30+50} = 0,9375V$$

$$R_{TH} = \frac{30 \cdot 50}{30+50} \cdot 1K = 18,75K \Omega$$

$$I_C = 0,5mA \rightarrow I_B = \frac{I_C}{\beta} = 0,005mA$$

$$I_B = \frac{V_{TH} - V_{BE}}{R_{TH}} \rightarrow V_{BE} = V_{TH} - I_B \cdot R_{TH} = 0,84375$$

$$I_C = I_S \cdot e^{V_{BE}/V_T} \Rightarrow I_S = I_C / e^{V_{BE}/V_T} = 4,03 \cdot 10^{-15} mA$$

b) $V_{BE} = V_{CE}$

$$V_{CE} = 2,5 - I_C(3K) \quad I_C = \beta I_B = \beta \left(\frac{V_{TH} - V_{BE}}{R_{TH}} \right)$$

$$V_{BE} = 2,5 - \beta \left(\frac{V_{TH} - V_{BE}}{R_{TH}} \right) \cdot 3K$$

$$\therefore V_{BE} = 0,83V$$

$$I_S = \frac{I_C}{\left(e^{V_{BE}/V_T} \right)} = \frac{\beta \cdot \left(\frac{V_{TH} - V_{BE}}{R_{TH}} \right)}{e^{V_{BE}/V_T}} = 7,84 \cdot 10^{-15} mA$$

$$17) \beta = 100 \quad I_S = 10^{-17} \text{ A} \quad V_A = \infty$$

④

$$V_{CE} > V_{BE} \rightarrow V_{CC} - I_C R_C$$

$$I_C \leq 833 \mu\text{A}$$

$$\frac{V_{CC} - V_{BE} - I_E R_E}{30 \text{ K}} - \frac{(V_{BE} + I_E R_E)}{R_Z} = I_B = I_C / \beta$$

$$R_Z = \frac{V_{BE} + I_E R_E}{\frac{V_{CC} - V_{BE} - I_E R_E}{30 \text{ K}} - \frac{I_C}{\beta}}$$

substituindo V_{BE} por $V_T \ln(I_C / I_S)$

$$\boxed{R_Z \leq 20,66 \text{ K}\Omega}$$

$$22) I_S = 6 \cdot 10^{-16} \text{ A} \quad \beta = 100 \quad V_A = \infty$$

$$V_{CC} - \textcircled{I_E} \cdot 500 - I_B \cdot 20 - I_E \cdot 400 = V_{BE}$$

$$V_{CC} - \frac{1+\beta}{\beta} \cdot I_C (500 + 400) - \frac{1}{\beta} \cdot I_C (20 \text{ K}) = V_T \ln(I_C / I_S)$$

$$I_C = 1,584 \text{ mA}$$

$$V_{BE} = V_T \ln(I_C / I_S) = 754 \text{ mV}$$

$$V_{CE} = V_{CC} - \textcircled{I_E} \cdot 500 - I_E \cdot 400 = V_{CC} - \frac{1+\beta}{\beta} \cdot I_C (500 + 400) = 1,06 \text{ V}$$

MODO ATIVO

31)

⑤

$$\frac{V_{BC} + I_C(5K)}{10K} - \frac{(V_{CC} - V_{BC} - I_C \cdot 5K)}{10K} = I_B = \frac{I_C}{\beta}$$

$$\Rightarrow V_{BC} = 300mV$$

$$I_C = 194\mu A$$

$$V_{EB} = V_T \ln(I_C/I_S) = 682mV$$

$$V_{CC} - \overset{\downarrow}{I_E} R_E - I_C \cdot 5K = V_{EC} = V_{EB} + 300mV$$

$$V_{CC} - \left[\frac{(1+\beta)}{\beta} \cdot I_C \right] R_E - I_C(5K) = V_{EB} + 300mV$$

$$\boxed{R_E = 2,776 K\Omega}$$

Caso R_E for reduzido à metade $\rightarrow R_E = 1,388 K\Omega$

$$\frac{V_{CC} - I_E R_E - V_{EB}}{10K} - \frac{V_{CC} - (V_{CC} - I_E R_E - V_{EB})}{10K} = I_B = \frac{I_C}{\beta}$$

$$I_C = \beta \cdot \frac{V_{CC} - \left(\frac{1+\beta}{\beta} \right) I_C \cdot R_E - V_T \ln(I_C/I_S)}{10K} - \beta \cdot \frac{V_{CC} - (V_{CC} - \frac{1+\beta}{\beta} I_C R_E - V_T \ln(I_C/I_S))}{10K}$$

$$I_C = 364\mu A$$

$$V_{EB} = 698\mu V$$

$$V_{EC} = 164\mu V$$

SATURADO

5.46

Resposta:

(a)

$$A_v = -\frac{R_1 + \frac{1}{g_{m2}}||r_{\pi 2}}{\frac{1}{g_{m1}} + R_E}$$

$$R_{in} = r_{\pi 1} + (1 + \beta_1)R_E$$

$$R_{out} = R_1 + \frac{1}{g_{m2}}||r_{\pi 2}$$

(b)

$$A_v = -\frac{R_C}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}||r_{\pi 2}}$$

$$R_{in} = r_{\pi 1} + (1 + \beta_1)\left(\frac{1}{g_{m2}}||r_{\pi 2}\right)$$

$$R_{out} = R_C$$

(c)

$$A_v = -\frac{R_C}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}||r_{\pi 2}}$$

$$R_{in} = r_{\pi 1} + (1 + \beta_1)\left(\frac{1}{g_{m2}}||r_{\pi 2}\right)$$

$$R_{out} = R_C$$

(d)

$$A_v = -\frac{R_C}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}||r_{\pi 2} + \frac{R_B}{1+\beta_1}}$$

$$R_{in} = R_B + r_{\pi 1} + (1 + \beta_1)\left(\frac{1}{g_{m2}}||r_{\pi 2}\right)$$

$$R_{out} = R_C$$

(e)

$$A_v = -\frac{R_C}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}||r_{\pi 2} + \frac{R_B}{1+\beta_1}}$$

$$R_{in} = R_B + r_{\pi 1} + (1 + \beta_1)\left(\frac{1}{g_{m2}}||r_{\pi 2}\right)$$

$$R_{out} = R_C$$

5.52

Resposta:

(a) $A_v = -8, 60.$ (b) $A_v = -21, 54.$ (c) $A_v = -14, 98.$

5.55

Resposta:

(a)

$$A_v = g_{m1} \left(R_C + \frac{1}{g_{m2}} || r_{\pi 2} \right)$$

(b)

$$A_v = g_{m1} r_{\pi 2}$$

(c)

$$A_v = g_{m1} \left(R_C + \frac{1}{g_{m3}} || r_{\pi 3} \right)$$

(d)

$$A_v = g_{m1} \left(R_C + \frac{1}{g_{m3}} || r_{\pi 3} \right) \left(\frac{R_E || \frac{1}{g_{m1}}}{R_E || \frac{1}{g_{m1}} + R_S} \right)$$

5.56

Resposta:

(a)

$$R_{in} = \frac{r_{\pi 1} + \frac{1}{g_{m2}} || r_{\pi 2}}{1 + \beta_1}$$

(b)

$$R_{in} = \frac{r_{\pi 1} + R_2}{1 + \beta_1}$$

(c)

$$R_{in} = \frac{r_{\pi 1} + R_2 || \frac{1}{g_{m2}} || r_{\pi 2}}{1 + \beta_1}$$

(d)

$$R_{in} = \frac{r_{\pi 1} + R_2 || r_{\pi 2}}{1 + \beta_1}$$

5.58

Resposta:

(a) $I_C = 1,02 \text{ mA}$, $V_{BE} = 725 \text{ mV}$ e $V_{CE} = 1,07 \text{ V}$.(b) $A_v = 39,2$, $R_{in} = 23,9 \text{ } \Omega$ e $R_{out} = 1 \text{ k}\Omega$.**5.68**

Resposta:

(a)

$$A_v = 1$$

$$R_{in} = \infty$$

$$R_{out} = \frac{1}{g_{m1}} || r_{\pi 1}$$

(b)

$$A_v = \frac{\frac{1}{g_{m2}} || r_{\pi 2}}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}} || r_{\pi 2}}$$

$$R_{in} = r_{\pi 1} + (1 + \beta_1) \left(\frac{1}{g_{m2}} \|r_{\pi 2}\| \right)$$

$$R_{out} = \frac{1}{g_{m1}} \|r_{\pi 1}\| \frac{1}{g_{m2}} \|r_{\pi 2}\|$$

(c)

$$A_v = \frac{\frac{r_{\pi 2} + R_S}{1 + \beta_2}}{\frac{1}{g_{m1}} + \frac{r_{\pi 2} + R_S}{1 + \beta_2}}$$

$$R_{in} = r_{\pi 1} + (1 + \beta_1) \left(\frac{r_{\pi 2} + R_S}{1 + \beta_2} \right)$$

$$R_{out} = \frac{1}{g_{m1}} \|r_{\pi 1}\| \left(\frac{r_{\pi 2} + R_S}{1 + \beta_2} \right)$$

(d)

$$A_v = \frac{R_E + \frac{1}{g_{m2}} \|r_{\pi 2}\|}{\frac{1}{g_{m1}} + R_E + \frac{1}{g_{m2}} \|r_{\pi 2}\|}$$

$$R_{in} = r_{\pi 1} + (1 + \beta_1) \left(R_E + \frac{1}{g_{m2}} \|r_{\pi 2}\| \right)$$

$$R_{out} = \frac{1}{g_{m1}} \|r_{\pi 1}\| \left(R_E + \frac{1}{g_{m2}} \|r_{\pi 2}\| \right)$$

(e)

$$A_v = \frac{\frac{1}{g_{m2}} \|r_{\pi 2}\|}{\frac{1}{g_{m1}} + R_E + \frac{1}{g_{m2}} \|r_{\pi 2}\|}$$

$$R_{in} = r_{\pi 1} + (1 + \beta_1) \left(R_E + \frac{1}{g_{m2}} \|r_{\pi 2}\| \right)$$

$$R_{out} = \left(\frac{1}{g_{m1}} \|r_{\pi 1} + R_E\| \right) \left\| \frac{1}{g_{m2}} \|r_{\pi 2}\| \right\|$$

5.69

Resposta:

(a)

$$r_{\pi 1} + (1 + \beta_1) r_{\pi 2}$$

(b)

$$\frac{r_{\pi 2} + \frac{1}{g_{m1}} \|r_{\pi 1}\|}{1 + \beta_2}$$

(c)

$$\beta_1 + \beta_2(1 + \beta_1)$$

5.71

Resposta: $A_v = 0,84$.

5.80

Resposta: $R_1 = 4,41 \text{ k}\Omega$, $R_2 = 3,62 \text{ k}\Omega$, $R_C = 500 \text{ }\Omega$ e $R_E = 92 \text{ }\Omega$.

5.83

Resposta: $R_1 = 29,33 \text{ k}\Omega$, $R_2 = 20,83 \text{ k}\Omega$, $R_C = 1 \text{ k}\Omega$, $R_E = 495 \text{ }\Omega$ e $C_B = 1,58 \text{ }\mu\text{F}$.

5.88

Resposta: $R_1 = 220,77 \text{ k}\Omega$.