
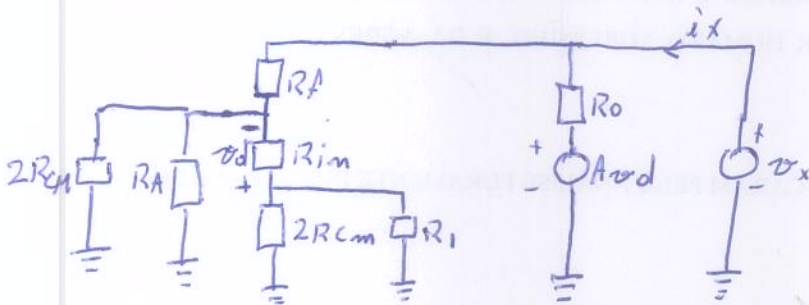
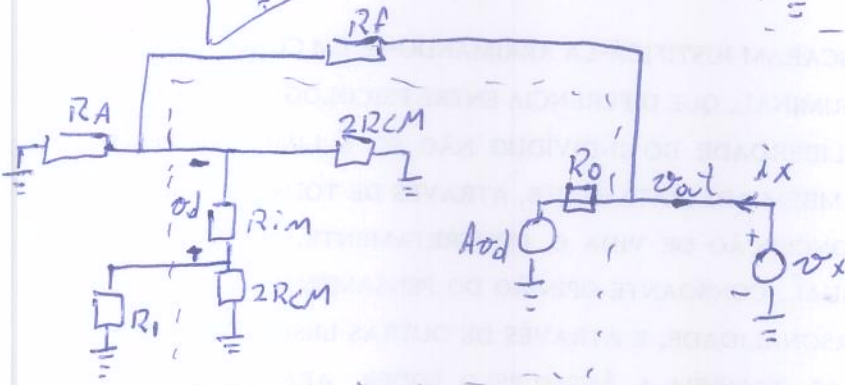


# Aula 12C

\* Resistência de saída (inversor e não o inversor)


→ Valores do 741:

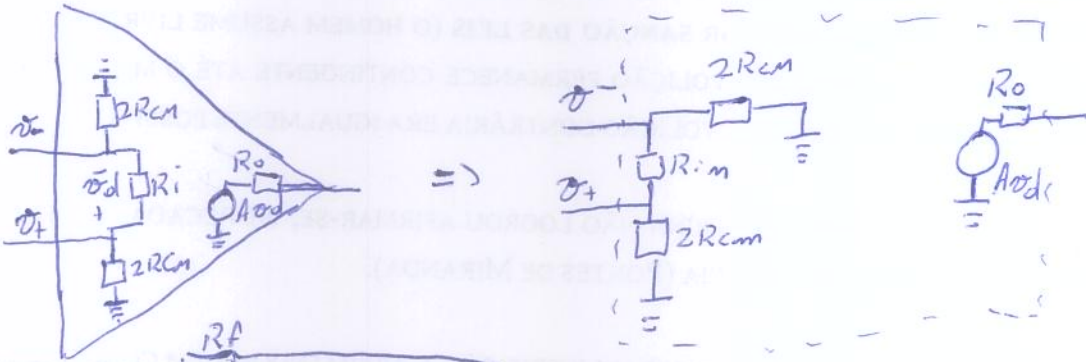- $R_i = 2M\Omega$
- $2R_{cm} = 400M\Omega$
- $R_o = 75\Omega$




$$R_i' = (2R_{cm} || R_i)$$

$$R_A' = (2R_{cm} || R_A)$$

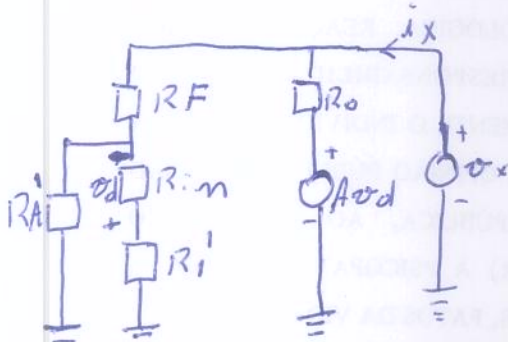

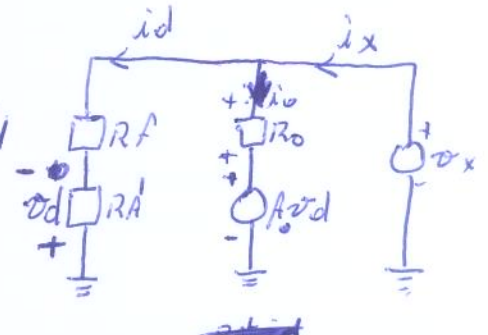$R_i \gg R_i' \Rightarrow R_i' \approx R_i$   
 $R_A' \ll R_i + R_i' \Rightarrow R_A' \approx R_A$



$$i_d = \frac{v_x}{R_A' + R_A}$$

$$v_d = -\frac{v_x}{R_A' + R_A} \cdot R_A'$$

$$i_o = \frac{v_x - A v_d}{R_o} \Rightarrow i_o = \frac{1}{R_o} \left[ v_x - A \left( -\frac{v_x}{R_A' + R_A} \cdot R_A' \right) \right]$$

$$i_o = \frac{1}{R_o} \left[ v_x + \frac{A v_x \cdot R_A'}{R_A' + R_A} \right]$$

$$i_o = \frac{v_x}{R_o} \left[ 1 + \frac{A \cdot R_A'}{R_A' + R_A} \right]$$

obs: Normalmente  $i_o \gg i_d \Rightarrow i_x \approx i_o$

$$\therefore R_{out} = \frac{R_o}{1 + \frac{A R_A'}{R_A' + R_A}} \sim \text{SAVANT}$$

$$R_{out} = \frac{R_o}{\frac{R_A' + R_A' + A R_A'}{R_A' R_A'}} \Rightarrow R_{out} = \frac{R_o (R_A' + R_A')}{R_A' (1+A) + R_A'} \xrightarrow{R_A' (1+A) \gg R_A'} R_{out} = \frac{R_o}{A} \left( 1 + \frac{R_A'}{R_A'} \right)$$

$$\rightarrow \text{REMEMBRE} \Rightarrow R_{out} = \frac{R_o}{A} \left( 1 + \frac{R_A'}{R_A'} \right) \sim \text{SAVANT}$$

$\hookrightarrow$  A realimentação diminui a resistência de saída.

$$i_x = i_d + i_o \Rightarrow i_x = \frac{v_x}{R_A' + R_A} + \frac{v_x}{R_o} \left[ 1 + \frac{A R_A'}{R_A' + R_A} \right] \Rightarrow i_x = v_x \left[ \frac{1}{R_A' + R_A} + \frac{1}{R_o} \left( 1 + \frac{A R_A'}{R_A' + R_A} \right) \right]$$



$$i_x = v_x \cdot \left[ \frac{R_o + (R_A' + R_A) + A R_A'}{R_o (R_A' + R_A)} \right] \Rightarrow R_{out} = \frac{v_x}{i_x} = \frac{R_o (R_A' + R_A)}{R_o + R_A' (1+A) + R_A'}$$

$$(R_A' (1+A)) \gg (R_o + R_A') \Rightarrow R_{out} = \frac{R_o}{A} \left( 1 + \frac{R_A'}{R_A'} \right)$$

$$\Rightarrow R_{out} = \frac{R_o \cdot A v_i}{A}$$


$\hookrightarrow$  A realimentação diminui  $R_{out}$

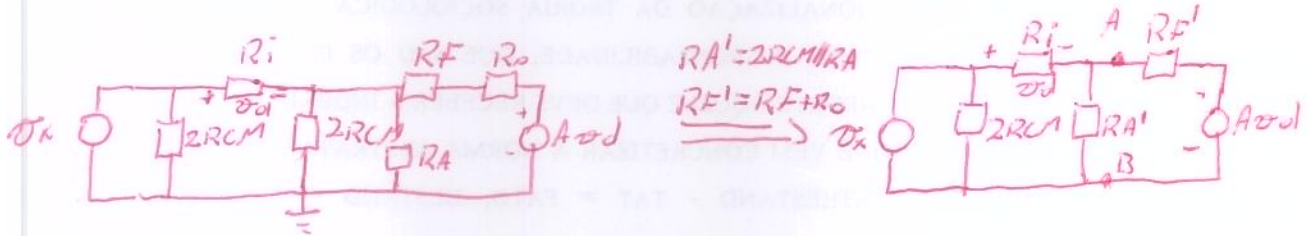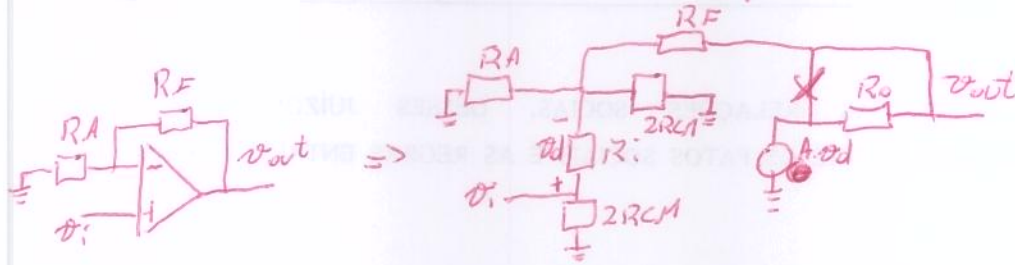\* Resistência de entrada - Amp. <sup>mão</sup> inverter



$$RA' = 2R_{CM} \parallel RA$$

$$RF' = RF + R_o$$

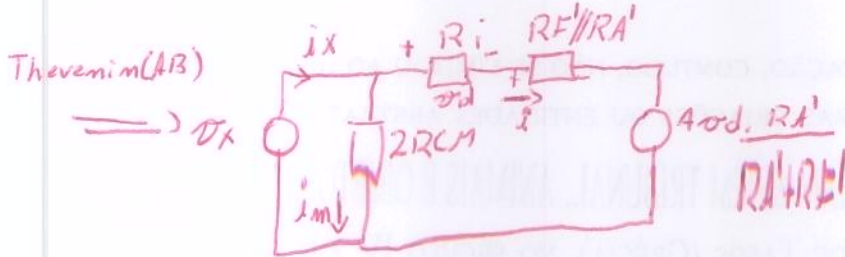

$$v_d = v_x - \left( \frac{v_d + A v_d R A'}{R A' + R F'} \right) \Rightarrow v_d = v_x \left[ \frac{v_d \cdot (R F' \parallel R A') + A v_d R A'}{R_i} \right]$$

$$v_x = \left( 1 + \frac{R F' \parallel R A'}{R_i} + \frac{A R A'}{R F' + R A'} \right) v_d = \dots$$

$$i = \frac{v_d}{R_i} = \frac{v_x}{R_i} \cdot \frac{1}{1 + \frac{R_F' // R_A' + A R_A'}{R_i} + \frac{A R_A' R_i}{R_F' + R_A'}} = \frac{v_x}{R_i + R_F' // R_A' + \frac{A R_A' R_i}{R_F' + R_A'}}$$

$$i = \frac{v_x}{R_i \left( 1 + \frac{A R_A'}{R_F' + R_A'} \right) + R_F' // R_A'}$$

$$i_x = i + i_m \Rightarrow i_x = \frac{v_x}{R_i \left( 1 + \frac{A R_A'}{R_F' + R_A'} \right) + R_F' // R_A'} + \frac{v_x}{2 R_{CM}}$$

$$R_{out} = \frac{v_x}{i_x} = R_i // R_{in}$$

$$\frac{i_x}{v_x} = \frac{R_{out}^{-1}}{R_i} = \frac{1}{R_F' // R_A' + R_i \left( 1 + \frac{A R_A'}{R_F' + R_A'} \right)} + \frac{1}{2 R_{CM}}$$

$$R_{out} = 2 R_{CM} // \left[ R_F' // R_A' + R_i \left( 1 + \frac{A R_A'}{R_F' + R_A'} \right) \right]$$

$$R_{out} = 2 R_{CM} // \left[ \frac{R_F' \cdot R_A' + R_i + R_i \cdot A R_A'}{R_F' + R_A'} \right]$$


$$\Downarrow R_i \cdot A R_A' \gg (R_F' \cdot R_A' + R_i)$$

$$R_{out} = 2 R_{CM} // \left[ \frac{R_i \cdot A \cdot R_A'}{R_F' + R_A'} \right]$$

$$R_{out} = 2 R_{CM} // \frac{R_i \cdot A}{1 + \frac{R_F'}{R_A'}} \Rightarrow R_{in} \approx 2 R_{CM} // \frac{R_i \cdot A}{A \sigma_i}$$

$R_F' \gg R_o$   
 $R_A \ll R_{CM}$

# \* Circuito Limitador de amplitude

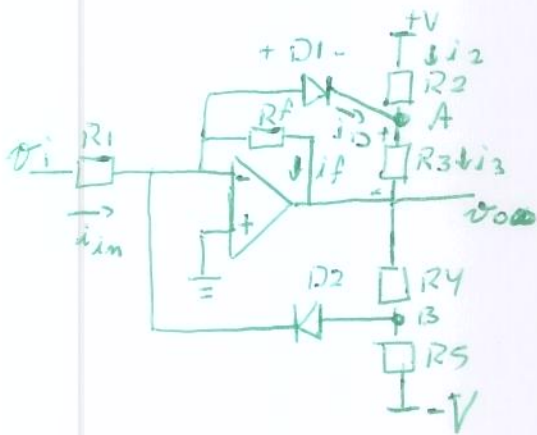

•  $v_i = 0 \Rightarrow v_o = 0 \Rightarrow V_A > 0 \text{ e } V_B < 0 \Rightarrow D_1 \text{ e } D_2 \text{ abertos}$

•  $v_o = -\frac{R_f}{R_1} v_i$   
↳ parte linear

•  $v_o \neq 0$

$\rightarrow V_A = V \cdot \frac{R_3}{R_2 + R_3} + v_o \cdot \frac{R_2}{R_2 + R_3}$  (Superposição: 1º termo  $v_o = 0$ , 2º termo  $V = 0$ )

$\rightarrow V_B = -V \frac{R_4}{R_4 + R_5} + v_o \frac{R_5}{R_4 + R_5}$

•  $v_i > 0 \Rightarrow v_o < 0 \Rightarrow v_B < 0 \Rightarrow D_2 \text{ aberto}$

$\rightarrow D_1 \text{ conduz quando } V_A = -V_{D_{on}}$

$-V_{D_{on}} = V \frac{R_3}{R_2 + R_3} + v_o \frac{R_2}{R_2 + R_3} \Rightarrow -V_{D_{on}}(R_2 + R_3) = V R_3 + v_o R_2$

$\Rightarrow v_o = -\frac{V_{D_{on}}(R_2 + R_3) - V R_3}{R_2}$

$\Rightarrow v_o = -V_{D_{on}} \left(1 + \frac{R_3}{R_2}\right) + V \frac{R_3}{R_2}$

$v_i = +\frac{R_1}{R_f} \left[ +V_{D_{on}} \left(1 + \frac{R_3}{R_2}\right) + V \frac{R_3}{R_2} \right]$

$\rightarrow$  Para  $D_1$  conduzindo ( $V_A = -V_{D_{on}}$ ) e ( $R_4 + R_5 = \text{carga}$ )

$i_{in} = \frac{v_i}{R_1} \quad | \quad i_{Rf} = -\frac{v_o}{R_f}$

$i_2 = \frac{V + V_{D_{on}}}{R_2}$

$i_3 = -\frac{v_o - V_{D_{on}}}{R_3}$

$i_D = i_3 - i_2 \Rightarrow i_D = -\frac{v_o}{R_3} - \frac{V_{D_{on}}}{R_3} - \frac{V}{R_2} - \frac{V_{D_{on}}}{R_2} \Rightarrow i_D = -\frac{v_o}{R_3} - K$

$i_{in} = i_{Rf} + i_D \Rightarrow i_{in} = -\frac{v_o}{R_f} - \frac{v_o}{R_3} - K \Rightarrow \frac{v_i}{R_1} = -v_o \left( \frac{1}{R_f} + \frac{1}{R_3} \right) - K$

$\frac{v_i}{R_1} = -v_o \frac{R_f + R_3}{R_f R_3} - K \Rightarrow v_o = -\frac{R_f R_3}{R_f + R_3} \frac{v_i}{R_1} - K$

•  $v_i < 0 \Rightarrow v_o > 0 \Rightarrow V_A > 0 \Rightarrow I_D$  aberto

$\rightarrow I_{D2}$  conduz ~~para~~ quando  $V_{I3} = V_{Dom}$

$$V_{Dom} = -V \frac{R_4}{R_4 + R_5} + v_o \frac{R_5}{L + R_4 + R_5}$$

$$v_{oL+} = V_{Dom} \left( 1 + \frac{R_4}{R_5} \right) + V \frac{R_4}{R_5}$$

$$v_{iL+} = -\frac{R_1}{R_F} \left[ V_{Dom} \left( 1 + \frac{R_4}{R_5} \right) + V \frac{R_4}{R_5} \right]$$

$\rightarrow$  Para  $I_{D2}$  conduzindo ( $V_{I3} = V_{Dom}$ ) e ( $R_3 = R_4 = \text{carga}$ )

$$v_o = -\frac{R_F \parallel R_4}{R_1} v_i - \frac{R_F \parallel R_4}{R_1} K' \sim$$

