
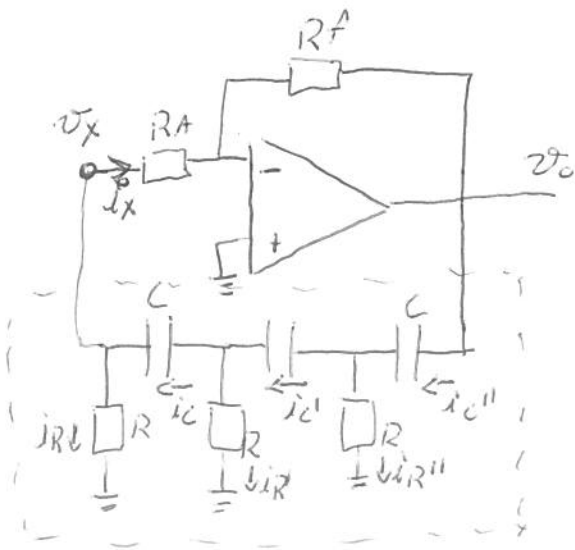
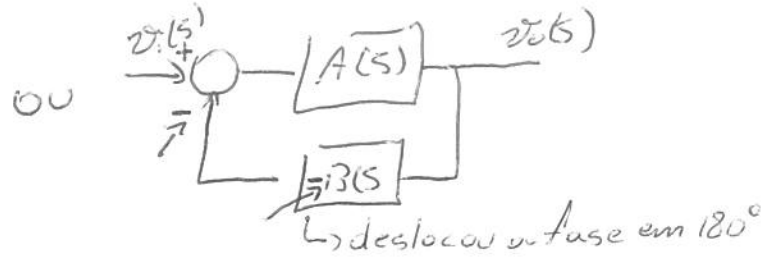


• Oscilador de deslocamento de fase

obs: Realimentação Positiva

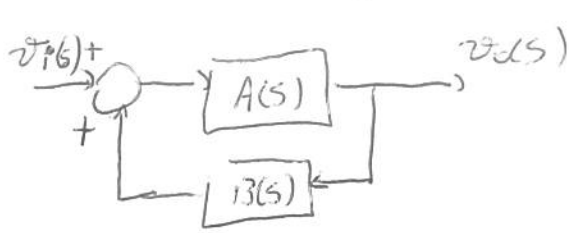


$$\bullet \frac{i_x}{v_x - 0} = \frac{0 - v_o}{R_F} \Rightarrow \frac{v_o}{v_x} = -\frac{R_F}{R_A} \rightarrow A(s)$$

FALTA DETERMINAR B(S)

$$B(s) = \frac{v_x(s)}{v_o(s)}$$

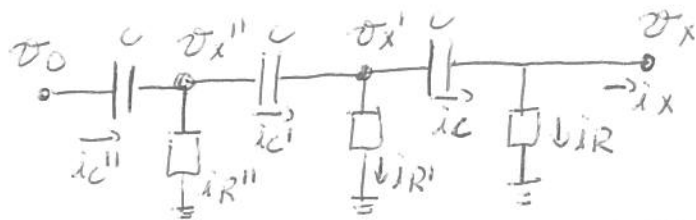obs. $A(s) = \frac{v_o}{v_x}$; $B(s) = \frac{v_x}{v_o} \Rightarrow L(s) = \frac{v_o}{v_x} \cdot \frac{v_x}{v_o} \Rightarrow L(s) = 1$
 ↳ condição de oscilação



Assuming $i_x \ll i_R \Rightarrow \boxed{RA \gg iR}$

$v_{x'} = v_x + \frac{i_c}{sC} \Rightarrow v_{x'} = \frac{i_R}{sC} + v_x \Rightarrow v_{x'} = v_x + \frac{v_x}{iR} \cdot \frac{1}{sC} \Rightarrow \boxed{v_{x'} = v_x \left(1 + \frac{1}{RSC} \right)}$

$v_{x''} = v_{x'} + \frac{i_c'}{sC} \Rightarrow v_{x''} = v_x \left(1 + \frac{1}{RSC} \right) + \frac{1}{sC} \left(\frac{v_{x'}}{iR} + i_c \right) \Rightarrow v_{x''} = v_x \left(1 + \frac{1}{RSC} \right) + \frac{1}{sC} \left[\frac{v_x}{R} \left(1 + \frac{1}{RSC} \right) + \frac{v_x}{R} \right]$

$v_{x''} = v_x \left\{ \left(1 + \frac{1}{RCS} \right) + \frac{1}{RCS} \left[\left(1 + \frac{1}{RCS} \right) + 1 \right] \right\} \Rightarrow v_{x''} = v_x \left\{ \frac{RCS+1}{RCS} + \frac{2RCS+1}{(RC)^2 S^2} \right\}$

$v_{x''} = v_x \frac{(RC)^2 S^2 + RCS + 2RCS + 1}{(RC)^2 S^2}$

$v_{x''} = v_x \frac{(RC)^2 S^2 + 3RCS + 1}{(RC)^2 S^2}$

$v_0 = v_{x''} + \frac{i_c''}{sC} \Rightarrow v_0 = v_x \frac{(RC)^2 S^2 + 3RCS + 1}{(RC)^2 S^2} + \frac{1}{sC} \left(\frac{v_{x''}}{iR} + i_c' \right)$

$i_c' = i_c + i_{R'} = \frac{v_x}{R} + \frac{v_{x'}}{R} = \frac{v_x}{R} + \frac{1}{R} v_x \left(\frac{RCS+1}{RCS} \right) = \frac{v_x}{R} \left(1 + \frac{RCS+1}{RCS} \right)$

$i_c' = \frac{v_x}{R} \cdot \left(\frac{2RCS+1}{RCS} \right)$

$\rightarrow v_0 = v_x \frac{(RC)^2 S^2 + 3RCS + 1}{(RC)^2 S^2} + \frac{1}{sC} \left[\frac{v_x}{R} \frac{(RC)^2 S^2 + 3RCS + 1}{(RC)^2 S^2} + \frac{v_x}{R} \frac{(2RCS+1)}{RCS} \right]$

$v_0 = v_x \left\{ \frac{(RC)^2 S^2 + 3RCS + 1}{(RC)^2 S^2} + \frac{1}{RCS} \left[\frac{(RC)^2 S^2 + 3RCS + 1}{(RC)^2 S^2} + \frac{2RCS + 1}{RCS} \right] \right\}$

$v_0 = v_x \left\{ \frac{(RC)^2 S^2 + 3RCS + 1}{(RC)^2 S^2} + \frac{3(RC)^2 S^2 + 4RCS + 1}{(RC)^3 S^3} \right\}$

$v_0 = v_x \cdot \left\{ \frac{(RC)^3 S^3 + 3(RC)^2 S^2 + RCS + 3(RC)^2 S^2 + 4RCS + 1}{(RC)^3 S^3} \right\}$

$\frac{v_x}{v_0} = \frac{(RC)^3 S^3}{(RC)^3 S^3 + 6(RC)^2 S^2 + 5RCS + 1} \rightarrow B(S)$

• $L(s) = A(s), B(s) = 1$

$$L(s) = \frac{-RF}{RA} \cdot \frac{\tau^3 s^3}{\tau^3 s^3 + 6\tau^2 s^2 + 5\tau s + 1} = 1$$

$$L(j\omega_0) = \frac{-RF}{RA} \cdot \frac{-\tau^3 j\omega_0^3}{-\tau^3 \omega_0^3 - 6\tau^2 \omega_0^2 j + 5\tau j\omega_0 + 1} = 1$$

$$L(j\omega_0) = \frac{-RF}{RA} \cdot \frac{\tau^3 \omega_0}{\tau^3 \omega_0^3 - 6\tau^2 \omega_0^2 j - 5\tau \omega_0 + j} = 1$$

$$L(j\omega_0) = \frac{-RF}{RA} \cdot \frac{\tau^3 \omega_0^3}{j \cdot (1 - 6\omega_0^2 \tau^2) + (\omega_0^3 \tau^3 - 5\omega_0 \tau)} = 1$$

• $|L(j\omega_0)| = -1 \Rightarrow 1 - 6(\omega_0 \tau)^2 = 0 \Rightarrow \omega_0 = \frac{1}{\tau\sqrt{6}}$

• $|L(j\omega_0)| = 1 \Rightarrow \frac{-RF}{RA} \frac{\tau^3 \omega_0^3}{\omega_0^3 \tau^3 - 5\omega_0 \tau} = 1$

$$\frac{-RF}{RA} \cdot \frac{\tau^3 \left(\frac{1}{\tau\sqrt{6}}\right)^3}{\left(\frac{1}{\tau\sqrt{6}}\right)^3 \tau^3 - 5 \frac{1}{\tau\sqrt{6}} \tau} = 1 \Rightarrow \frac{-RF}{RA} \cdot \frac{\frac{1}{6\sqrt{6}}}{\frac{1}{6\sqrt{6}} - \frac{5}{\sqrt{6}}} = 1$$

$$\frac{-RF}{RA} \cdot \frac{\frac{1}{6\sqrt{6}}}{\frac{1 - 30}{6\sqrt{6}}} = 1 \Rightarrow \frac{RF}{RA} = 29$$