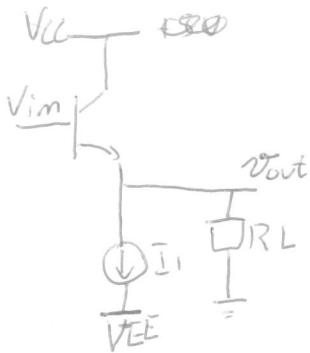


# \* Amplificadores de Potência (Seguidor de Emissor)

=> Eficiência ( $\eta$ ) -> entrada senoidal =>  $v_{in} = V_p \sin \omega t$

$$\eta = \frac{P_{out}}{P_{out} + P_{circ.}}$$

$\underbrace{\hspace{10em}}_{A_{\text{env}}}$



- $I_c \approx I_E = I_1 + \frac{v_{out}}{R_L} = I_1 + \frac{V_p \sin \omega t}{R_L}$
- $V_{CE} = V_{cc} - v_{out} = V_{cc} - V_p \sin \omega t$  (máxima excursão do sinal)

$$P_{circ. Q_1} = \frac{1}{T} \int_0^T I_c \cdot V_{CE} dt = \frac{1}{T} \int_0^T \left( I_1 + \frac{V_p \sin \omega t}{R_L} \right) (V_{cc} - V_p \sin \omega t) dt$$

$$P_{circ. Q_1} = \frac{1}{T} \int_0^T \left[ I_1 (V_{cc} - V_p \sin \omega t) + \frac{V_p \sin \omega t}{R_L} (V_{cc} - V_p \sin \omega t) \right] dt$$

$$P_{circ. Q_1} = \frac{1}{T} \left\{ \int_0^T I_1 \cdot V_{cc} dt - \int_0^T I_1 V_p \sin \omega t dt + \int_0^T \frac{V_{cc} V_p \sin \omega t}{R_L} dt - \int_0^T \frac{V_p^2 \sin^2 \omega t}{R_L} dt \right\}$$

$$P_{circ. Q_1} = \frac{1}{T} \left\{ I_1 V_{cc} \cdot T - \frac{V_p^2}{R_L} \int_0^T \frac{1 - \cos 2\omega t}{2} dt \right\}$$

$$P_{circ. Q_1} = \frac{1}{T} \left\{ I_1 V_{cc} \cdot T - \frac{V_p^2}{2 R_L} \left[ \int_0^T dt - \int_0^T \cos 2\omega t dt \right] \right\}$$

$$P_{circ. Q_1} = \frac{1}{T} \left\{ I_1 V_{cc} T - \frac{V_p^2}{2 R_L} [T - 0] \right\}$$

↳ máxima excursão do sinal

$$P_{circ. Q_1} = I_1 V_{cc} - \frac{V_p^2}{2 R_L}$$

Condição mínima

$$I_1 = \frac{V_p}{R_L}$$

$$P_{circ. Q_1} = I_1 \cdot V_{cc} - \frac{V_p I_1}{2}$$

$$P_{circ. Q_1} = I_1 \left( V_{cc} - \frac{V_p}{2} \right)$$

$$\xrightarrow{V_p = 0}$$

$$P_{circ. Q_1} = V_{cc} \cdot I_1$$

MAX

- $I_1$  pode ser gerada por meio de um transistor

$$P_{av I_1} = \frac{1}{T} \int_0^T I_1 \cdot \overbrace{(V_p \sin \omega t - V_{EE})}^{v_{out}} dt$$

$V_{I_1}$

$$\boxed{P_{av I_1} = -V_{EE} I_1} \quad \xrightarrow{V_{EE} = -V_{CC}} \quad \boxed{P_{av I_1} = V_{CC} I_1}$$

$L_s V_{CC} = 0$

- $P_{cinc} = P_{Q1} + P_{I_1} \Rightarrow \boxed{P_{cinc} = I_1 \left( 2V_{CC} - \frac{V_p}{2} \right)}$

- $P_{out} = P_{RL} \Rightarrow P_{av RL} = \frac{1}{T} \int_0^T \frac{(v_{out})^2}{RL} dt = \frac{1}{T} \int_0^T \frac{(V_p \sin \omega t)^2}{RL} dt = \frac{V_p^2}{RL T} \int_0^T \frac{(1 - \cos 2\omega t)}{2} dt$


$$P_{av out} = \frac{V_p^2}{2RL T} \cdot (T - 0) \Rightarrow \boxed{P_{av out} = \frac{V_p^2}{2RL}}$$

- $\eta = \frac{\frac{V_p^2}{2RL}}{\frac{V_p^2}{2RL} + I_1 \left( 2V_{CC} - \frac{V_p}{2} \right)}$

$$\underline{I_1 = \frac{V_p}{R_C}}, \quad \eta = \frac{\left( \frac{V_p}{2RL} \right)}{\left( \frac{V_p}{2RL} \right) + \frac{2 \cdot V_{CC} \cdot \frac{V_p}{R_C} - \frac{V_p^2}{2RL}}$$

$$\boxed{\eta = \frac{V_p}{4V_{CC}}}$$
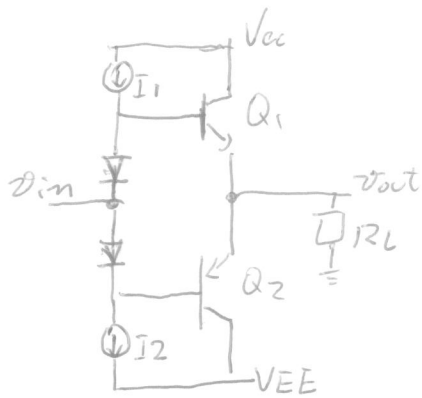
# # Amplificadores de Potência (Push-Pull)



- entrada senoidal  $\Rightarrow v_{in} = V_p \sin \omega t$
- $I_{Q1} = I_{Q2} \approx \phi$  /  $v_{out} = 0$
- Cada transistor conduz ~~em~~ apenas metade do ciclo
- $v_{out} = V_p \sin \omega t$ ;  $A \approx \approx 1$
- $I_{RL} = \frac{v_{out}}{R_L} = \frac{V_p \sin \omega t}{R_L}$   
 $\downarrow$   
 $I_C \approx I_E$

## # Q1 conduzindo

$$V_{CE} = V_{cc} - v_{out} = V_{cc} - V_p \sin \omega t$$

$$P_{a\text{os}Q1} = \frac{1}{T} \int_0^{T/2} V_{CE} \cdot I_C = \frac{1}{T} \int_0^{T/2} (V_{cc} - V_p \sin \omega t) \cdot \frac{V_p \sin \omega t}{R_L} dt$$

$$P_{a\text{os}Q1} = \frac{1}{T R_L} \left\{ \int_0^{T/2} V_{cc} V_p \sin \omega t dt - \int_0^{T/2} \frac{V_p^2 \sin^2 \omega t}{2} dt \right\}$$

$$P_{a\text{os}Q1} = \frac{1}{T R_L} \left\{ \frac{V_{cc} \cdot V_p}{\omega} \left( \frac{\cos \omega t}{\omega} \right) \Big|_0^{T/2} - \left[ \int_0^{T/2} \frac{V_p^2}{2} dt - \int_0^{T/2} \frac{\cos 2\omega t}{2} dt \right] \right\}$$

$$P_{a\text{os}Q1} = \frac{1}{T R_L} \left\{ \frac{-V_{cc} V_p}{\frac{2\pi}{T}} \left[ -\left( \frac{\cos 2\pi \cdot \frac{T}{2}}{2} - \cos \phi \right) \right] - \frac{V_p^2 \cdot T}{4} \right\}$$

$$P_{a\text{os}Q1} = \frac{1}{T R_L} \left\{ \frac{+V_{cc} V_p}{2\pi} - \frac{V_p^2 T}{4} \right\}$$

$$P_{a\text{os}Q1} = \frac{V_p}{R_L} \left( \frac{V_{cc}}{\pi} - \frac{V_p}{4} \right)$$

$$P_{a\text{os}Q1, \text{max}}$$

$$\frac{dP_{a\text{os}Q1}}{dV_p} = -\frac{1}{2} \frac{V_p}{R_L} + \frac{V_{cc}}{\pi R_L} = 0 \Rightarrow \frac{1}{R_L} \left( \frac{V_{cc}}{\pi} - \frac{V_p}{2} \right) = 0 \Rightarrow V_p = \frac{2V_{cc}}{\pi}$$

$$P_{a\text{os}Q1, \text{MAX}} = \frac{2V_{cc} \pi}{R_L} \left( \frac{V_{cc}}{\pi} - \frac{2V_{cc} \pi}{4} \right) \Rightarrow P_{a\text{os}Q1, \text{MAX}} = \frac{V_{cc}^2}{\pi^2 \cdot R_L}$$

• Considerando desprezando  $I_{B1}$  e  $I_{B2}$ , podemos desprezar a potência dissipada por  $I_1$  e  $I_2$ .

∴  $P_{avcinc} = P_{avQ1} + P_{avQ2} = 2 \cdot P_{avQ1}$

$$P_{avcinc} = \frac{2V_p^2}{RL} \left( \frac{V_{cc}}{\pi} - \frac{V_p}{4} \right)$$

→ A potência dissipada na carga é a mesma do seguidor de emissor

$$P_{avout} = \frac{V_p^2}{2RL}$$

$$\Rightarrow \eta = \frac{\frac{V_p^2}{2RL}}{\frac{V_p^2}{2RL} + \frac{2V_p}{RL} \left( \frac{V_{cc}}{\pi} - \frac{V_p}{4} \right)} = \frac{\frac{V_p^2}{2RL}}{\frac{V_p^2 + 4V_p \left( \frac{V_{cc}}{\pi} - \frac{V_p}{4} \right)}{2RL}}$$

$$\eta = \frac{V_p^2}{V_p^2 + \frac{4V_p V_{cc}}{\pi} - \frac{4V_p^2}{4}} \Rightarrow \boxed{\eta = \frac{V_p \cdot \pi}{4V_{cc}}}$$