

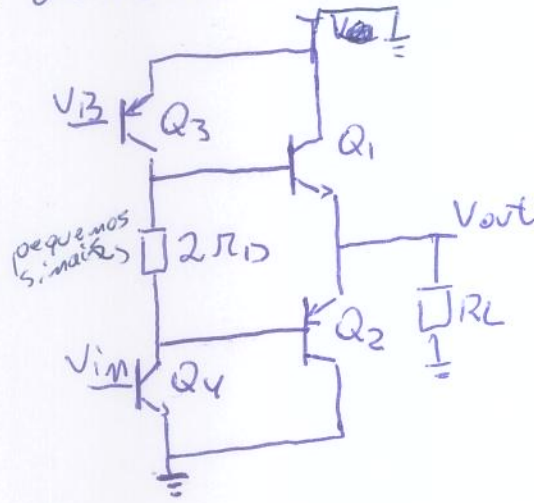
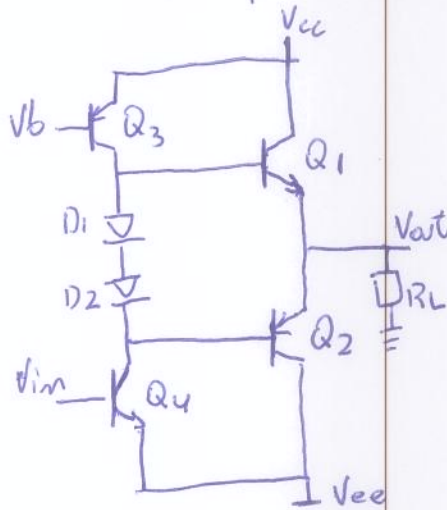
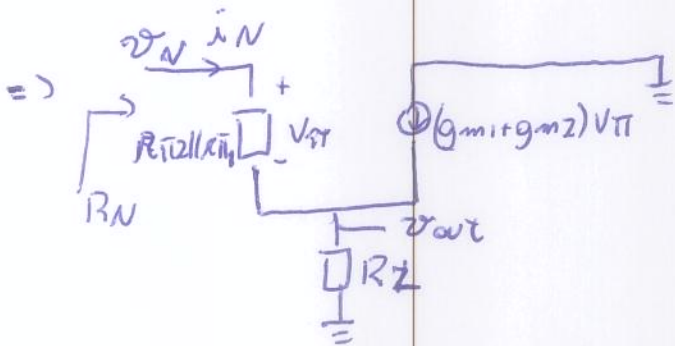


Amplificador de Potência (GANHO)

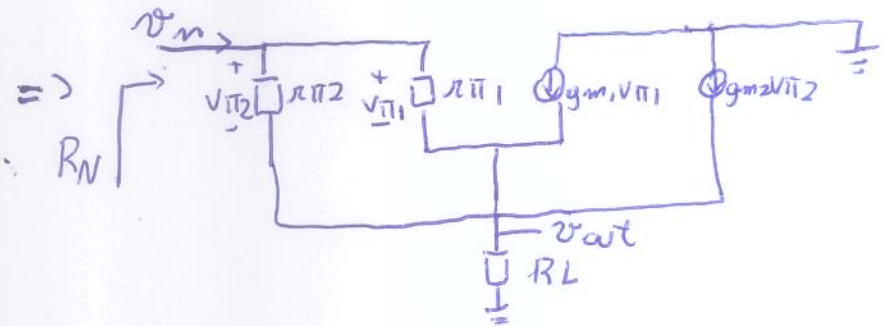

• $Q_3 \Rightarrow$ Fonte de corrente $\Rightarrow Z_3 \sim \infty$

• $r_D \sim 0$

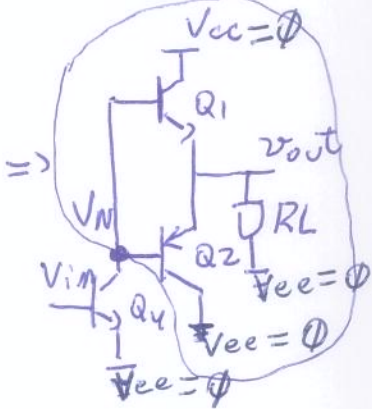

$$\frac{v_{out}}{R_L} = \frac{v_{\pi} - v_{out}}{r_{\pi 2} || r_{\pi 1}} + (g_{m1} + g_{m2}) \cdot (v_{\pi} - v_{out})$$

$$v_{out} = \left(\frac{v_{\pi}}{r_{\pi 1} || r_{\pi 2}} + (g_{m2} + g_{m1}) v_{\pi} \right) \cdot R_L$$


$$v_{out} = v_{\pi} \left(\frac{1}{r_{\pi 1} || r_{\pi 2}} + g_{m2} + g_{m1} \right) \cdot R_L$$

$$v_N = v_{\pi} + v_{\pi} \left(\frac{1}{r_{\pi 1} || r_{\pi 2}} + g_{m2} + g_{m1} \right) \cdot R_L$$

$$v_N = v_{\pi} \left(1 + \left(\frac{1}{r_{\pi 1} || r_{\pi 2}} + g_{m2} + g_{m1} \right) R_L \right)$$

$$\frac{v_{out}}{v_N} = \frac{\left(\frac{1}{r_{\pi 1} || r_{\pi 2}} + g_{m2} + g_{m1} \right) \cdot R_L}{1 + \left(\frac{1}{r_{\pi 1} || r_{\pi 2}} + g_{m2} + g_{m1} \right) \cdot R_L} \cdot \left(\frac{1}{r_{\pi 1} || r_{\pi 2}} + g_{m2} + g_{m1} \right)^{-1}$$

$$\frac{v_{out}}{v_{in}} = \frac{R_L}{\left(\frac{1}{r_{\pi 1} || r_{\pi 2}} + g_{m2} + g_{m1} \right)^{-1} + R_L} \quad \Rightarrow \quad \therefore \frac{v_{out}}{v_N} \approx \frac{R_L}{R_L + \frac{1}{g_{m1} + g_{m2}}} \quad \textcircled{1}$$

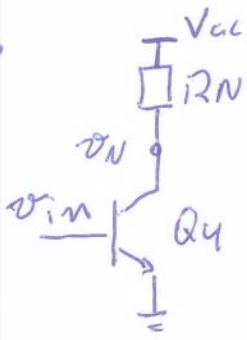


$$i_N = \frac{v_N}{r_{\pi 1} \parallel r_{\pi 2}} \Rightarrow R_N = \frac{v_N}{i_N}$$

$$R_N = \frac{1 + \left(\frac{1}{r_{\pi 1} \parallel r_{\pi 2}} + g_{m1} + g_{m2} \right) R_L}{\frac{1}{r_{\pi 1} \parallel r_{\pi 2}}}$$

$$R_N = (r_{\pi 1} \parallel r_{\pi 2}) + R_L \cdot (1 + (g_{m1} + g_{m2}) \cdot (r_{\pi 1} \parallel r_{\pi 2})) \gg 1$$
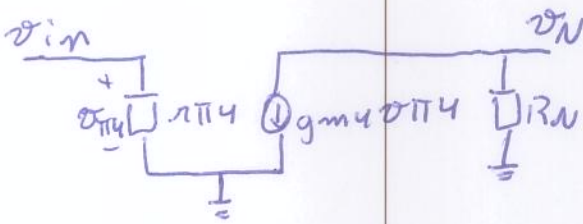
$$\therefore R_N \approx (r_{\pi 1} \parallel r_{\pi 2}) + R_L \cdot (g_{m1} + g_{m2}) \cdot (r_{\pi 1} \parallel r_{\pi 2})$$



$$v_N = -g_{m4} v_{\pi 4} R_N$$

$$v_{in} = v_{\pi 4}$$

$$\frac{v_N}{v_{in}} = -g_{m4} R_N$$

• Ganho total

$$A_v = \frac{v_{out}}{v_{in}} = \frac{v_N}{v_{in}} \cdot \frac{v_{out}}{v_N}$$

$$A_v = -g_{m4} \cdot [r_{\pi 1} \parallel r_{\pi 2} + R_L (g_{m1} + g_{m2}) \cdot (r_{\pi 1} \parallel r_{\pi 2})] \cdot \frac{v_{out}/v_N}{R_L + \frac{1}{g_{m1} + g_{m2}}}$$

$$\left. \begin{array}{l} \beta_1 = \beta_2 \\ I_{c1} = I_{c2} \end{array} \right\} \beta$$

$$\bullet \beta_1 = \beta_2 \text{ e } I_{c1} \approx I_{c2}$$


$$A_v = -g_{m4} [r_{\pi 1} \parallel r_{\pi 2} + R_L (g_{m1} + g_{m2}) \cdot (r_{\pi 1} \parallel r_{\pi 2})]$$

ou seja

$$R_L (g_{m1} + g_{m2}) (r_{\pi 1} \parallel r_{\pi 2}) \gg r_{\pi 1} \parallel r_{\pi 2}$$

$$\therefore A_v = -g_{m4} (r_{\pi 1} \parallel r_{\pi 2}) \cdot (g_{m1} + g_{m2}) \cdot R_L$$

* Exemplo 13.10

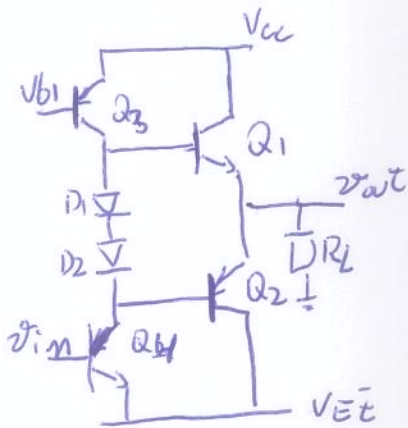

$|A_{V_{pot}}| = 5$

$I_{C1}, I_{C2}, I_3, I_{C4}?$

$|A_{V_{pot}}| = 0,8$

$R_L = 8 \Omega$

$\beta_{mpn} = 2\beta_{pnp} = 100$

$I_{C1} \sim I_{C2}$

$A_{V_{pot}} = \frac{R_L}{R_L + \frac{1}{g_{m1} + g_{m2}}} \Rightarrow 0,8 = \frac{8}{8 + \frac{1}{g_{m1} + g_{m2}}} \Rightarrow 8 = 6,4 + \frac{0,8}{g_{m1} + g_{m2}}$

$\frac{0,8}{g_{m1} + g_{m2}} = 1,6 \Rightarrow g_{m1} + g_{m2} = 0,5 \Rightarrow \frac{I_{C1} \sim I_{C2}}{V_T} \approx 0,25$

$g_{m1} = \frac{I_{C1}}{V_T} \Rightarrow 0,25 = \frac{I_{C1}}{26 \cdot 10^{-3}} \Rightarrow I_{C1} \approx I_{C2} \approx 6,5 \text{ mA}$

$|A_{V_{Q2}}| = 5 \cdot 0,8 = 4 \Rightarrow |A_{V_{Q2E}}|$

$r_{\pi 1} = \frac{\beta_1}{g_{m1}} = \frac{100}{0,25} \Rightarrow r_{\pi 1} = 400 \Omega \Rightarrow r_{\pi 1} || r_{\pi 2} \approx 133 \Omega$

$r_{\pi 2} = \frac{\beta_2}{g_{m2}} = \frac{50}{0,25} \Rightarrow r_{\pi 2} = 200 \Omega$

$|A_{V_{Q2}}| = 5 \cdot 0,8 = 4 = |-g_{m4} [r_{\pi 1} || r_{\pi 2} + R_L (g_{m1} + g_{m2}) r_{\pi 1} || r_{\pi 2}] \cdot 0,8|$

$g_{m4} = 7,518 \text{ mS}$

$g_{m4} = \frac{I_{C4}}{V_T} \Rightarrow I_{C4} = 195,48 \mu\text{A}$



$I_{C3} = 195,48 \mu\text{A}$

$v_{out \text{ max}} \Rightarrow I_{C1 \text{ max}} \Rightarrow Q_4 \text{ corte} \Rightarrow Q_2 \text{ corte}$
 $v_{out \text{ max}} = I_{C1 \text{ max}} \cdot R_L = \beta_1 \cdot I_{C3} \cdot R_L = 100 \cdot 195,48 \cdot 10^{-6} \cdot 8$

$v_{out \text{ max}} = 0,156 \text{ V} \sim$ baixa amplitude de saída
 $I_{C1 \text{ max}} = 19,5 \text{ mA}$ Tem que aumentar I_{C1} e, $\therefore I_{C3}$

fonte de corrente (3)

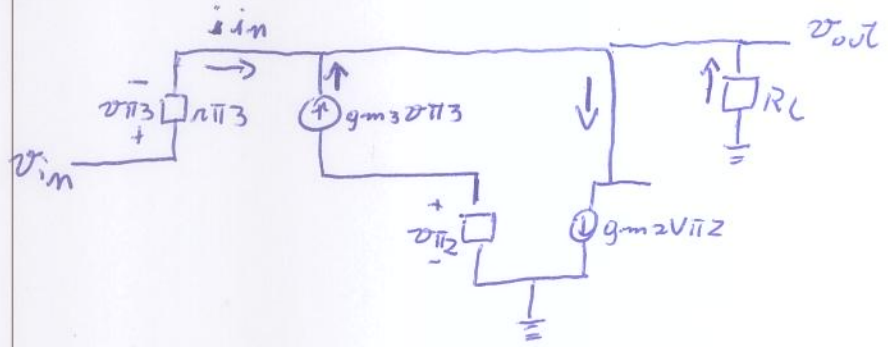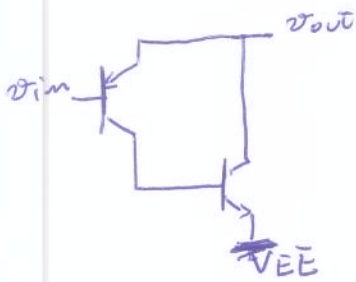• Transistor PNP de potência (Darlington)



• $v_{\pi 3} = v_{in} - v_{out}$ (1)

• $v_{\pi 2} = -r_{\pi 2} g_{m3} v_{\pi 3}$ $\Rightarrow v_{\pi 2} = -r_{\pi 2} g_{m3} (v_{in} - v_{out})$ (2)

• $v_{out} = -R_L \left(g_{m2} v_{\pi 2} - g_{m3} v_{\pi 3} - \frac{v_{\pi 3}}{r_{\pi 3}} \right)$

(1) & (2) $\Rightarrow v_{out} = -R_L \left[g_{m2} (-r_{\pi 2} g_{m3} (v_{in} - v_{out})) - g_{m3} (v_{in} - v_{out}) - \frac{v_{in} - v_{out}}{r_{\pi 3}} \right]$

$v_{out} = -R_L \left[-g_{m2} r_{\pi 2} g_{m3} (v_{in} - v_{out}) - g_{m3} (v_{in} - v_{out}) - \frac{v_{in} - v_{out}}{r_{\pi 3}} \right]$

$v_{out} = -R_L \left[-\beta_2 g_{m3} v_{in} + \beta_2 g_{m3} v_{out} - \left(g_{m3} + \frac{1}{r_{\pi 3}} \right) (v_{in} - v_{out}) \right]$

$v_{out} = -R_L \left[-\beta_2 g_{m3} v_{in} + \beta_2 g_{m3} v_{out} - \left(g_{m3} + \frac{1}{r_{\pi 3}} \right) v_{in} + \left(g_{m3} + \frac{1}{r_{\pi 3}} \right) v_{out} \right]$

$v_{out} \cdot \left[1 + R_L \left(\beta_2 g_{m3} + g_{m3} + \frac{1}{r_{\pi 3}} \right) \right] = v_{in} R_L \left(\beta_2 g_{m3} + g_{m3} + \frac{1}{r_{\pi 3}} \right)$

$v_{out} \cdot \left[1 + R_L g_{m3} (\beta_2 + 1) + \frac{1}{r_{\pi 3}} \right] = v_{in} R_L \left[g_{m3} (\beta_2 + 1) + \frac{1}{r_{\pi 3}} \right]$

$A_v = \frac{v_{out}}{v_{in}} = \frac{R_L \left[g_{m3} (\beta_2 + 1) + \frac{1}{r_{\pi 3}} \right]}{1 + R_L \left[g_{m3} (\beta_2 + 1) + \frac{1}{r_{\pi 3}} \right]}$

$A_v = \frac{R_L}{\frac{1}{g_{m3} (\beta_2 + 1) + \frac{1}{r_{\pi 3}}} + R_L}$

$$i_{in} = \frac{v_{in}}{r_{\pi 3}} \stackrel{+}{=} \frac{v_{in} - v_{out}}{r_{\pi 3}}$$

Z_{in}

$$i_{in} = \frac{1}{r_{\pi 3}} \left(v_{in} - v_{in} \cdot \frac{R_L}{g_{m3}(\beta_2+1) + \frac{1}{r_{\pi 3}}} \right)$$

$v_{out} = v_{in} A_v$
 \downarrow
 $\frac{g_{m3}}{\beta_3}$
 $\sim g_{m3}(\beta_2+1)$

$$i_{in} = \frac{v_{in}}{r_{\pi 3}} \left(1 - \frac{R_L}{\frac{1}{g_{m3}(\beta_2+1)} + R_L} \right) = \frac{v_{in}}{r_{\pi 3}} \left(1 - \frac{R_L \cdot g_{m3}(\beta_2+1)}{1 + R_L g_{m3}(\beta_2+1)} \right)$$


~~$$i_{in} = v_{in} \left(\frac{1}{r_{\pi 3}} - \frac{R_L g_{m3}(\beta_2+1)}{r_{\pi 3} + R_L g_{m3}(\beta_2+1)} \right)$$~~

$$i_{in} = \frac{v_{in}}{r_{\pi 3}} \left(\frac{1 + R_L g_{m3}(\beta_2+1) - R_L g_{m3}(\beta_2+1)}{1 + R_L g_{m3}(\beta_2+1)} \right)$$

$$Z_{in} = \frac{v_{in}}{i_{in}} = r_{\pi 3} \cdot (1 + R_L g_{m3}(\beta_2+1))$$

$$\beta_3 = r_{\pi 3} g_{m3} \Rightarrow \boxed{Z_{in} = r_{\pi 3} + \beta_3 (\beta_2+1) R_L}$$

* Z_{out}

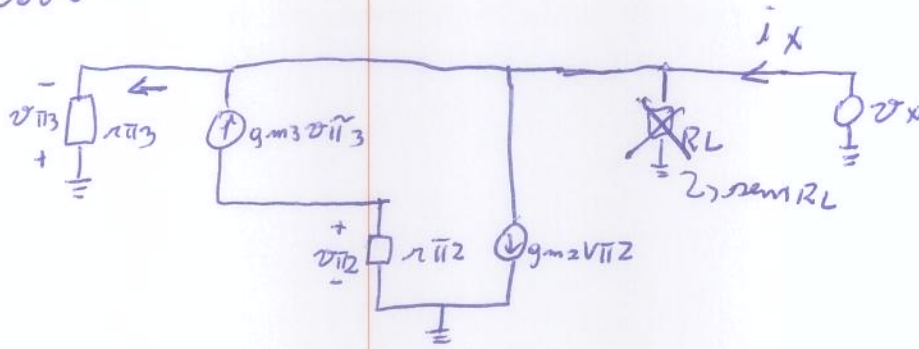

• $v_{\pi 3} = -v_x$ ①

• $v_{\pi 2} = g_{m3} v_{\pi 3} r_{\pi 2} \Rightarrow v_{\pi 2} = g_{m3} v_x r_{\pi 2}$ ②

• $i_x = g_{m2} v_{\pi 2} + \frac{v_x}{r_{\pi 3}} - g_{m3} v_{\pi 3}$

①② $\Rightarrow i_x = g_{m2} g_{m3} v_x r_{\pi 2} + \frac{v_x}{r_{\pi 3}} + g_{m3} v_x$

$i_x = g_{m3} \beta_2 v_x + \frac{v_x}{r_{\pi 3}} + g_{m3} v_x$

$Z_{out} = \frac{v_x}{i_x} = \frac{1}{g_{m3} \beta_2 + \frac{1}{r_{\pi 3}} + g_{m3}}$

$Z_{out} = \frac{1}{(\beta_2 + 1)g_{m3} + \frac{1}{r_{\pi 3}}} \Rightarrow Z_{out} \approx \frac{1}{(\beta_2 + 1)g_{m3}}$

$\underbrace{\frac{1}{r_{\pi 3}}}_{\frac{g_{m3}}{\beta}}$