

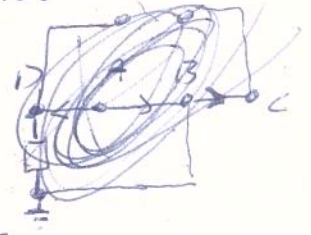
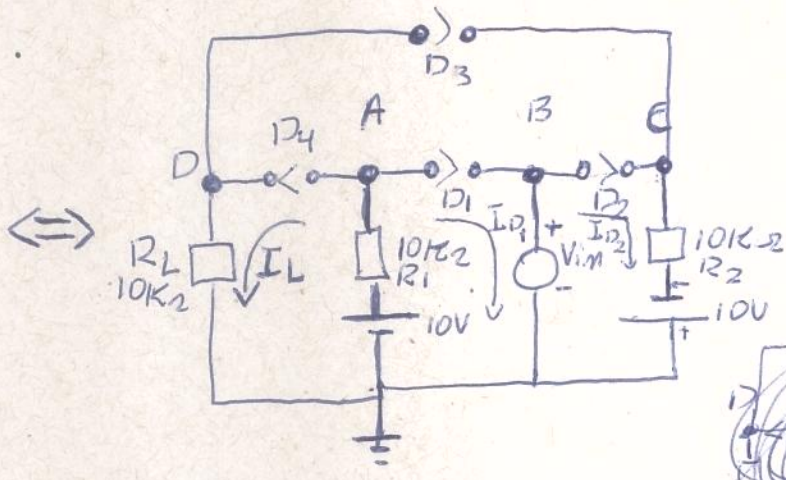


ULAF5

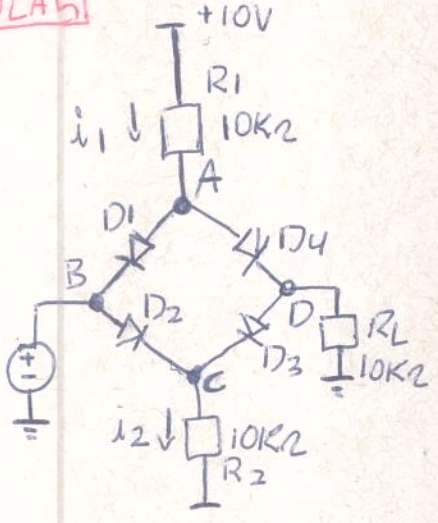

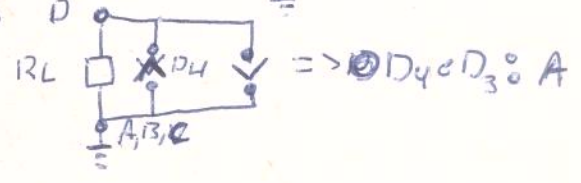* $V_{in} = 0 \Rightarrow D_1: F; D_2: F \Rightarrow V_A = V_B = V_C = 0V \Rightarrow D_4: A$



* $V_{in} > 0 \Rightarrow D_1: F; D_2: F \Rightarrow V_A = V_B = V_C = V_{in}$

Como $V_A = V_{in} > 0 \Rightarrow D_4: F \Rightarrow V_D = V_C \Rightarrow D_3: A$

• $I_L = \frac{V_{in}}{R_L} > 0$


• $10 \cdot (I_L + I_{D1}) = 10 - V_{in} \Rightarrow 10 \left(\frac{V_{in}}{10} + I_{D1} \right) = 10 - V_{in} \Rightarrow I_{D1} = \frac{10 - 2V_{in}}{10}$
 $\Rightarrow D_1: F \Rightarrow I_{D1} > 0 \Rightarrow V_{in} < 5V \Rightarrow V_L = V_{in}$

• $10 \cdot I_{D2} = 10 + V_{in} \Rightarrow I_{D2} = \frac{10 + V_{in}}{10} > 0$

$\Rightarrow V_{in} \geq 5V \Rightarrow D_1: A; D_2: F; D_4: F \Rightarrow \begin{cases} V_C = V_{in} \\ V_D = \frac{10 \cdot 10 - 5V}{10 + 10} \end{cases} \Rightarrow V_C > V_D \Rightarrow D_3: A$
 $\Rightarrow V_L = 5V$

* $V_{in} < 0 \Rightarrow D_1: F; D_2: F \Rightarrow V_A = V_B = V_C = V_{in}$

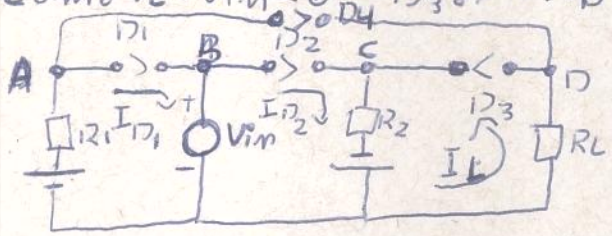Como $V_C = V_{in} < 0 \Rightarrow D_3: F \Rightarrow V_D = V_A \Rightarrow D_4: A$



• $I_L = \frac{-V_{in}}{R_L} > 0$
 • $I_{D1} = \frac{10 - 2V_{in}}{10} > 0$

• $10 \cdot (I_{D2} + I_L) = 10 + V_{in} \Rightarrow I_{D2} = \frac{10 + 2V_{in}}{10}$

$\Rightarrow D_2: F \Rightarrow I_{D2} > 0 \Rightarrow V_{in} > -5V \Rightarrow V_L = V_{in}$

• $V_{in} \leq -5V \Rightarrow D_2: A; D_1: F; D_3: F \Rightarrow \begin{cases} V_A = V_{in} \\ V_D = \frac{-10 \cdot 10 - 5V}{10 + 10} \end{cases} \Rightarrow V_A < V_D \Rightarrow D_4: A$
 $\Rightarrow V_L = -5V$

