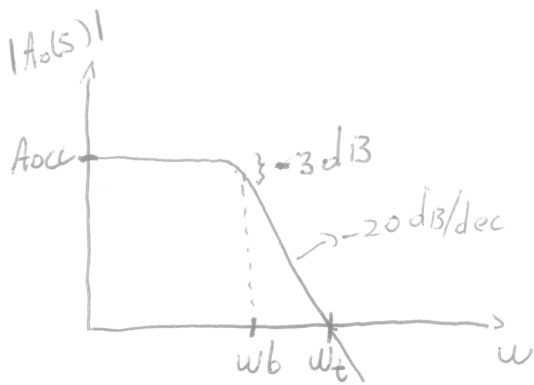


• Largura de Banda Finita (Pedra)



$$A_0(s) = \frac{A_{occ}}{1 + \frac{s}{\omega_b}}$$


poço $\Rightarrow s_p = -\omega_b$
 \downarrow
 corresponde a uma queda de 3 dB em Aocc

• $\omega \gg \omega_b$

$$A_0(s) \approx \frac{A_{occ}}{\frac{s}{\omega_b}} \Rightarrow A_0(j\omega) \approx \frac{A_{occ}}{\frac{j\omega}{\omega_b}} \Rightarrow |A_0(j\omega)| \approx \frac{A_{occ} \omega_b}{\omega} \quad (A)$$

$$|A_0(j\omega)| = \frac{A_{occ} \omega_b}{\omega} \Rightarrow |A_0(j\omega)| = 1 \Rightarrow \omega_t \approx A_{occ} \omega_b \quad (B)$$

• Amplificador inversor

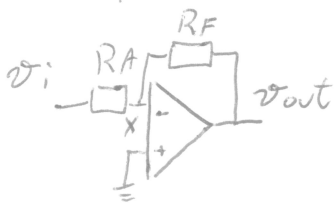

• $v_+ = 0 \Rightarrow (0 - v_x) \cdot A_o = v_{out} \quad (1) \quad v_x = -\frac{v_{out}}{A_o}$
 • $v_- = v_x$

• $\frac{v_i - v_x}{R_A} = \frac{v_x - v_{out}}{R_F} \Rightarrow R_F v_i - R_F v_x = R_A v_x - R_A v_{out}$

(1) $\Rightarrow R_F v_i + R_F \frac{v_{out}}{A_o} = -R_A \frac{v_{out}}{A_o} - R_A v_{out} \Rightarrow R_F v_i = -v_{out} \left(\frac{R_F + R_A}{A_o} + R_A \right) \rightarrow A_{oid}$


$$A_o = \frac{v_{out}}{v_i} = \frac{-R_F}{\frac{R_F + R_A}{A_o} + R_A} \cdot A_o^{-1} = \frac{-R_F/R_A}{1 + \frac{(R_F/R_A + 1)}{A_o}} \Rightarrow A_o = \frac{-R_F/R_A}{1 + \frac{(R_F/R_A + 1)}{A_o}}$$

\Rightarrow Fazendo $A_o = A_o(s)$


$$A_o(s) \frac{-R_F/R_A}{1 + \frac{(R_F/R_A + 1)}{A_{occ}} \frac{1 + \frac{s}{\omega_b}}{1 + \frac{s}{\omega_b}}} = \frac{-R_F/R_A}{1 + \frac{(R_F/R_A + 1)}{A_{occ}} \cdot \left(1 + \frac{s}{\omega_b}\right)} = \frac{-R_F/R_A}{1 + \frac{(R_F/R_A + 1)}{A_{occ}} + \frac{(R_F/R_A + 1) \cdot s}{A_{occ} \omega_b}}$$

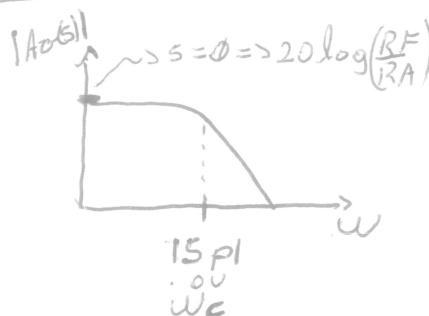(B) $\Rightarrow A_o(s) = \frac{-R_F/R_A}{1 + \frac{(R_F/R_A + 1)}{A_{occ}} + \frac{(R_F/R_A + 1) s}{\omega_t}}$ $A_o \gg \frac{(R_F + 1)}{R_A} \Rightarrow A_o(s) \approx \frac{-R_F/R_A}{1 + \frac{(R_F/R_A + 1) \cdot s}{\omega_t}}$

• Polo $\Rightarrow s_p = -\frac{\omega_t}{(R_F/R_A + 1)}$
 $\omega_c = \omega_{corte}$



Amp. não inversor

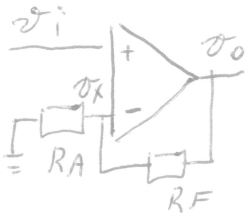

$$\left. \begin{aligned} v_+ &= v_i \\ v_- &= v_x \end{aligned} \right\} A_o(v_i - v_x) = v_o \Rightarrow v_o = \frac{A_o v_i - v_o R_F}{R_A} \quad (A)$$

$$v_x = \frac{v_o}{R_A} \Rightarrow v_x = v_o \frac{R_A}{R_F + R_A} \quad (B)$$

$$(B) \rightarrow (A) \Rightarrow A_o \left(v_i - \frac{v_o R_A}{R_F + R_A} \right) = v_o \Rightarrow A_o v_i = v_o \left(1 + \frac{A_o R_A}{R_F + R_A} \right)$$

$$A_v = \frac{A_o \cdot A_o^{-1}}{1 + \frac{A_o R_A}{R_F + R_A} \cdot A_o^{-1}} = \frac{1}{1 + \frac{R_A}{R_F + R_A}} \cdot \frac{R_F + R_A}{R_A} \Rightarrow A_v = \frac{1 + R_F/R_A}{1 + \frac{R_A}{R_F + R_A} + 1}$$

\Rightarrow Fazendo $A_o = A_o(s)$

$$A_v(s) = \frac{1 + R_F/R_A}{1 + \frac{R_A}{A_{occ} \left(\frac{1 + R_F/R_A}{R_A} \right) + 1}} \Rightarrow A_o(s) = \frac{1 + R_F/R_A}{\left(\frac{1 + s\omega_b}{A_{occ}} \right) \left(\frac{1 + R_F/R_A}{R_A} \right) + 1} = \frac{1 + R_F/R_A}{\frac{1 + R_F/R_A}{A_{occ}} + \frac{(1 + R_F/R_A)s + 1}{A_{occ} \omega_b}}$$

$$A_v(s) = \frac{A_{oid}}{1 + \frac{1 + R_F/R_A}{A_{occ}} + \frac{(1 + R_F/R_A)s + 1}{A_{occ} \omega_b}}$$

$$A_{occ} \rightarrow \frac{1 + R_F/R_A}{R_A} \Rightarrow A_o(s) \approx \frac{1 + R_F/R_A}{\left(\frac{1 + R_F/R_A}{\omega_b} \right) s + 1}$$

• Polo $\Rightarrow s_p = \frac{-\omega_b}{1 + R_F/R_A}$
 $\omega_c = \omega_{corte}$

obs: $A_{oid} \cdot \omega_{corte} = \omega_b$

