
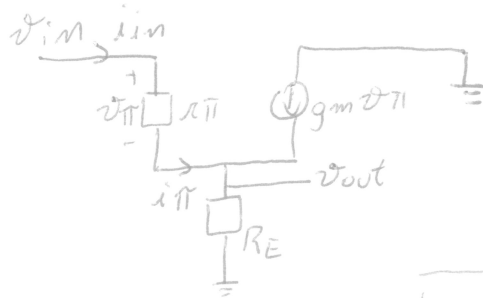


* Degradador del modo común

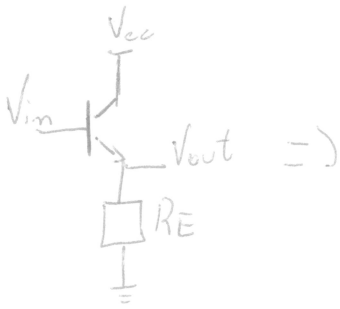

$$v_{out} = R_E \cdot (i_{\pi} + g_m v_{\pi}) = R_E \cdot \left(\frac{v_{\pi}}{r_{\pi}} + g_m v_{\pi} \right) \Rightarrow v_{out} = v_{\pi} R_E \cdot \left(\frac{1}{r_{\pi}} + g_m \right)$$

$$v_{in} = v_{\pi} + v_{out} \Rightarrow v_{in} = v_{\pi} \cdot \left(1 + R_E \left(\frac{1}{r_{\pi}} + g_m \right) \right)$$

$$A_v = \frac{v_{out}}{v_{in}} = \frac{R_E \left(\frac{1}{r_{\pi}} + g_m \right)}{1 + R_E \left(\frac{1}{r_{\pi}} + g_m \right)} = \frac{R_E \cdot \left(\frac{1 + g_m r_{\pi}}{r_{\pi}} \right)}{1 + R_E \left(\frac{1 + g_m r_{\pi}}{r_{\pi}} \right)} = \frac{R_E \cdot \left(\frac{g_m}{\beta} + g_m \right)}{1 + R_E \left(\frac{g_m}{\beta} + g_m \right)}$$

$$A_v = \frac{R_E \cdot \left(\frac{g_m(\beta+1)}{\beta} \right)}{1 + R_E \left(\frac{g_m(\beta+1)}{\beta} \right)} = \frac{R_E \left(\frac{g_m(\beta+1)}{\beta} \right)}{\beta + R_E g_m(\beta+1)} = \frac{R_E g_m(\beta+1)}{\beta + R_E g_m(\beta+1)} \cdot g_m^{-1}$$

$$A_v = \frac{R_E \cdot (\beta+1)}{\beta + R_E \cdot (\beta+1)} \quad \beta \gg 1 \Rightarrow A_v \approx \frac{R_E}{1 + R_E g_m}$$


$$i_{in} = \frac{v_{\pi}}{r_{\pi}}$$

$$Z_{in} = \frac{v_{in}}{i_{in}} = \frac{\left[1 + R_E \left(\frac{1}{r_{\pi}} + g_m \right) \right] v_{\pi}}{\frac{v_{\pi}}{r_{\pi}}} = r_{\pi} \cdot \left[1 + R_E \left(\frac{1}{r_{\pi}} + g_m \right) \right]$$


$$Z_{in} = r_{\pi} + R_E r_{\pi} \cdot \left(\frac{1}{r_{\pi}} + g_m \right)$$

$$Z_{in} = r_{\pi} + R_E \cdot \left(1 + \frac{g_m r_{\pi}}{\beta} \right)$$



* PUSH-PULL

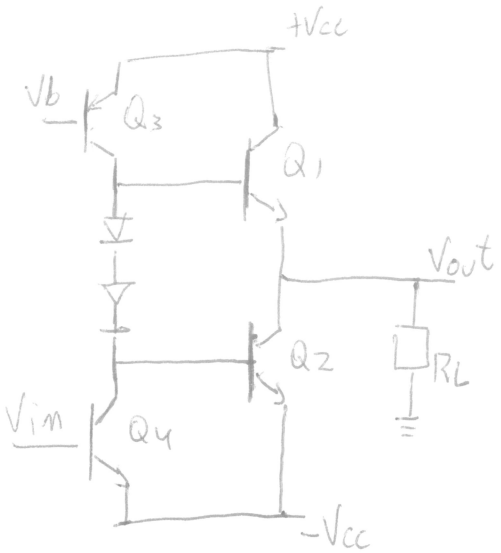

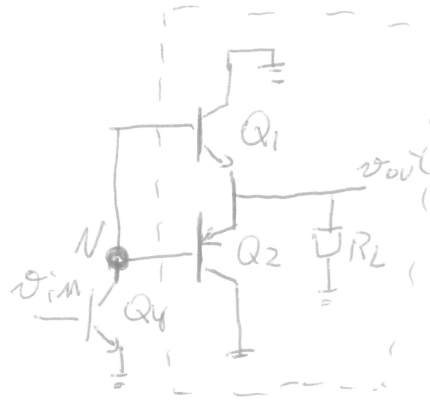$\beta_D \approx \beta$
 $V_A = \infty$
 \Rightarrow



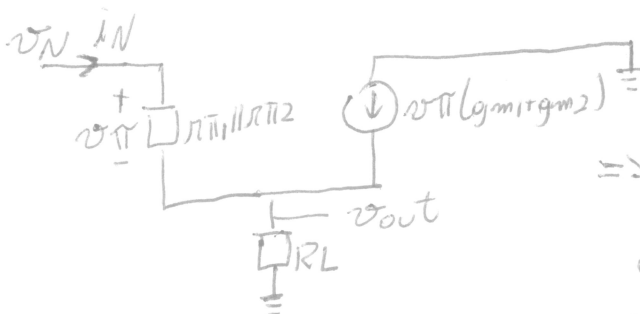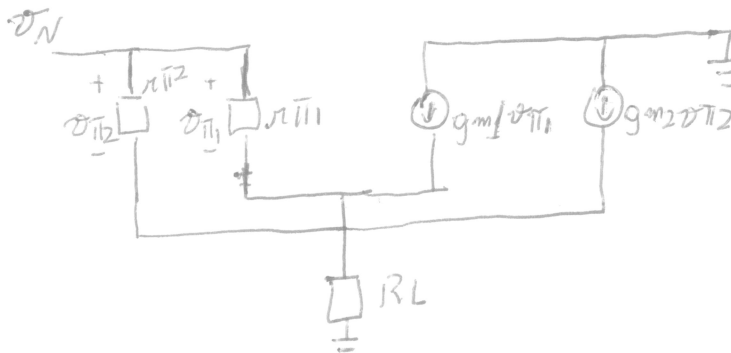\Rightarrow Mod. Pequenos sinais estágio de saída



\Rightarrow i_{in} : lar ao seguidor de emissor
 $v_{out} = R_L \cdot \left(\frac{v_{pi}}{r_{pi1} || r_{pi2}} + (g_{m1} + g_{m2}) v_{pi} \right)$

$v_{in} = v_{pi} + v_{out}$
 $i_{in} = \frac{v_{pi}}{r_{pi1} || r_{pi2}}$

$$\frac{v_{out}}{v_N} = \frac{R_L \left(\frac{1}{r_{pi1} || r_{pi2}} + (g_{m1} + g_{m2}) \right)}{1 + R_L \left(\frac{1}{r_{pi1} || r_{pi2}} + (g_{m1} + g_{m2}) \right)}$$


$$\frac{v_{out}}{v_N} \approx \frac{R_L}{\frac{1}{g_{m1} + g_{m2}} + R_L}$$

$Z_N = \frac{v_N}{i_N} = \frac{v_{pi} \left(1 + R_L \left(\frac{1}{r_{pi1} || r_{pi2}} + g_{m1} + g_{m2} \right) \right)}{v_{pi} / (r_{pi1} || r_{pi2})}$

$Z_N = r_{pi1} || r_{pi2} + R_L + \underbrace{(1 + (g_{m1} + g_{m2}) \cdot r_{pi1} || r_{pi2})}_{\gg 1}$

$Z_N \approx r_{pi1} || r_{pi2} + R_L (g_{m1} + g_{m2}) \cdot r_{pi1} || r_{pi2}$

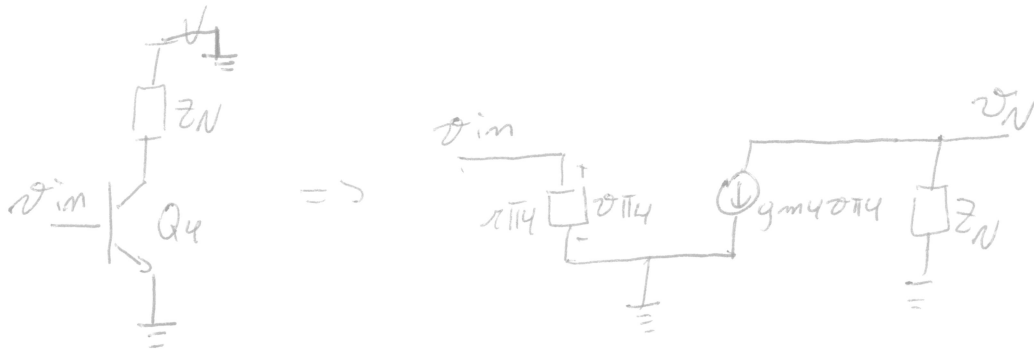* Modelo pequenos sinais estágio de entrada



$$v_N = -g_{m4} v_{\pi 4} Z_N$$

$$v_{in} = v_{\pi 4} \Rightarrow \frac{v_N}{v_{in}} = -g_{m4} Z_N$$

* GANHO TOTAL - A_v

$$A_v = \frac{v_N}{v_{in}} \cdot \frac{v_{out}}{v_N} = -g_{m4} Z_N \cdot \frac{R_L}{R_L + \frac{1}{g_{m1} + g_{m2}}} \cdot \frac{\pi_{\pi 1} // \pi_{\pi 2} + R_L \cdot (g_{m1} + g_{m2}) \cdot \pi_{\pi 1} // \pi_{\pi 2}}$$

• Assumindo $\beta_1 = \beta_2 = \beta$ e $I_{c1} = I_{c2}$

$$g_{m1} + g_{m2} = \frac{\beta}{\pi_{\pi 1}} + \frac{\beta}{\pi_{\pi 2}} = \frac{\beta \cdot (\pi_{\pi 1} + \pi_{\pi 2})}{\pi_{\pi 1} \cdot \pi_{\pi 2}} \Rightarrow \boxed{g_{m1} + g_{m2} = \frac{\beta}{\pi_{\pi 1} // \pi_{\pi 2}}}$$

$$A_v \approx -g_{m4} \cdot \left[\pi_{\pi 1} // \pi_{\pi 2} + R_L (g_{m1} + g_{m2}) \cdot \pi_{\pi 1} // \pi_{\pi 2} \right] \cdot \frac{R_L}{R_L + \frac{1}{g_{m1} + g_{m2}}}$$

$$A_v \approx -g_{m4} \left[\pi_{\pi 1} // \pi_{\pi 2} + \beta R_L \right] \cdot \frac{R_L}{R_L + \frac{\pi_{\pi 1} // \pi_{\pi 2}}{\beta}}$$

$$R_L \gg \frac{\pi_{\pi 1} // \pi_{\pi 2}}{\beta} \Rightarrow A_v \approx -g_{m4} [\pi_{\pi 1} // \pi_{\pi 2} + \beta R_L]$$

$$\beta R_L \gg \pi_{\pi 1} // \pi_{\pi 2} \Rightarrow \boxed{A_v \approx -g_{m4} \cdot \beta R_L}$$

$$A_v \approx -g_{m4} (g_{m1} + g_{m2}) \cdot \pi_{\pi 1} // \pi_{\pi 2} \cdot R_L$$