

Lista de Exercícios (10, 12, 14, 15, 17, 23, 29)
 RAZAVI - CAP 2 pg 48

2.10
 $N_D = 5 \cdot 10^{17}$ $T = 300K$ $k = 1,38 \cdot 10^{-23} J/K$
 $N_A = 4 \cdot 10^{16}$ $E_g = 1,2 eV = 1,792 \cdot 10^{-19} J$ $q = 1,6 \cdot 10^{-19} C$

a) n e p ?

$$n_i = 5,2 \cdot 10^{15} T^{3/2} \cdot \exp\left(\frac{-E_g}{2kT}\right) \Rightarrow n_i = 1,0776 \cdot 10^{10} cm^{-3}$$

* Lado P

$$p = N_A \Rightarrow p = 4 \cdot 10^{16} cm^{-3}$$

$$n = \frac{n_i^2}{p} \Rightarrow n = 2,903 \cdot 10^3 cm^{-3}$$

* Lado N

$$n = N_D \Rightarrow n = 5 \cdot 10^{17} cm^{-3}$$

$$p = \frac{n_i^2}{n} \Rightarrow p = 232,24 cm^{-3}$$

b) V_0 ?

+ $T = 250K$

$$\rightarrow n_i = 5,2 \cdot 10^{15} T^{3/2} \exp\left(\frac{-E_g}{2kT}\right) \Rightarrow n_i = 1,081 \cdot 10^8 cm^{-3}$$

$$V_0 = \frac{kT}{q} \ln\left(\frac{N_A \cdot N_D}{n_i^2}\right) \Rightarrow V_0(250) = 0,9053V$$

$$+ T = 300K \Rightarrow n_i = 1,0776 \cdot 10^{10} cm^{-3} \Rightarrow V_0(300) = 0,8482V$$

$$+ T = 350K \Rightarrow n_i = 2,9897 \cdot 10^{11} cm^{-3} \Rightarrow V_0(350) = 0,7884V$$

$$V_0 = \frac{kT}{q} \cdot \left[\ln N_A + \ln N_D - \ln \left(5,02 \cdot 10^{15} T^{3/2} \exp\left(\frac{-E_g}{2kT}\right) \right)^2 \right]$$

$$V_0 = \frac{kT}{q} \left[\ln N_A + \ln N_D - 2 \ln(5,02 \cdot 10^{15}) - 3 \ln T - \ln \left[\exp\left(\frac{-E_g}{2kT}\right) \right]^2 \right]$$

$$V_0 = \frac{kT}{q} \cdot \left[\ln N_A + \ln N_D - 2 \ln(5,02 \cdot 10^{15}) - 3 \ln T + \frac{E_g}{2kT} \right]$$

$\frac{dV}{dT}$

$$\frac{dV_0}{dT} = \frac{k}{q} \cdot \left[\ln N_A + \ln N_D - 2 \ln(5,02 \cdot 10^{15}) - 3 \ln T + \frac{E_g}{2kT} \right] +$$

$$+ \frac{kT}{q} \cdot \left[0 + 0 - 2 \cdot 0 - 3 \cdot \frac{1}{T} - \frac{E_g}{2kT^2} \right]$$

$$\frac{dV_0}{dT} = \frac{k}{q} \left[\ln N_A + \ln N_D - 2 \ln(5,02 \cdot 10^{15}) - 3 \ln T - 3 \right]$$

$$\frac{dV_0}{dT} = \frac{k}{q} \cdot \left[\ln(N_A \cdot N_D) - \ln \left[(5,02 \cdot 10^{15})^2 \cdot T^3 \right] - 3 \right]$$

\Rightarrow Se $\ln(N_A \cdot N_D) < \ln \left[(5,02 \cdot 10^{15})^2 \cdot T^3 \right] - 3$, V_0 decai com a temperatura
 Caso Atual

2.13) $T=300K$ $\phi_0 = 1.04V$
 $N_A = 2 \cdot 10^{16} \text{ cm}^{-3}$ $\epsilon_{Si} = 1,04 \cdot 10^{-12} \text{ F/cm}$ $E_g = 1,2eV = 1,792 \cdot 10^{-19} \text{ J}$
 $N_D = 9 \cdot 10^{15} \text{ cm}^{-3}$ $V_{i2} = 1,6V$ $q = 1,6 \cdot 10^{-19} \text{ C}$
 $k = 1,38 \cdot 10^{-23} \text{ J/K}$

a) $n_i = 5 \cdot 2 \cdot 10^{15} \cdot T^{3/2} \cdot \exp\left(-\frac{E_g}{2kT}\right) \Rightarrow n_i = 1,0776 \cdot 10^{10}$

$V_0 = \frac{kT}{q} \ln \frac{N_A N_D}{n_i^2} \Rightarrow V_0 = 0,6979V$

$C_{J0} = \sqrt{\frac{\epsilon_{Si}}{2} \frac{N_A N_D \cdot L}{N_A + N_D V_0}} \Rightarrow C_{J0} = 1,4951 \cdot 10^{-8} \text{ F/cm}^2$

$C_J = \frac{C_{J0}}{\sqrt{1 + \frac{V_{i2}}{V_0}}} \Rightarrow C_J = 8,2395 \cdot 10^{-9} \text{ F/cm}^2$

b) $C_J' = 2 \cdot C_J$

$\sqrt{\frac{\epsilon_{Si} \cdot N_A N_D \cdot L}{2(N_A + N_D V_0)}} = 2 C_J \Rightarrow$ *Só utilizando método numérico*
 $\frac{N_A'}{N_A} \sim 5,125$

2.14) $V_D = 750mV$ $V_T \sim 26mV$
 $I_D = 1mA$


a) $I_D = I_S \cdot \exp\left(\frac{V_D}{V_T}\right) \Rightarrow I_S = I_D \exp\left(-\frac{V_D}{V_T}\right)$
 $I_S = 1mA \exp\left(-\frac{750}{26}\right) \Rightarrow I_S = 2,9667 \cdot 10^{-13} \text{ mA}$

b) $I_S = A q n_i^2 \left(\frac{D_n}{N_A L_n} + \frac{D_p}{N_D L_p} \right)$

$I_S \propto A \Rightarrow$ dobra a área $\Rightarrow I_S' = 2 \cdot I_S$

$V_d = V_T \cdot \ln \frac{I_D}{I_S'} \Rightarrow V_D = V_T \cdot \ln \frac{I_D}{2 \cdot I_S} \Rightarrow V_D = 734,9782mV$

2.15

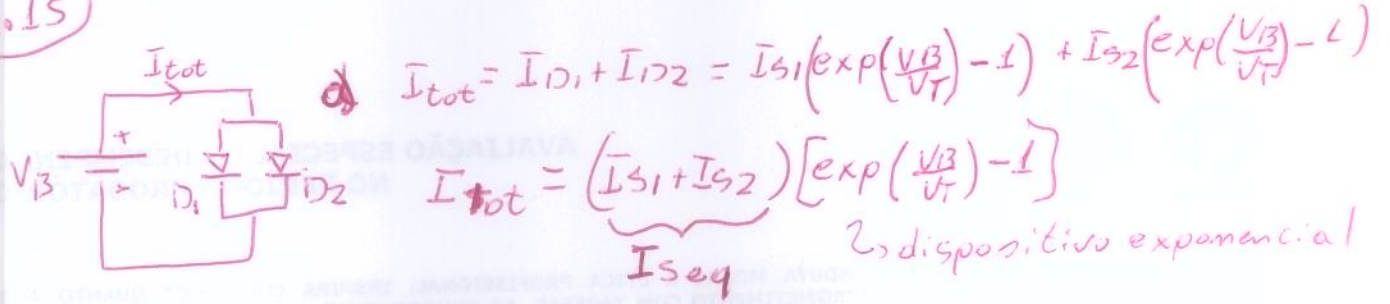

b) $V_{D1} = V_{D2}$

$$V_T \ln \frac{\bar{I}_{D1}}{\bar{I}_{S1}} = V_T \ln \frac{\bar{I}_{D2}}{\bar{I}_{S2}} \Rightarrow \boxed{\frac{\bar{I}_{D1}}{\bar{I}_{S1}} = \frac{\bar{I}_{D2}}{\bar{I}_{S2}}} \quad (1)$$

~~$$\bar{I}_{tot} = \bar{I}_{D1} + \bar{I}_{D2} \Rightarrow \bar{I}_{D1} + \frac{\bar{I}_{D1} \bar{I}_{S2}}{\bar{I}_{S1}} \Rightarrow \bar{I}_{D1} = \frac{\bar{I}_{tot} \cdot \bar{I}_{S1}}{\bar{I}_{S1} + \bar{I}_{S2}}$$~~

$$+\bar{I}_{tot} = \bar{I}_{D1} + \bar{I}_{D2} \Rightarrow \boxed{\bar{I}_{D2} = \bar{I}_{tot} - \bar{I}_{D1}} \quad (2)$$

(2) \rightarrow (1)

$$\frac{\bar{I}_{D1}}{\bar{I}_{S1}} = \frac{\bar{I}_{tot} - \bar{I}_{D1}}{\bar{I}_{S2}} \Rightarrow \bar{I}_{D1} \bar{I}_{S2} = \bar{I}_{S1} \bar{I}_{tot} - \bar{I}_{D1} \bar{I}_{S1}$$


$$\bar{I}_{D1} (\bar{I}_{S1} + \bar{I}_{S2}) = \bar{I}_{S1} \bar{I}_{tot}$$

$$\Rightarrow \boxed{\bar{I}_{D1} = \frac{\bar{I}_{S1} \bar{I}_{tot}}{\bar{I}_{S1} + \bar{I}_{S2}}} \quad (3)$$

~~(3)~~
$$\boxed{\bar{I}_{D1} = \bar{I}_{tot} - \bar{I}_{D2}} \quad (4)$$

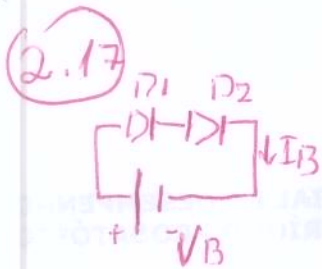(4) \rightarrow (1)

$$\frac{\bar{I}_{tot} - \bar{I}_{D2}}{\bar{I}_{S1}} = \frac{\bar{I}_{D2}}{\bar{I}_{S2}} \Rightarrow \boxed{\bar{I}_{D2} = \frac{\bar{I}_{S2} \cdot \bar{I}_{tot}}{\bar{I}_{S1} + \bar{I}_{S2}}} \quad (5)$$



$I_B, V_{D1}, V_{D2} ?$

$$V_B = V_{D1} + V_{D2}$$

$$V_B = V_T \ln \frac{I_B}{I_{S1}} + V_T \ln \frac{I_B}{I_{S2}}$$

$$V_B = V_T \ln \frac{I_B^2}{I_{S1} \cdot I_{S2}}$$

$$\Rightarrow \frac{V_B}{V_T} = \ln \frac{I_B^2}{I_{S1} \cdot I_{S2}} \Rightarrow \frac{I_B^2}{I_{S1} \cdot I_{S2}} = \exp \frac{V_B}{V_T} \Rightarrow I_B = \sqrt{I_{S1} \cdot I_{S2} \exp \frac{V_B}{V_T}}$$


$$\Rightarrow V_{D1} = V_T \ln \frac{I_B}{I_{S1}} \Rightarrow V_{D1} = V_T \ln \frac{\sqrt{I_{S1} \cdot I_{S2} \exp \frac{V_B}{V_T}}}{I_{S1}}$$

$$V_{D1} = V_T \ln \frac{I_{S2}^{1/2} \cdot I_{S2}^{1/2} \cdot \exp \frac{V_B}{2V_T}}{I_{S1}} \Rightarrow V_{D1} = V_T \left[\ln \frac{I_{S2}^{1/2}}{I_{S1}^{1/2} \cdot I_{S1}'} + \ln \exp \frac{V_B}{2V_T} \right]$$

$$V_{D1} = V_T \ln \sqrt{\frac{I_{S2}}{I_{S1}} + \frac{V_B}{2}}$$

$$\Rightarrow V_{D2} = V_T \ln \frac{I_B}{I_{S2}} \Rightarrow V_{D2} = V_T \ln \sqrt{\frac{I_{S1}}{I_{S2}} + \frac{V_B}{2}}$$

2.23

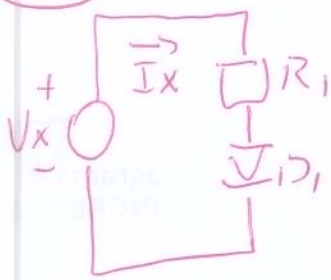

I_x (mA)	V_x (V)
0,2	1
0,5	2

$V_T = 26 \text{ mV}$

$$V_{D1} = V_T \ln \frac{I_x}{I_S} \quad \left. \begin{array}{l} V_x - R_1 I_x = V_T \ln \frac{I_x}{I_S} \\ V_{D1} = V_x - R_1 I_x \end{array} \right\}$$

$$\Rightarrow \begin{cases} 1 - R_1 0,2 \cdot 10^{-3} = 26 \cdot 10^{-3} \ln \frac{0,2 \cdot 10^{-3}}{I_S} & (1) \\ 2 - R_1 0,5 \cdot 10^{-3} = 26 \cdot 10^{-3} \ln \frac{0,5 \cdot 10^{-3}}{I_S} & (2) \end{cases}$$

$$(2) - (1) \Rightarrow 1 - R_1 (0,5 - 0,2) \cdot 10^{-3} = 26 \cdot 10^{-3} \ln \frac{0,5 \cdot 10^{-3} \cdot I_S}{0,2 \cdot 10^{-3}}$$

$$1 - 0,3 \cdot 10^{-3} R_1 = 26 \cdot 10^{-3} \ln \frac{0,5}{0,2}$$

0,9163

0,0238

$$R_1 = \frac{0,0238 - 1}{-0,3 \cdot 10^{-3}} \Rightarrow \boxed{R_1 = 3,2539 \cdot 10^3 \Omega}$$


$$\boxed{R_1 = 3,2539 \text{ k}\Omega}$$

$$I_S = I_D \exp \frac{-V_D}{V_T} = I_0 \exp \frac{-(V_x - R_1 I_x)}{26 \cdot 10^{-3}}$$

$$= 0,2 \cdot \exp \left(\frac{-(1 - 0,2 \cdot 10^{-3} \cdot 3,2539 \cdot 10^3)}{26 \cdot 10^{-3}} \right)$$

$$\boxed{I_S = 2,9362 \cdot 10^{-10} \text{ A}}$$

2.29

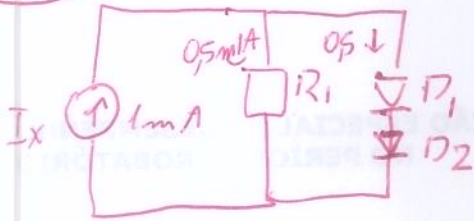

$$I_S = 5 \cdot 10^{-16} \text{ A}$$

$R_1 ?$

$$V_D = V_T \ln \frac{I_D}{I_S} \quad \text{with } I_D = 0,5 \cdot 10^{-3} \text{ A}$$

$$2 \cdot V_D = R_1 \cdot 0,5 \cdot 10^{-3}$$

$$V_D = 0,25 \cdot 10^{-3} R_1$$

$$0,25 \cdot 10^{-3} R_1 = 26 \cdot 10^{-3} \ln \frac{0,5 \cdot 10^{-3}}{5 \cdot 10^{-16}} \Rightarrow R_1 = \frac{26 \cdot 10^{-3}}{0,25 \cdot 10^{-3}} \ln \frac{0,5 \cdot 10^{-3}}{5 \cdot 10^{-16}}$$

$$R_1 = 2,87 \text{ k}\Omega$$

