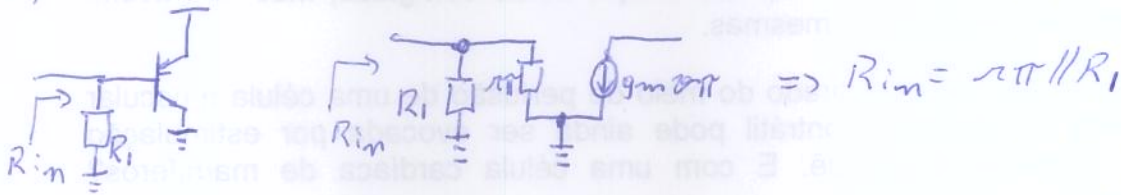


RAZAVI (5.5, 5.6, 5.9b, 5.13, 5.17, 5.38d, 5.47b, 5.52, 5.55, 5.58, 5.63, 5.68, 5.71, 5.72, 5.73)
 CAP5



5.5 $V_A = \infty$, Z_{in} ?

a)




$\Rightarrow R_{in} = r_{\pi} \parallel R_1$

b)

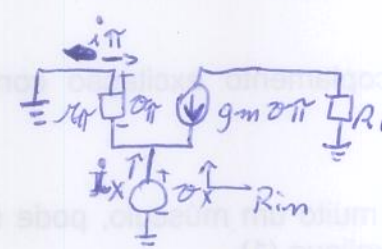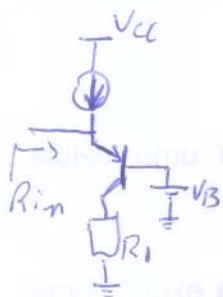


$$\begin{aligned}
 & i_{\pi} + g_m v_{\pi} + i_x = 0 \\
 & \frac{v_{\pi}}{r_{\pi}} + g_m v_{\pi} + i_x = 0 \\
 & v_{\pi} \cdot \left(\frac{1}{r_{\pi}} + g_m \right) = -i_x \\
 & -v_x \left(\frac{1}{r_{\pi}} + g_m \right) = -i_x \Rightarrow R_{in} = \frac{v_x}{i_x} = \frac{1}{\left(g_m + \frac{1}{r_{\pi}} \right)} \\
 & R_{in} = \frac{1}{g_m} \parallel r_{\pi}
 \end{aligned}$$

c)

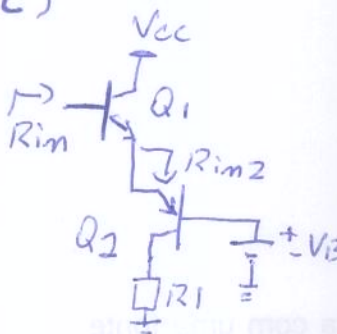

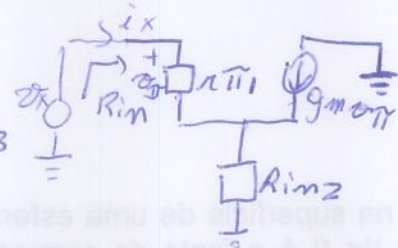$R_{in2} = \frac{1}{g_{m2}} \parallel R_{\pi2}$





$$\begin{aligned}
 v_x &= v_{\pi_1} + \left(\frac{v_{\pi_1}}{r_{\pi_1}} + g_{m1} v_{\pi_1} \right) R_{in2} \\
 i_x &= v_{\pi_1} \left[\left(\frac{1}{r_{\pi_1}} + g_{m1} \right) R_{in2} \right] \\
 v_{\pi_1} &= r_{\pi_1} i_x \\
 v_x &= r_{\pi_1} i_x \left[\left(\frac{1}{r_{\pi_1}} + g_{m1} \right) R_{in2} \right]
 \end{aligned}$$

$R_{in} = \frac{v_x}{i_x} = r_{\pi_1} \left[\left(\frac{1}{r_{\pi_1}} + g_{m1} \right) R_{in2} \right] = \left(1 + \beta_1 \right) R_{in2}$

$R_{in} = \frac{v_x}{i_x} = r_{\pi_1} \left[1 + \left(\frac{1}{r_{\pi_1}} + g_{m1} \right) R_{in2} \right] = r_{\pi_1} + \left(\frac{1}{r_{\pi_1}} + g_{m1} \right) R_{in2} r_{\pi_1}$

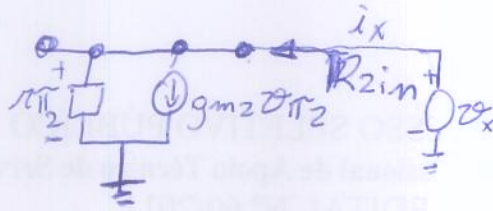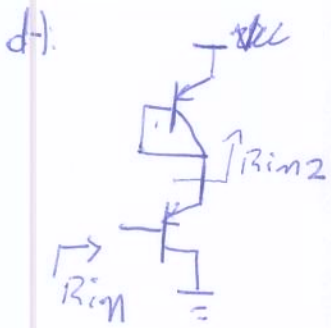
$R_{in} = r_{\pi_1} + \left(1 + \beta_1 \right) R_{in2} \Rightarrow R_{in} = r_{\pi_1} + (1 + \beta) \cdot \left(\frac{1}{g_{m2}} \parallel R_{\pi2} \right)$



$$i_x = g_{m2} v_{\pi 2} + \frac{v_x}{r_{\pi 2}}$$



$$i_x = g_{m2} v_x + \frac{v_x}{r_{\pi 2}}$$
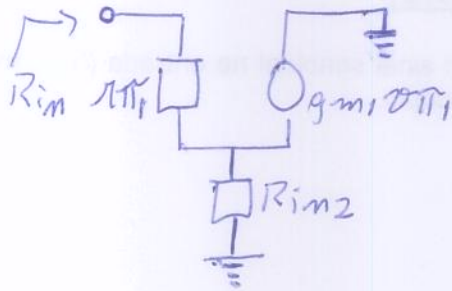
$$R_{in 2} = \frac{i_x}{v_x} = \frac{1}{g_{m2} + \frac{1}{r_{\pi 2}}} = \frac{1}{\frac{1}{r_{\pi 2}} \parallel g_{m2}}$$



mesmo caso anterior

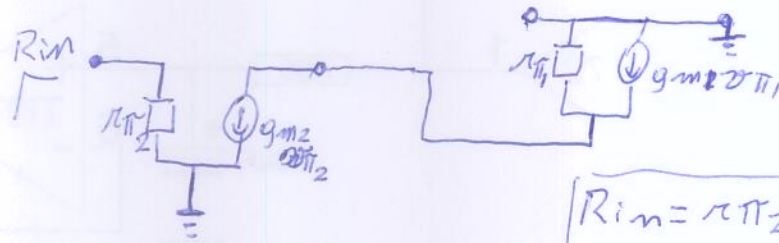
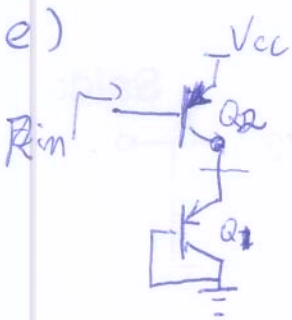
$$R_{in} = r_{\pi 1} + (1 + \beta) \cdot \left(\frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$



$$R_{in} = r_{\pi 2}$$




5.6

a) $V_A \neq \infty$

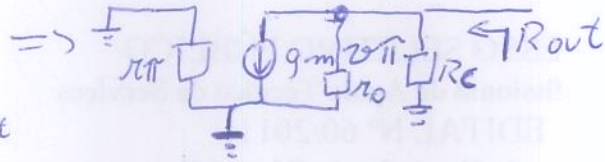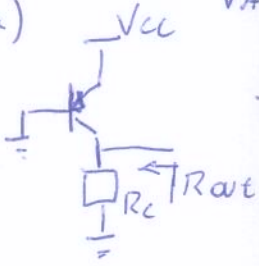

$$R_{out} = R_c \parallel r_o$$

b)

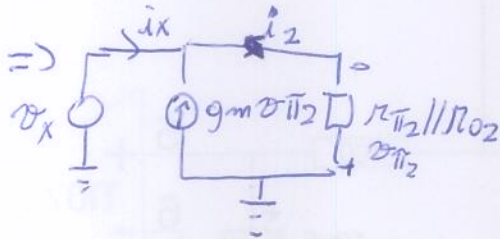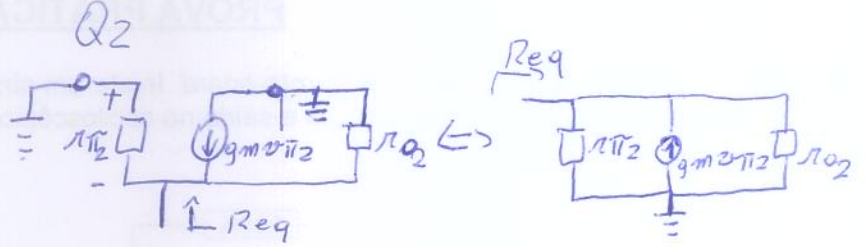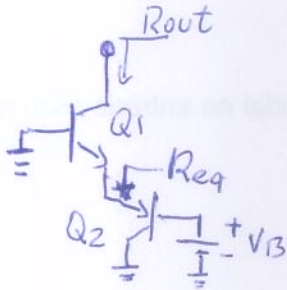



$$i_x + g_m v_{\pi 2} + i_2 = 0$$


$$i_x + g_m v_{\pi 2} + \frac{v_{\pi 2}}{r_{\pi 2} \parallel r_{o 2}} = 0$$

$$i_x = -\frac{v_{\pi 2}}{v_x} \left(g_m + \frac{1}{r_{\pi 2} \parallel r_{o 2}} \right)$$

$$i_x = v_x \left(g_m + \frac{1}{r_{o 2} \parallel r_{\pi 2}} \right)$$
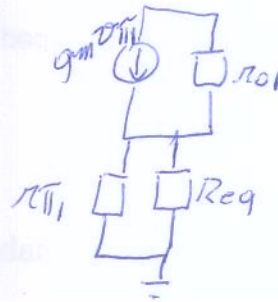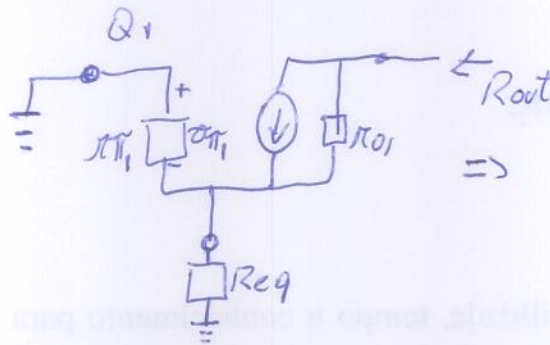
$$\Rightarrow \frac{v_x}{i_x} = R_{eq} = \frac{1}{g_{m 2} \parallel r_{\pi 2} \parallel r_{o 2}}$$



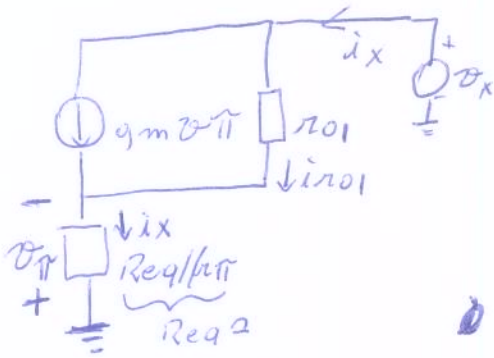

$$i_x = g_{m1} v_{\pi 1} + i_{\pi 01}$$

$$\begin{cases} i_x = g_{m1} v_{\pi 1} + \frac{v_x + v_{\pi 1}}{\pi_{01}} \\ i_x = -\frac{v_{\pi 1}}{R_{eq2}} \Rightarrow v_{\pi 1} = -i_x R_{eq2} \end{cases}$$

~~$$i_x = \frac{i_x R_{eq2} g_{m1}}{R_{eq2}} + \frac{v_x - i_x R_{eq2}}{\pi_{01}} - i_x R_{eq2}$$~~

~~$$i_x = -\frac{i_x R_{eq2} g_{m1}}{R_{eq2}} + \frac{v_x - i_x R_{eq2}}{\pi_{01}} - i_x R_{eq2} = i_x (1 + g_{m1} R_{eq2})$$~~

~~$$i_x = -g_{m1} i_x R_{eq2} + \frac{v_x - i_x R_{eq2}}{\pi_{01}}$$~~

~~$$i_x = -g_{m1} i_x R_{eq2} + \frac{v_x}{\pi_{01}} - \frac{i_x R_{eq2}}{\pi_{01}}$$~~

~~$$i_x \cdot (g_{m1} R_{eq2} + \frac{R_{eq2}}{\pi_{01}} + 1) = \frac{v_x}{\pi_{01}}$$~~


$$R_{out} = \frac{v_x}{i_x} = \pi_{01} \cdot \left(1 + R_{eq2} \cdot (g_{m1} + \frac{1}{\pi_{01}}) \right)$$

$$R_{out} = \pi_{01} + \pi_{01} R_{eq2} (g_{m1} + \frac{1}{\pi_{01}})$$

$$R_{out} = \pi_{01} + R_{eq2} \cdot (g_{m1} \pi_{01} + 1)$$

$$R_{out} = \pi_{01} + (1 + g_{m1} \pi_{01}) \pi_{\pi 1} \parallel \frac{1}{g_{m2}} \parallel \pi_{\pi 2} \parallel \pi_{02}$$

5.9

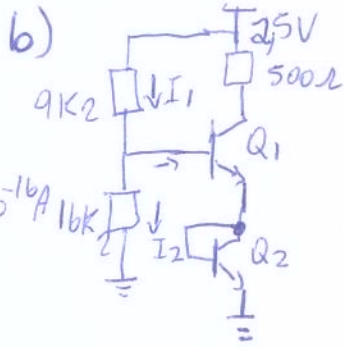

$$\beta = 100$$

$$I_s = 5 \cdot 10^{-16} \text{ A}$$

$$I_{E1} = I_{E2}$$

$$\Rightarrow I_{C1} = I_{C2} \Rightarrow \begin{cases} V_{BE1} = V_{BE2} \\ I_{B1} = I_{B2} \end{cases}$$

$$I_{B1} = I_1 - I_2 = \frac{V_{CC} - 2V_{BE}}{9 \cdot 10^3} - \frac{2V_{BE}}{16 \cdot 10^3}$$

$$I_{C1} = \beta I_{B1} = \beta \cdot \left(\frac{V_{CC} - 2V_{BE}}{9 \cdot 10^3} - \frac{2V_{BE}}{16 \cdot 10^3} \right)$$

$$I_{C1} = \beta \cdot \left(\frac{V_{CC} - 2V_T \ln \frac{I_{C1}}{I_s}}{9 \cdot 10^3} - \frac{2V_T \ln \frac{I_{C1}}{I_s}}{16 \cdot 10^3} \right)$$

$$I_{C1} - \beta \left(\frac{V_{CC} - 2V_T \ln \frac{I_{C1}}{I_s}}{9 \cdot 10^3} - \frac{2V_T \ln \frac{I_{C1}}{I_s}}{16 \cdot 10^3} \right) = 0$$

$$I_{C1} - \frac{\beta V_{CC}}{9 \cdot 10^3} + \frac{2\beta V_T \ln(I_{C1}/I_s)}{9 \cdot 10^3} + \frac{2\beta V_T \ln I_{C1}/I_s}{16 \cdot 10^3} = 0$$

$$I_C - \frac{\beta V_{CC}}{9 \cdot 10^3} + \frac{32\beta V_T \ln I_{C1}/I_s + 18\beta V_T \ln I_{C1}/I_s}{9 \cdot 16 \cdot 10^6} = 0$$

$$I_C - \frac{\beta V_{CC}}{9 \cdot 10^3} + \frac{50\beta V_T \ln I_{C1}/I_s}{9 \cdot 16 \cdot 10^6} = 0$$

⇓ Cálculo numérico

$$\boxed{I_C \approx 1,72 \text{ mA}}$$

$$V_{BE} = V_{BE1} = V_{BE2} = V_T \ln I_C / I_s = 5V_{BE} = \underline{751 \text{ mV}}$$

$$\underline{V_{CE2} = V_{BE} = 751 \text{ mV}}$$

$$V_{CE1} = 2,5 - 500 I_C - V_{CE2} \Rightarrow \underline{V_{CE1} = 890 \text{ mV}}$$

$$V_{B1} = 2 \cdot V_{BE} = \underline{1,502 \text{ V}}$$

$$V_{C1} = 2,5 - 500 I_C = 1,64 \text{ V} \Rightarrow V_{C1} > V_{B1} \Rightarrow Q_1 \text{ modo ACtivo}$$

Q2 próximo a saturação

5

5.9 b) Resolução iterativa

(1) $V_{BE} = 0,7$

$$I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \Rightarrow I_C = 1,0482 \cdot 10^{-4} A$$

$$I_B = \frac{V_{CC} - 2V_{BE}}{9 \cdot 10^3} - \frac{2V_{BE}}{16 \cdot 10^3} \Rightarrow I_B = 3,4722 \cdot 10^{-5} A$$

(2) $I_C = \beta I_B = 3,4722 \cdot 10^{-3} A$

$$V_{BE} = V_T \ln \frac{I_C}{I_S} = 0,7688 V$$

$$I_B = 1,0836 \cdot 10^{-5} A$$

(3) $I_C = 1,0836 \cdot 10^{-3} A$

$$V_{BE} = 0,7385 V$$

$$I_B = 2,1349 \cdot 10^{-5} A$$

(4) $I_C = 2,1349 \cdot 10^{-3} A$

$$V_{BE} = 0,7561 V$$

$$I_B = 1,5227 \cdot 10^{-5} A$$

(5) $I_C = 1,5227 \cdot 10^{-3} A$

$$V_{BE} = 0,7474 V$$

$$I_B = 1,8278 \cdot 10^{-5} A$$

(6) $I_C = 1,8278 \cdot 10^{-3} A$

$$V_{BE} = 0,7521 V$$

$$I_B = 1,6629 \cdot 10^{-5} A$$

(7) $I_C = 1,66 \cdot 10^{-3} A$

$$V_{BE} = 0,7497 V$$

$$I_B = 1,7482 \cdot 10^{-5} A$$

(8) $I_C = 1,7482 \cdot 10^{-3} A$

$$V_{BE} = 0,7497 V$$

$$I_B = 1,7482 \cdot 10^{-5} A$$

mw