
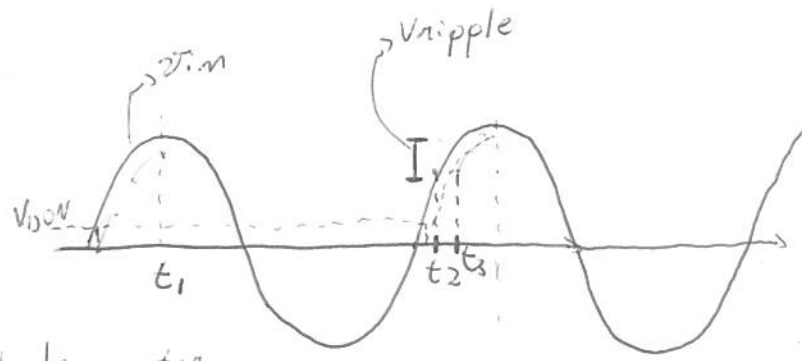


* Retificador 1/2 onda

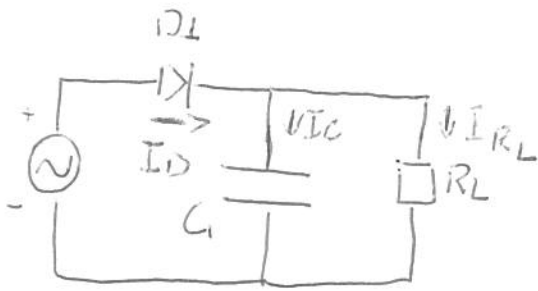

→ fórmula da descarga do capacitor

→ tempo de descarga

$$\bullet V_{out}(t) = (V_p - V_{DC}) \exp\left(-\frac{\Delta t}{R_L C_1}\right), \quad \Delta t = t_2 - t_1$$

$$\bullet \exp\left(-\frac{\Delta t}{R_L C_1}\right) \underset{\text{Taylor}(\Delta t=0)}{\approx} \exp\left(\frac{-0}{R_L C_1}\right) \cdot (\Delta t - 0)^0 + \frac{1}{R_L C_1} \exp\left(\frac{-0}{R_L C_1}\right) \cdot (\Delta t - 0)^1 = \left[\exp\left(\frac{-\Delta t}{R_L C_1}\right) = 1 - \frac{\Delta t}{R_L C_1} \right]$$

$$\bullet V_{out}(t) \approx (V_p - V_{DC}) \left(1 - \frac{\Delta t}{R_L C_1} \right) = (V_p - V_{DC}) - (V_p - V_{DC}) \cdot \frac{\Delta t}{R_L C_1}$$

$$\bullet V_{out} \approx V_p - V_{DC} - V_{ripple}$$



$$\left\{ V_{ripple} = (V_p - V_{DC}) \frac{\Delta t}{R_L C_1} \Rightarrow V_{ripple} \approx (V_p - V_{DC}) \cdot \frac{I}{R_L C_1} \right.$$

$$V_{ripple} \approx \frac{V_p - V_{DC}}{R_L C_1 f}$$

$$\bullet \frac{V_p - V_{DC}}{R_L} \approx \bar{I}_L \Rightarrow V_{ripple} \approx \frac{\bar{I}_L}{C_1 f}$$

* Corrente do diodo

• Assumindo que $V_p \gg V_{R0} =$

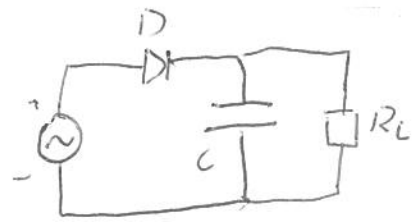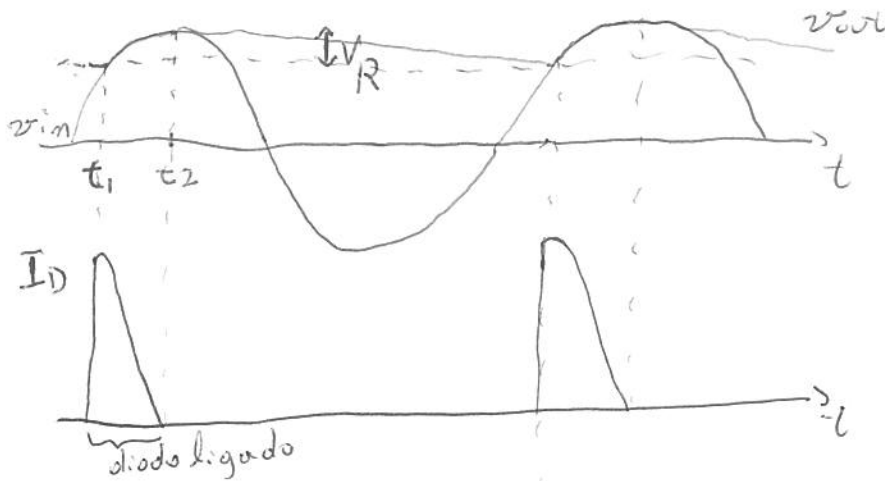

• $i_L = \frac{v_{out}}{R}$; $i_C = C \frac{dv_o}{dt}$

• $i_D = i_C + i_L$

• $i_D = C \frac{dv_{out}}{dt} + \frac{v_{out}}{R}$ como $V_R \ll V_p \Rightarrow \frac{v_{out}}{R} \approx \frac{V_p}{R} \Rightarrow i_D \approx C \frac{dv_{out}}{dt} + \frac{V_p}{R}$

• $v_{out} = V_p \sin \omega t$, $t_1 \leq t \leq t_2$ ②

• em t_1

• $v_{out} = V_p - V_R$

• $v_{out} = V_p \sin \omega t_1$

$\Rightarrow \begin{cases} \sin \omega t_1 = 1 - \frac{V_R}{V_p} & \text{③} \\ \cos \omega t_1 = \sqrt{1 - \left(1 - \frac{V_R}{V_p}\right)^2} & \text{④} \end{cases}$ 2) $\sin^2 \theta + \cos^2 \theta = 1$

• De ① e ② $C \frac{dv_{out}}{dt}$

$i_D \approx C V_p \omega \cos \omega t + \frac{V_p}{R}$

• $i_{D \text{ pico}} \Rightarrow t = t_1$

$i_{Dp} = V_p \omega C \cos \omega t_1 + \frac{V_p}{R} \stackrel{\text{④}}{\Rightarrow} i_{Dp} = V_p \omega C \sqrt{1 - \left(1 - \frac{V_R}{V_p}\right)^2} + \frac{V_p}{R}$
 $\underbrace{1 - \left(1 - \frac{V_R}{V_p}\right)^2}_{1 - \frac{2V_R}{V_p} + \left(\frac{V_R}{V_p}\right)^2}$

$i_{Dp} \approx C \omega V_p \sqrt{\frac{2V_R}{V_p} - \frac{V_R^2}{V_p^2}} + \frac{V_p}{R}$

• Como $V_R \ll V_p \Rightarrow \frac{2V_R}{V_p} \gg \frac{V_R^2}{V_p^2} \Rightarrow$

$i_{Dp} \approx \frac{V_p}{R} \cdot \left(R L C \omega \sqrt{\frac{2V_R}{V_p}} + 1 \right)$
ripple

* Corrente no diodo \rightarrow outra forma de resolver


$$I_D = \bar{I}_{R_L} + I_C \Rightarrow \boxed{\bar{I}_{Dp} = \frac{V_p}{R_L} + C \frac{dV_{out}}{dt}} \quad (1)$$

• Para $t_1 < t \leq t_2$

$$\Rightarrow V_{out} = V_p \cos \omega t$$

(Taylor ($t_2 = \phi$))

$$V_{out} = V_p \cdot \left[\cos \phi (t - \phi)^0 - \cancel{\sin \phi (t - \phi)^1} - \frac{\cos \phi \cdot (\phi - 0)^2}{2! \omega^2 t^2} \right]$$
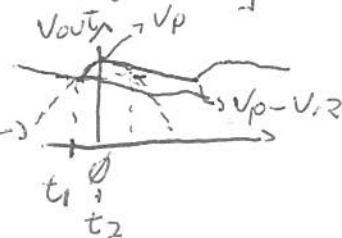
$$\boxed{V_{out} \approx V_p \left[1 - \frac{\omega^2 t^2}{2} \right]} \quad (2) \Rightarrow$$


$$t = t_2 = \phi \Rightarrow V_{out} = V_p$$

$$(2) \cdot \frac{dV_{out}}{dt} \approx -V_p \cdot \frac{d}{dt} \left[\frac{\omega^2 t^2}{2} \right] \Rightarrow \boxed{\frac{dV_{out}}{dt} = -V_p \omega^2 t} \quad (3)$$

$$(2) \cdot t = t_1 \Rightarrow V_{out} = V_p \left[1 - \frac{\omega^2 t_1^2}{2} \right] = V_p - V_r/2 \Rightarrow V_p - \frac{V_p \omega^2 t_1^2}{2} = V_p - V_r/2$$



$$\boxed{t_1 = \frac{t_1}{\omega} \sqrt{\frac{2V_r}{V_p}} \cdot \frac{1}{\omega}} \Rightarrow \boxed{t_1 = -\sqrt{\frac{2V_r}{V_p}} \cdot \frac{1}{\omega}} \quad (4)$$

$$(4) \rightarrow (3) \cdot \frac{dV_{out}}{dt} = -V_p \omega^2 \cdot \left(-\sqrt{\frac{2V_r}{V_p}} \cdot \frac{1}{\omega} \right) \Rightarrow \boxed{\frac{dV_{out}}{dt} = V_p \cdot \omega \sqrt{\frac{2V_r}{V_p}}} \quad (5)$$


$$(5) \rightarrow (1) \cdot I_{Dp} \approx \frac{V_p}{R_L} + C V_p \omega \sqrt{\frac{2V_r}{V_p}} \Rightarrow \boxed{\bar{I}_{Dp} \approx \frac{V_p}{R_L} \left(1 + R_L C \omega \sqrt{\frac{2V_r}{V_p}} \right)}$$

Ok

* Duplicador de tensão

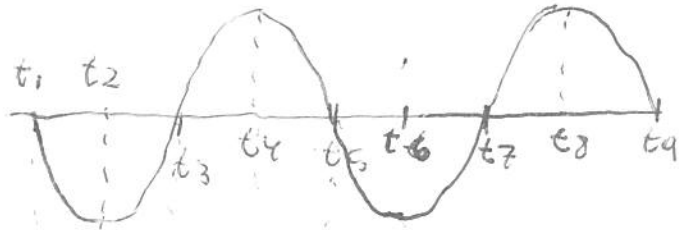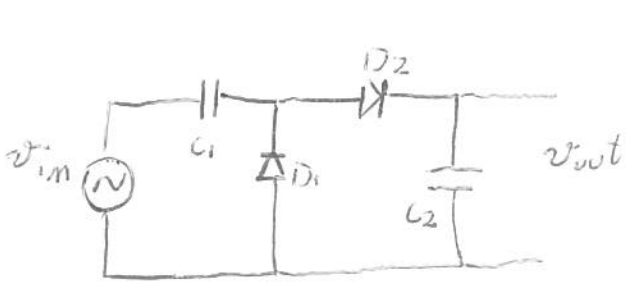

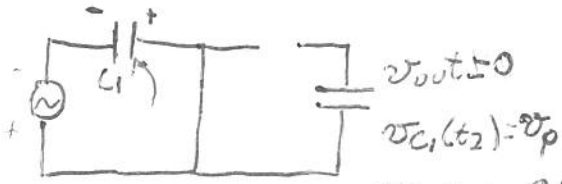
$t_1 < t < t_2 \Rightarrow D_1$ fechado; D_2 aberto



$v_{D_1}(t_2) = 0 (-v_p + v_p)$



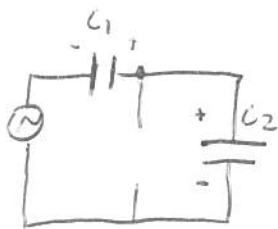$t_2 < t < t_3 \Rightarrow D_1$ aberto; D_2 fechado




$\hookrightarrow v_{D_1} < 0$


\rightarrow Divisor Capacitivo

$\Delta V_C = \frac{V_p}{2} \Rightarrow V_{C_2} = V_p/2$

$V_{C_1} = V_p - V_p/2 = V_p/2$ em t_3

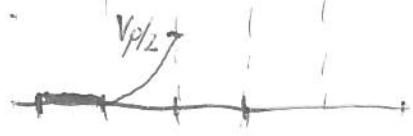

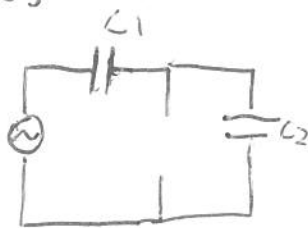
$t_3 < t < t_4 \Rightarrow D_1$ aberto; D_2 fechado



$\Delta V_C = V_p/2$

$V_{C_2} = V_{C_2}(t_3) + \Delta V_C$


$V_{C_1} = V_{C_1}(t_3) + \Delta V_C$

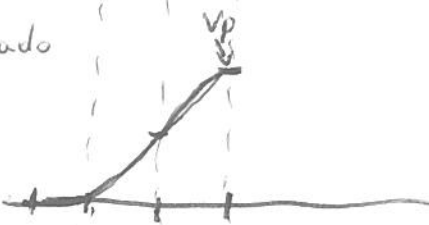

$\Delta V_{C_2}(t_4) = V_p$


$V_{C_1}(t_4) = 0$

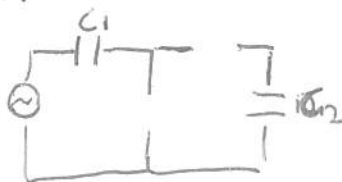$t_4 < t < t_5 \Rightarrow D_1$ aberto; D_2 aberto




$v_{C_2}(t_5) = v_{C_2}(t_4) = V_p$

$v_{C_1}(t_5) = v_{C_1}(t_4) = 0$

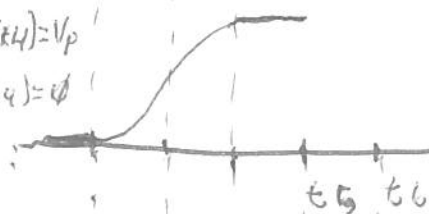


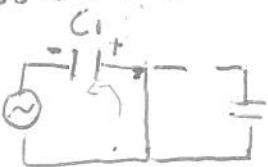$t_5 < t < t_6 \Rightarrow D_1$ fechado; D_2 aberto




$v_{C_2}(t_6) = v_{C_2}(t_5) = V_p$

$v_{C_1}(t_6) = V_p$

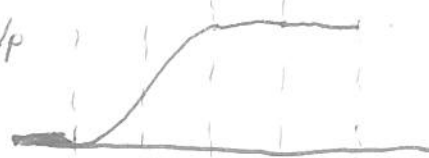


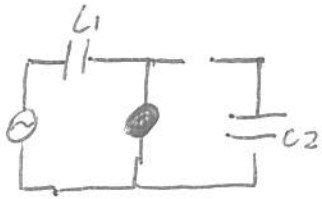$t_6 < t < t_7 \rightarrow D_1$ Aberto; D_2 aberto




$$V_{C_2}(t_7) = V_{C_2}(t_6) = V_p$$

$$V_{C_1}(t_7) = V_{C_2}(t_6) = V_p$$

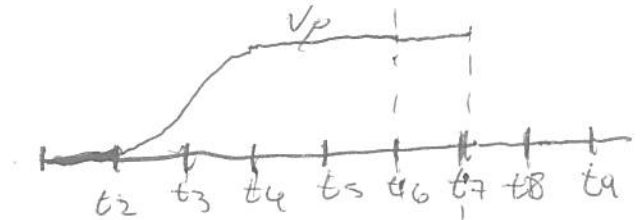

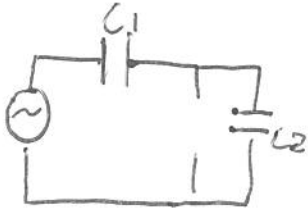$t_7 < t \leq t_8 \rightarrow D_1$ aberto; D_2 fechado




$$\Delta V_{C_2} = V_p/2$$


$$V_{C_2}(t_8) = V_{C_2}(t_7) + V_p/2$$

$$V_{C_2}(t_8) = V_{C_1}(t_7) + V_p/2$$
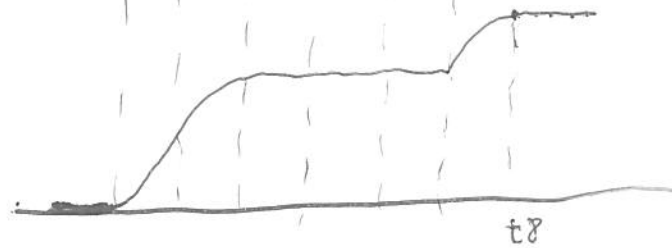
$$\Rightarrow \begin{cases} V_{C_2}(t_8) = V_p + V_p/2 \\ V_{C_1}(t_8) = V_p - V_p/2 \end{cases}$$



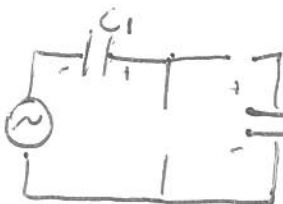$t_8 < t \leq t_9 \rightarrow D_1$ aberto e D_2 Aberto



$$V_{C_2}(t_9) = V_{C_2}(t_8) = V_p + V_p/2$$

$$V_{C_1}(t_9) = V_{C_1}(t_8) = V_p/2$$